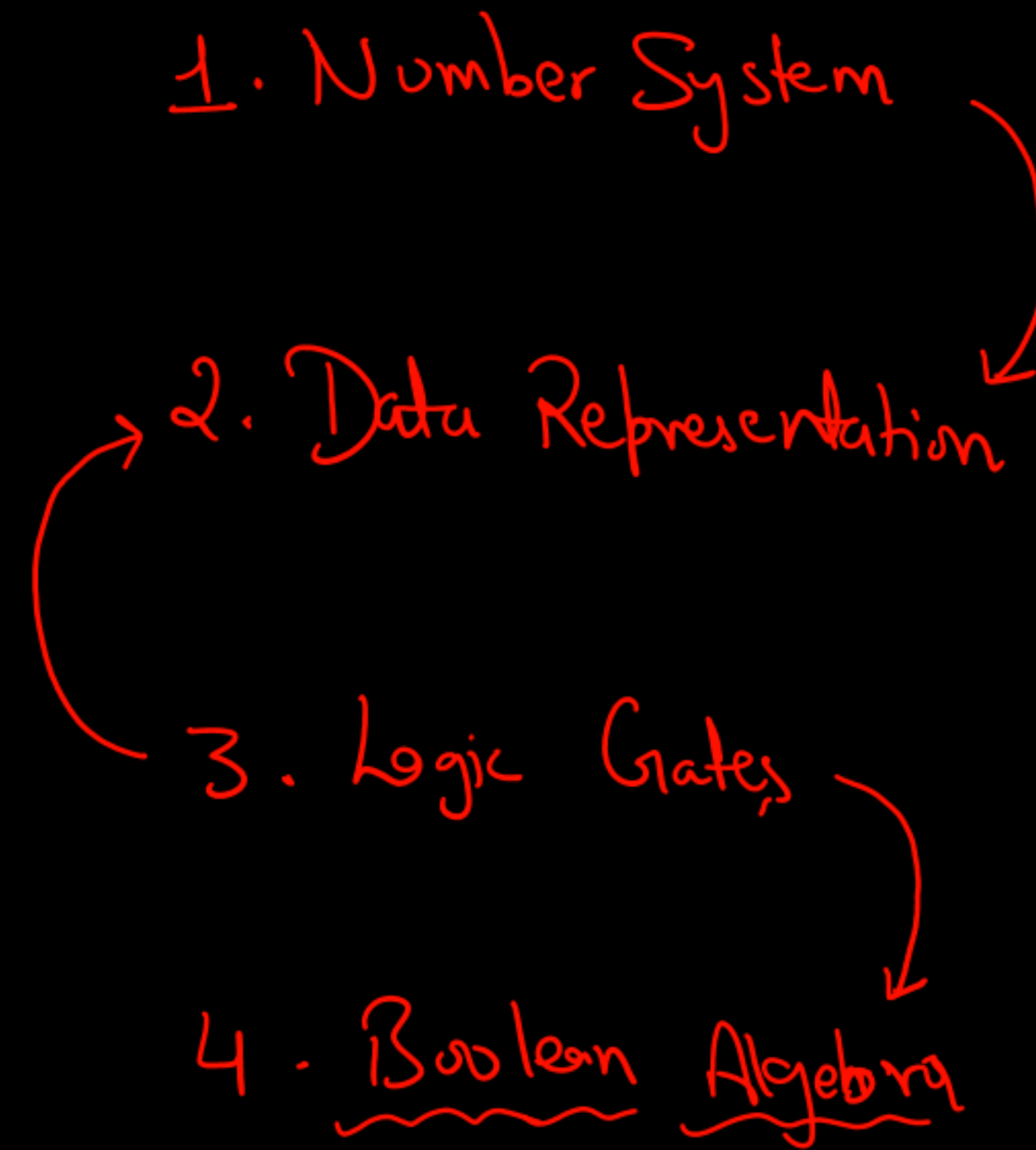


Digital Electronics
UNIT-04
Boolean Algebra

1. Number System
 2. Data Representation
 3. Logic Gates
 4. Boolean Algebra
- 

Boolean Algebra

↳ George Boole → Book → The Laws of thought
(1854)

Boolean Algebra

↳ It is a mathematics of two variables - 'high' and 'low', that is
used to analyse and simplify the digital circuit
↳ (logic)

→ Only Binary numbers are used, i.e. $\text{Value} = \{0, 1\}$

Following are the basic important rules used in Boolean Algebra


1) Variables used can have any two values, i.e. 0 or 1

2) Complement of a variable is represented by 'overbar' ($\bar{}$) or prime (')

Ex. $A=0, \quad \bar{A}=1, \quad A'=1$


3) OR-ing: ORing of a variable is represented by (+) plus symbol.

Ex. $A+B \rightarrow A \text{ OR } B$
 $A \text{ OR } B \text{ OR } C \rightarrow A+B+C$

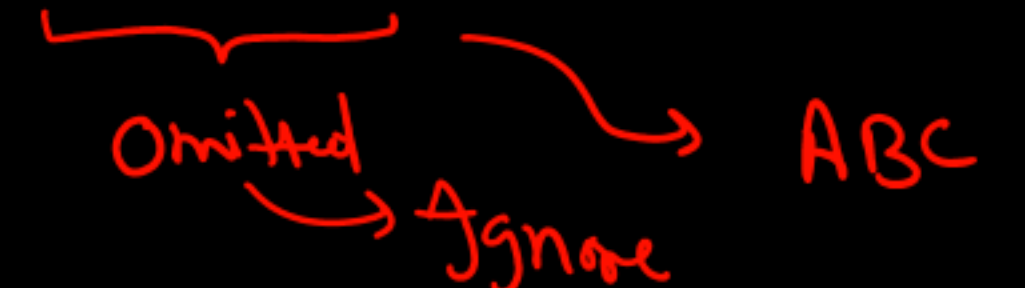4) AND-ing: If two or more variables are represented by writing a dot (\cdot) between them such as $A \cdot B \cdot C \Rightarrow A \text{ AND } B \text{ AND } C$


Boolean Laws


AND Law

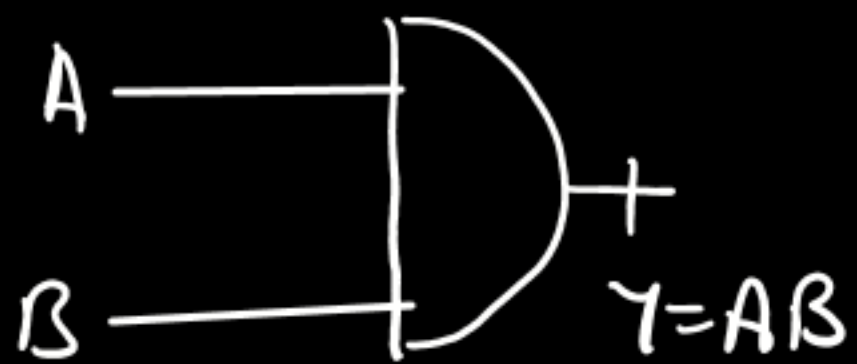

$A = B = \text{High}, \text{O/p} = \text{high}$

- a) $A \cdot 0 = 0$ (Disabled)
- b) $A \cdot 1 = A$ (Enabled)
- c) $A \cdot A = A$ (Buffer)
- d) $A \cdot \bar{A} = 0$ (Disabled)

OR Law

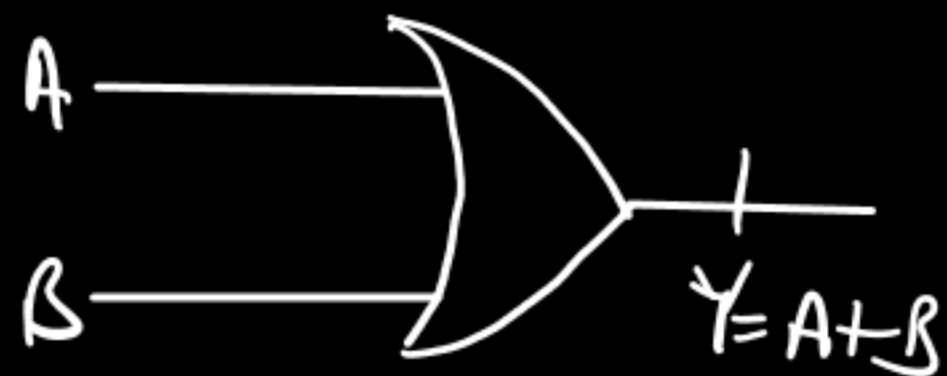

$A \text{ / } B = 1, \text{O/p} = 1$

- a) $A + 0 = A$ (Enabled)
- b) $A + 1 = 1$ (Disabled)
- c) $A + A = A$ (Buffer)
- d) $A + \bar{A} = 1$ (Disabled)

Inversion Law

↳ The law uses NOT operation.

$$\overline{\overline{A}} = A$$

⇒ The double inversion of a variable results the original variable itself.

$$A = 0 \quad \overline{\overline{A}} \Rightarrow \overline{1} = 0$$

$$A = 1, \quad \overline{\overline{A}} = \overline{0} = 1$$

Commutative law:

↳ If we change the sequence of the variables it does not have any effect on the output of the logical circuit

$$\underline{\text{Ex}} \quad A + B = B + A, \quad A \cdot B = B \cdot A$$

Associative Law:

↳ This law states that the order in which the logic operation are performed is irrelevant as their effect is same.

↳ unwanted / wrong / unexpected

followed by AND, OR, XOR, XNOR ✓

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

⇒ NAND & NOR gates do not follow this law

Distributive Law:

↳ It states the following condition:



$$A \cdot (B + C) = AB + AC \quad \checkmark \quad \longleftarrow \text{Same as Normal algebra.}$$

De-Morgan's first Theorem: $\overline{AB} = \overline{A} + \overline{B}$


A	B	AB	\overline{AB}	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$\overline{AB} = \overline{A} + \overline{B}$
NAND gate \longleftarrow OR gate

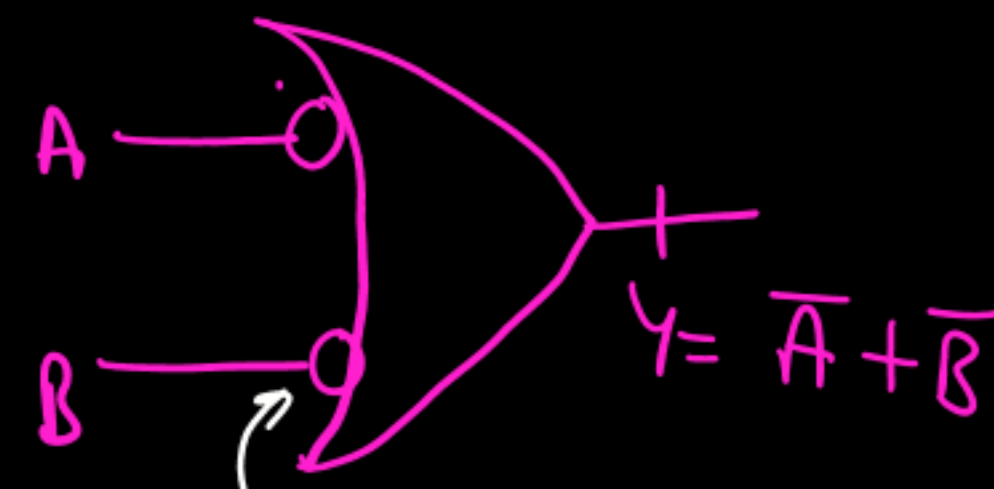
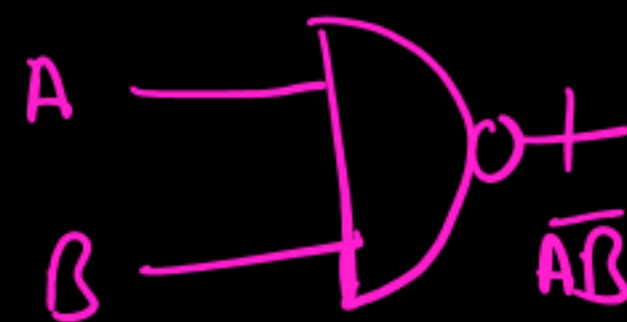
$$\overline{AB} = \overline{A} + \overline{B}$$



Bubble implies Inversion

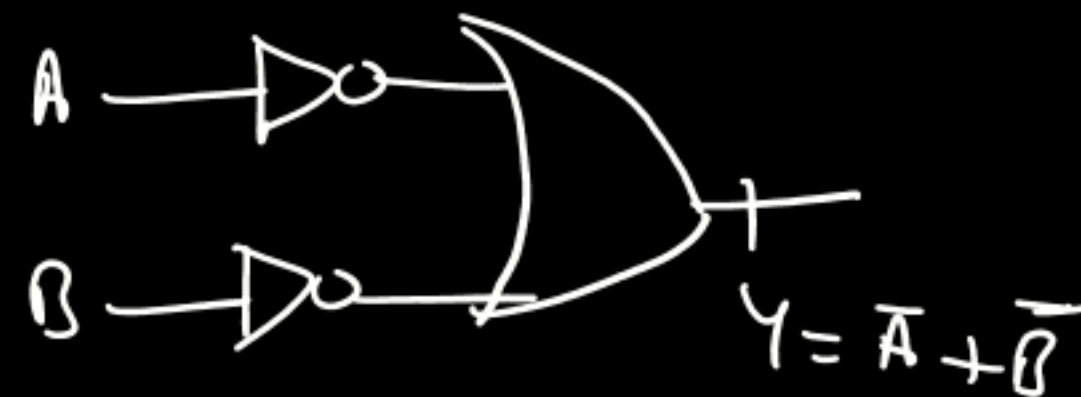

Using Venn Diagram

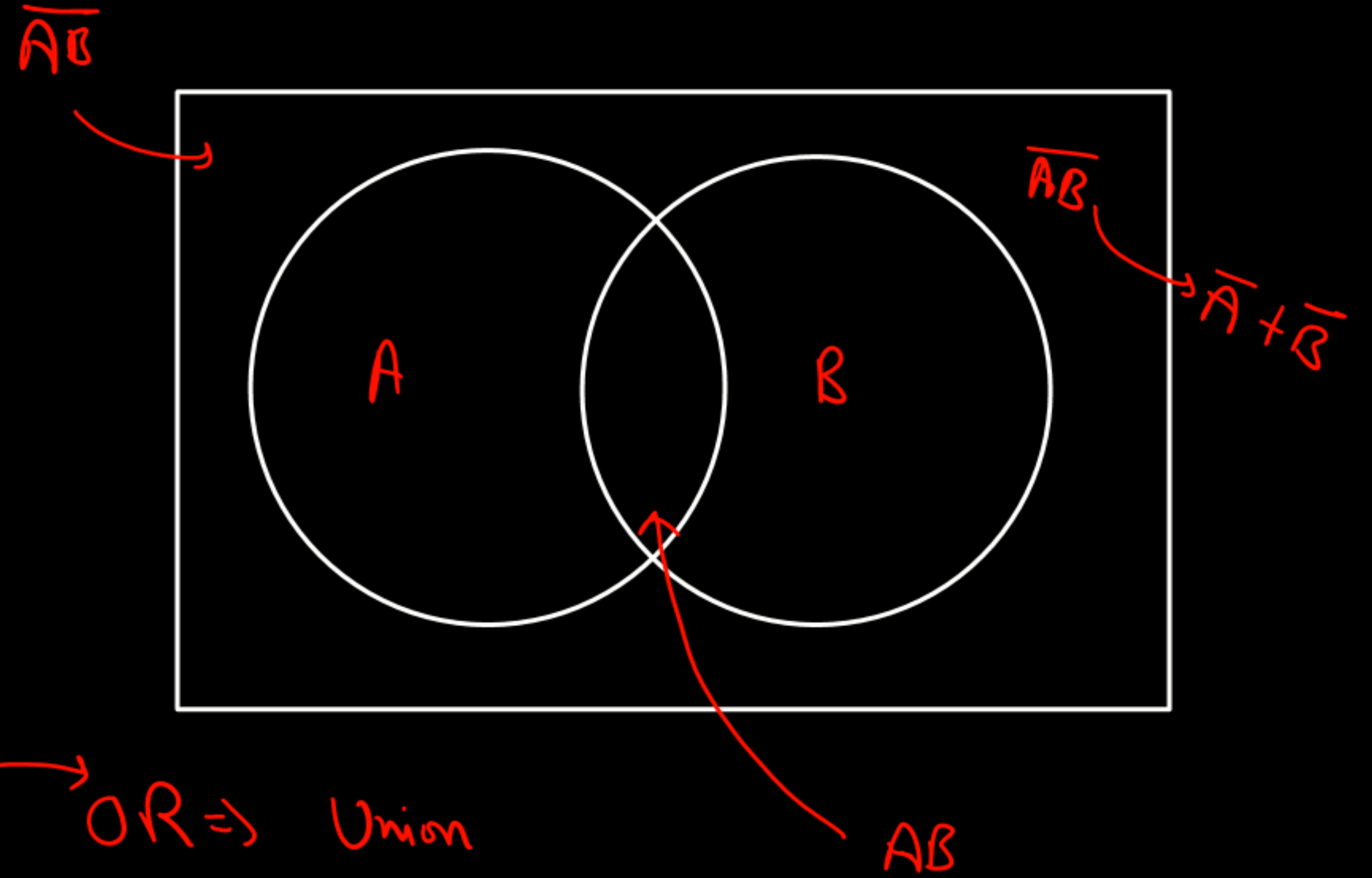
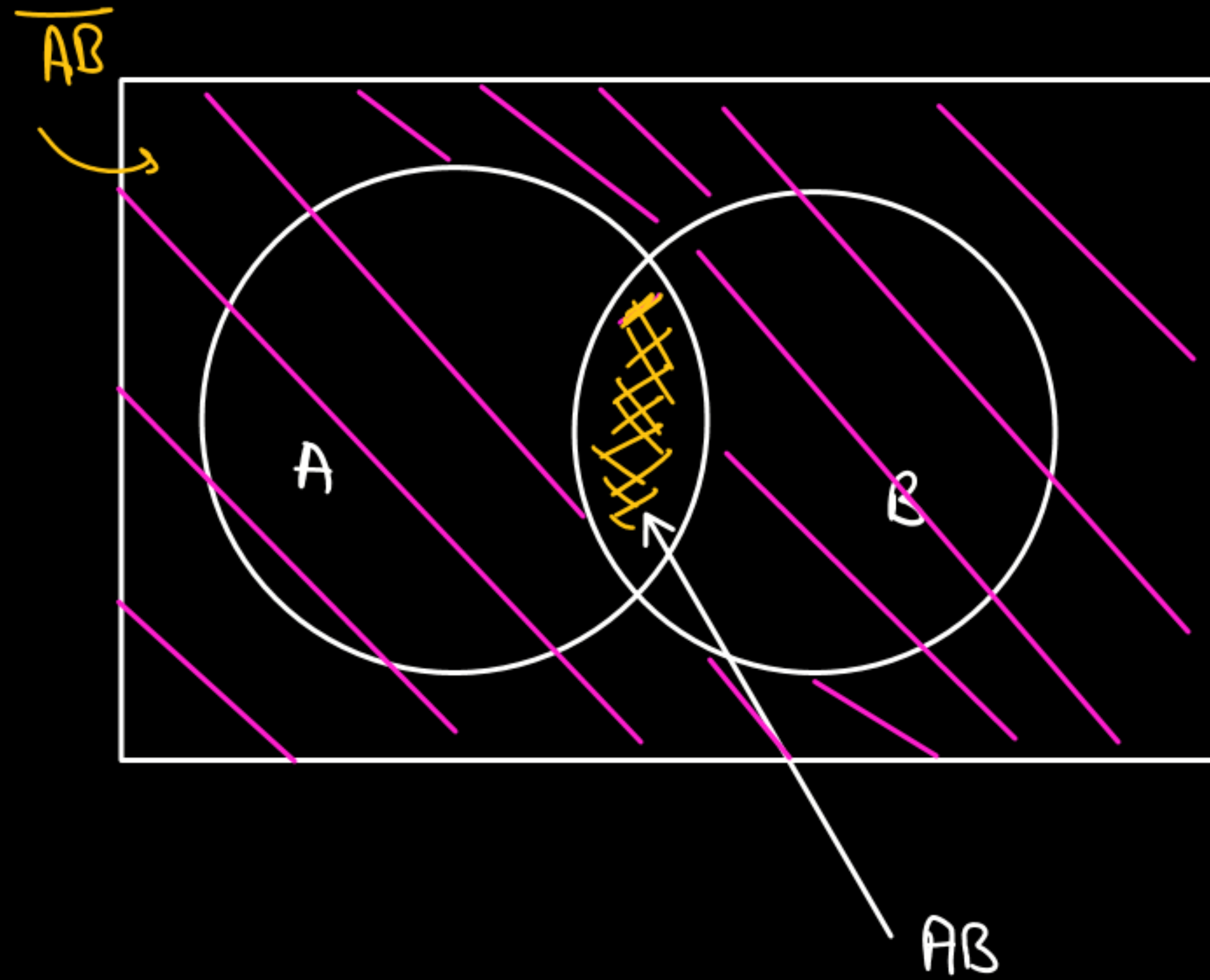


$A \cup B$ \rightarrow OR \Rightarrow Union
 $A \cap B$ \rightarrow AND = Intersection

De-Morgan's Second Theorem: $\overline{A+B} = \bar{A} \cdot \bar{B}$

A	B	A+B	$\overline{A+B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$\overline{A+B} = \bar{A} \cdot \bar{B}$

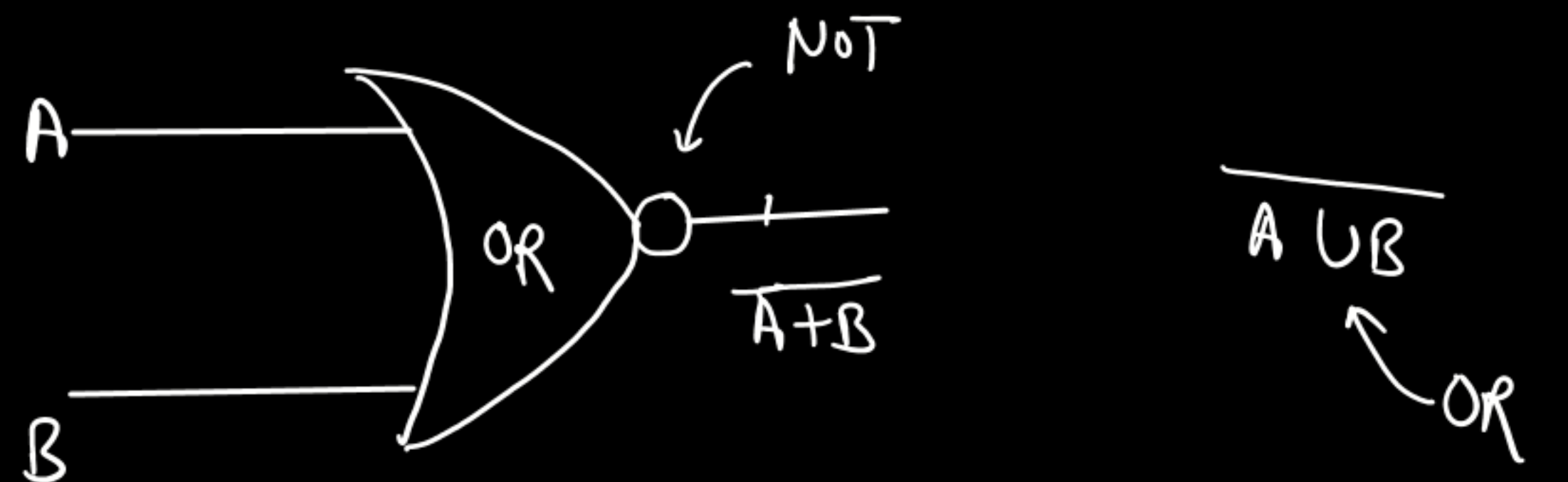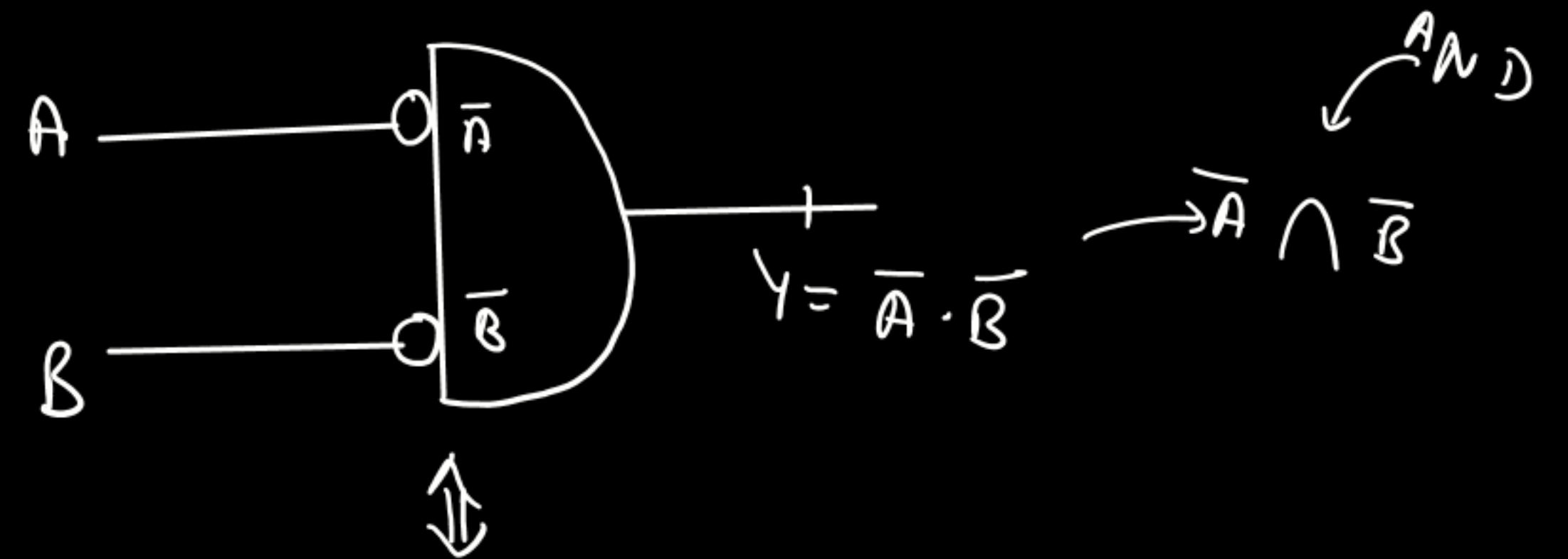


Bubbled Input AND gate = NOR gate

↓
Inverter

Implication & Inhibition

Implication

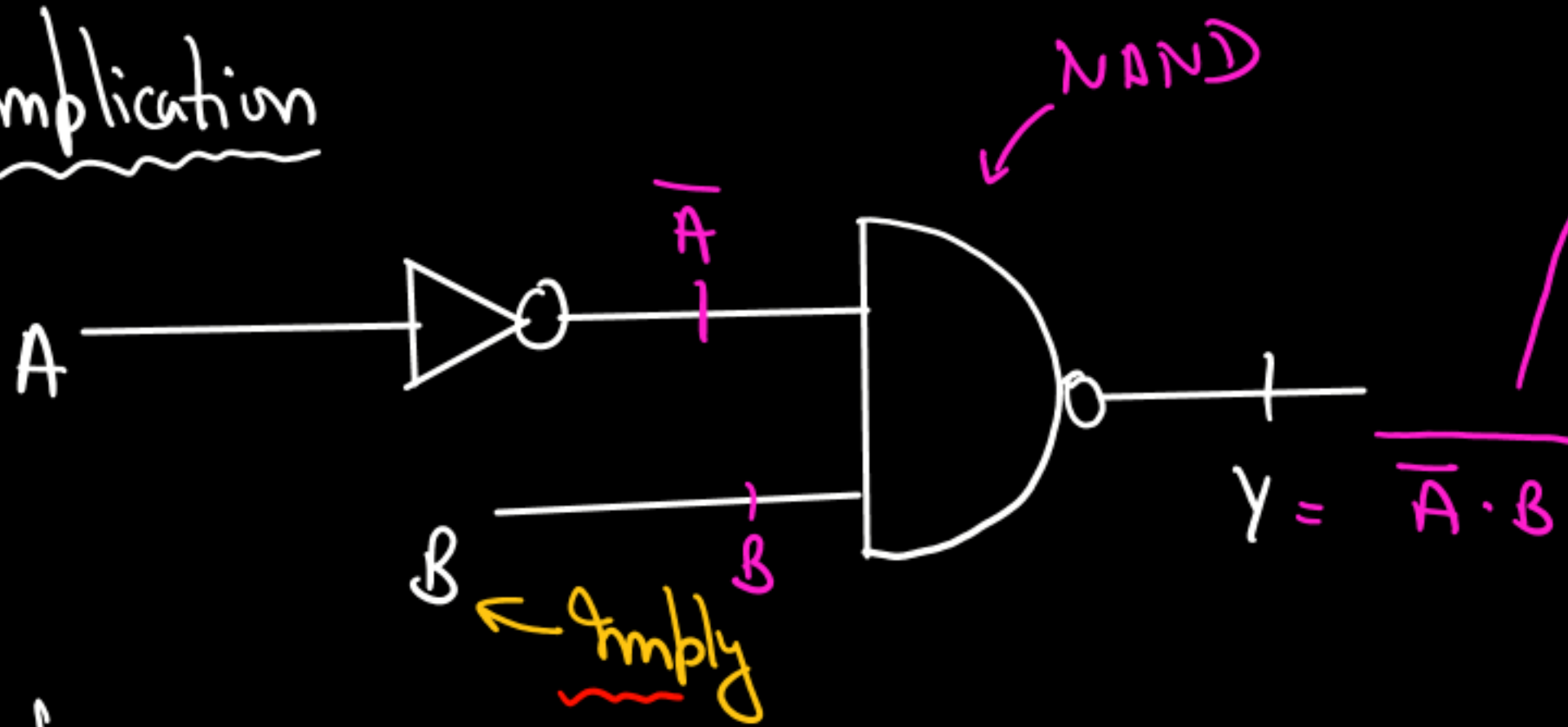


$$\overline{AB} = \bar{A} + \bar{B}$$

$\bar{A} + \bar{B}$
Inversion law
 $\Rightarrow \bar{A + B}$

Input $\rightarrow \bar{A} \rightarrow A$
 $B \rightarrow \bar{B}$

Inhibition

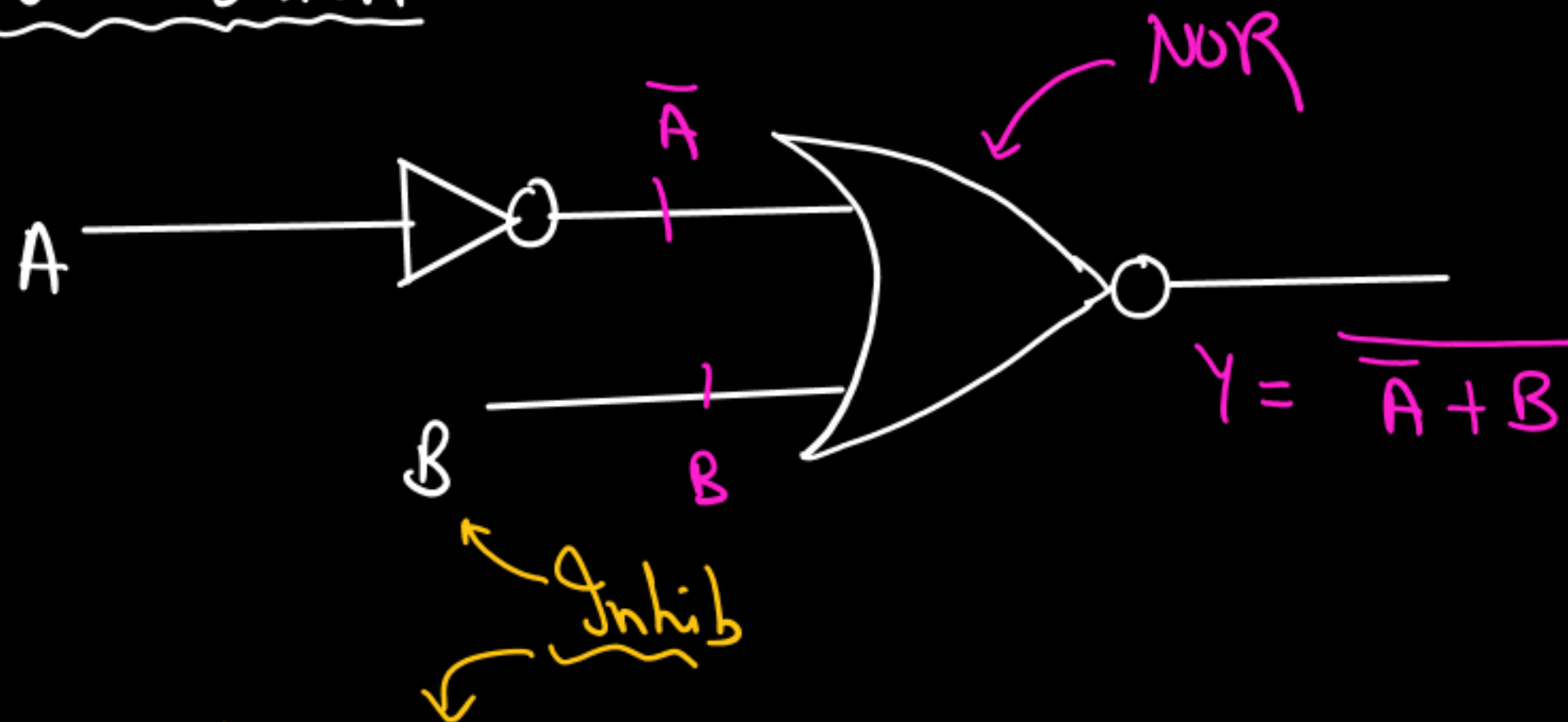

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

$\bar{A} + \bar{B} = \bar{A} \cdot \bar{B}$
Inversion law
 $= \overline{A \cdot B}$

$$\bar{\bar{A}} = A$$

\Rightarrow If Inhib = 1, then A will not reach to output

$\Rightarrow A \cdot \bar{B}$, $B=1$, $\Rightarrow A \cdot \bar{1} = A \cdot 0 = 0$

\times Inhib = 1, $B=1$, $Y = A + \bar{B}$

$\Rightarrow A + \bar{1} = A + 0 = A$

\hookrightarrow if Inhib = 1, $A \rightarrow$ output

