
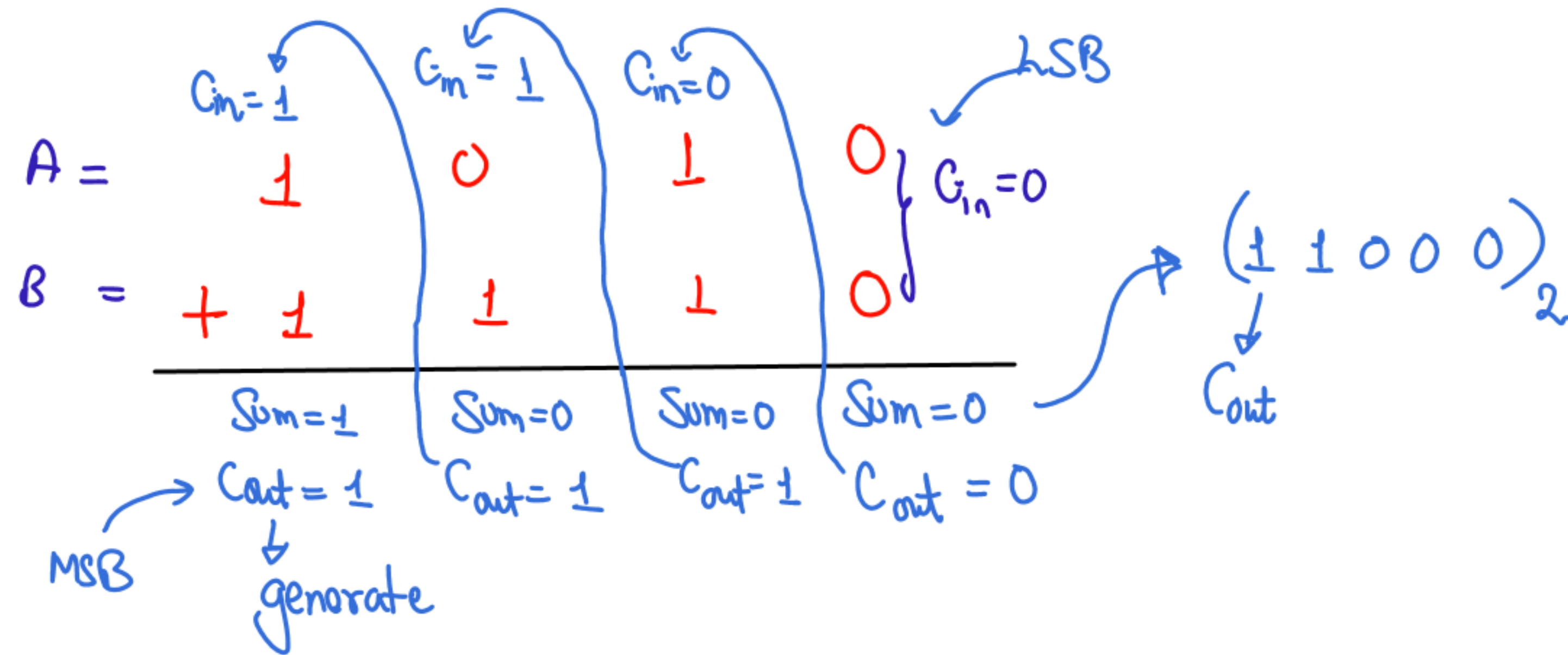



Parallel Adder Circuit:

'It is a chain of full adders connected parallelly where the C_{in} of a adder is the C_{out} of previous adder.'

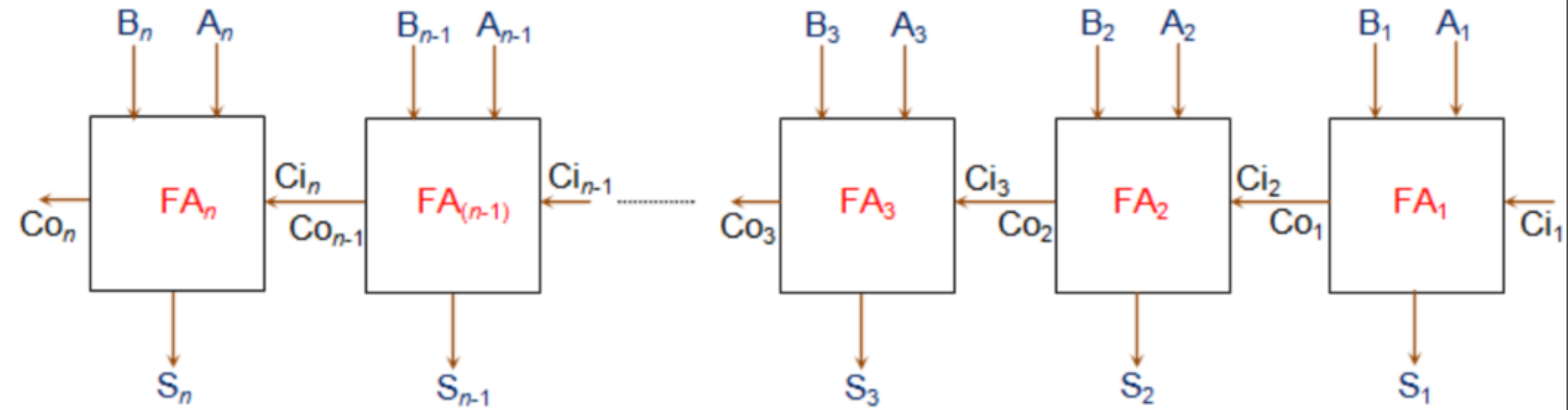* It is also called as ripple carry adder.



Propagation Delay in Parallel Adder

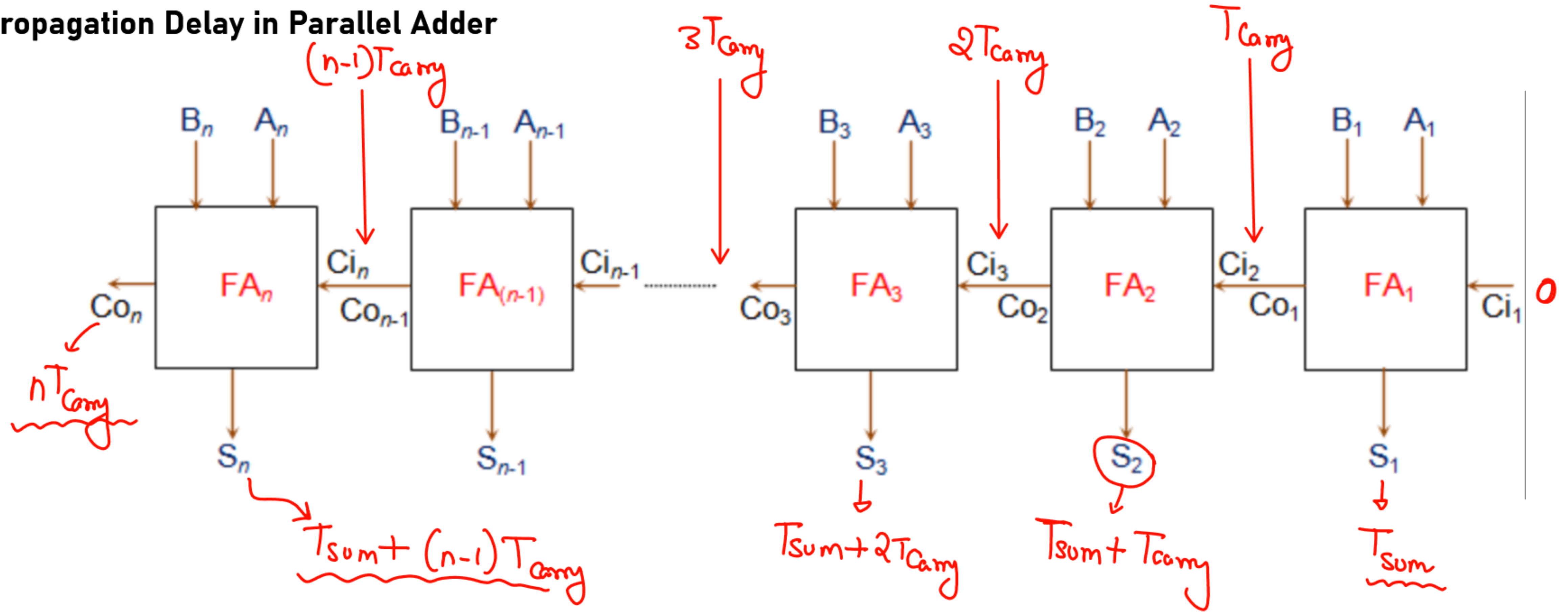

Suppose time taken by a full adder
for sum = T_{sum}
for Carry out = T_{carry}

$$\begin{aligned} S_n &= T_{\text{sum}} + (n-1)T_{\text{carry}} \\ Co_n &= nT_{\text{carry}} \end{aligned} \rightarrow \text{max}$$

Parallel Subtractor using full adder

A Parallel subtractor is a digital circuit Capable to find the diff. b/w 2^{or} more than two bits.

$$A - B \rightarrow A + \bar{B} + 1$$


$$= A + 2's \text{ Complement of } B$$

$$= A + [1's \text{ Complement of } B] + 1$$

3 bits

XOR Property	
$B \oplus 0 = B$	
$B \oplus 1 = \bar{B}$	

Inverter

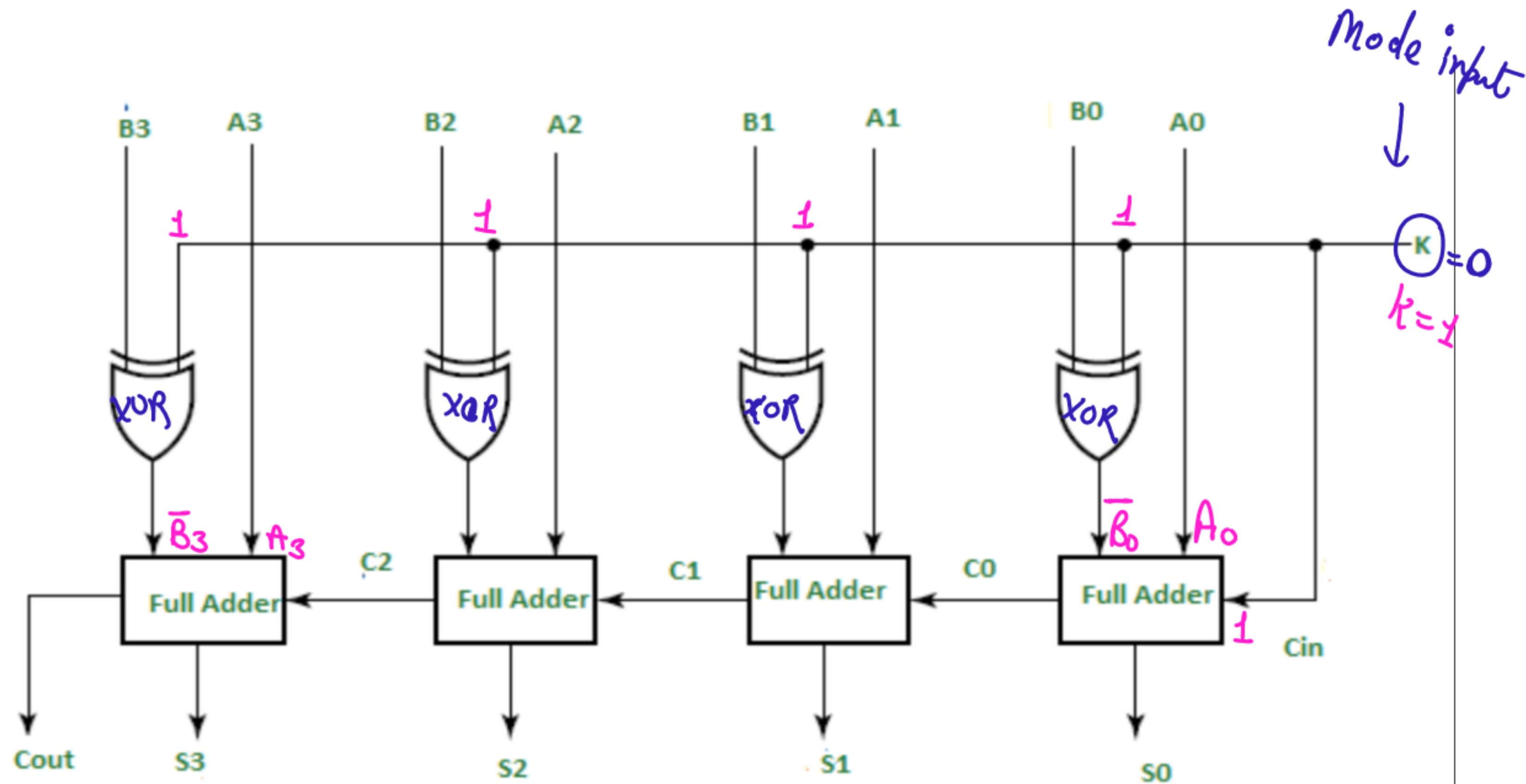

If Mode Input (K) = 0 then it works as Parallel Adder.

$$S = A_0 + \bar{B}_0 + 1$$

Propagation delay in full adder:

if $A=B=1$

$T_{X1} \Rightarrow$ No delay

$Y = T_{A2}$ but if $C_{in} = 0$, then No delay for Sum

Sum depends on Carry

else $C_{in} = 1$, then $T_{Sum} = T_{X2}$

if $C_{in} = 0$, $z = 0$ (No delay)

$C_{in} = 1$, $z = 0$ (No delay)

$$C_{out} = T_{A1} + T_{OR}$$

if $A=0$ & $B=1$ OR $A=1$ & $B=0$


$y =$ No delay, if $C_{in} = 1$

\Rightarrow Sum = 0 (no delay)

if $C_{in} = 0$

\Rightarrow Sum = $[T_{X1} + T_{X2}]$

$$C_{out} = T_{X1} + T_{A2} + T_{OR}$$

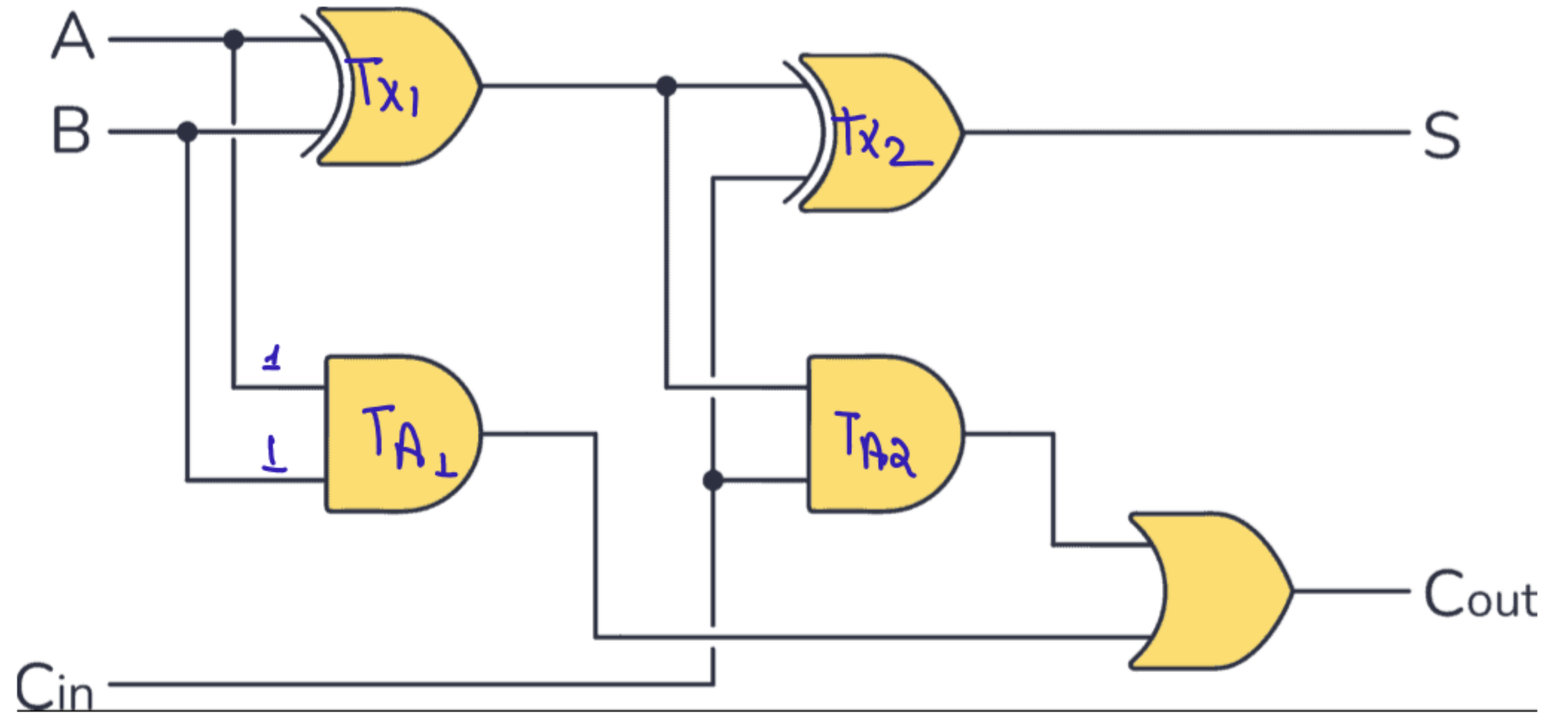

Overall delay:

$$\text{Sum} = T_{X1} + T_{X2} + \underline{T_{cin}}$$

$$\text{Cost} = T_{X1} + T_{A2} + T_{OR}$$

If inputs are identical then we will not add the delay of Carry input


Serial Adder

* That adds upto 'n' bits by using single full adder by performing operation for 'n' times.

→ It is slower than Parallel adder

Handle the process

Send sequence of bits <

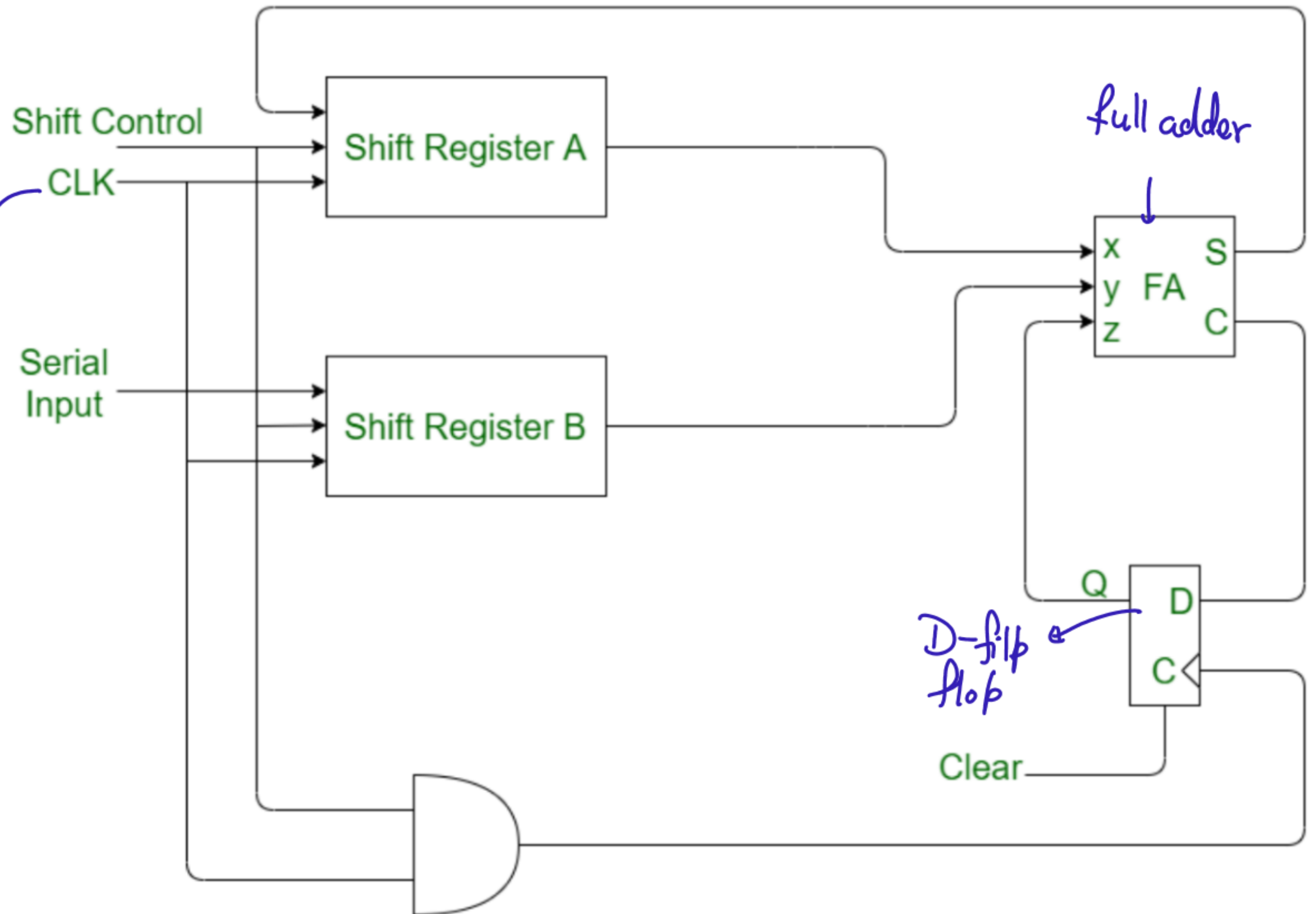

Code Converter

↳ A Code Converter is a circuit that Convert the Binary Code to other Codes.


Ex
↓
BCD \rightarrow XS-3
Excess -3 \rightarrow BCD
BCD \rightarrow Gray Code
BCD \rightarrow 7-Segment Code.

Code Compensator
↓
Compare the JIP Values
& gives the o/p.

Magnitude Comparator

↳ It is a digital circuit that
Compares two values
↓
Binary

→ less than
→ greater than
→ equals to

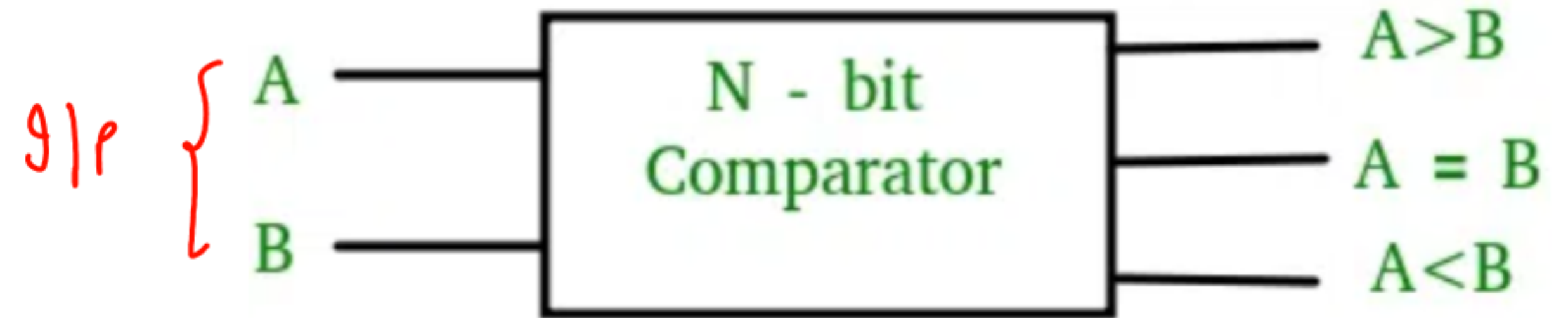

* here A & B are not only a single bit
It can be multiple bit number

eg

A = 0

B = 1

Single
bit

A = 10

B = 01

two digit

A = 101

B = 111

3 bit
number

1 bit Magnitude Comparator

A & B holds single Bit

	A	B	A < B	A = B	A > B
0	0	0	0	1 $\bar{A}\bar{B}$	0
1	0	1	1 $\bar{A}B$	0	0
2	1	0	0	0	1 $A\bar{B}$
3	1	1	0	1 AB	0


Expression

$$A < B : \bar{A}B$$

$$A = B : AB + \bar{A}\bar{B} \rightarrow A \odot B$$

$$\underline{A > B : A\bar{B}}$$

1 bit Magnitude Comparator

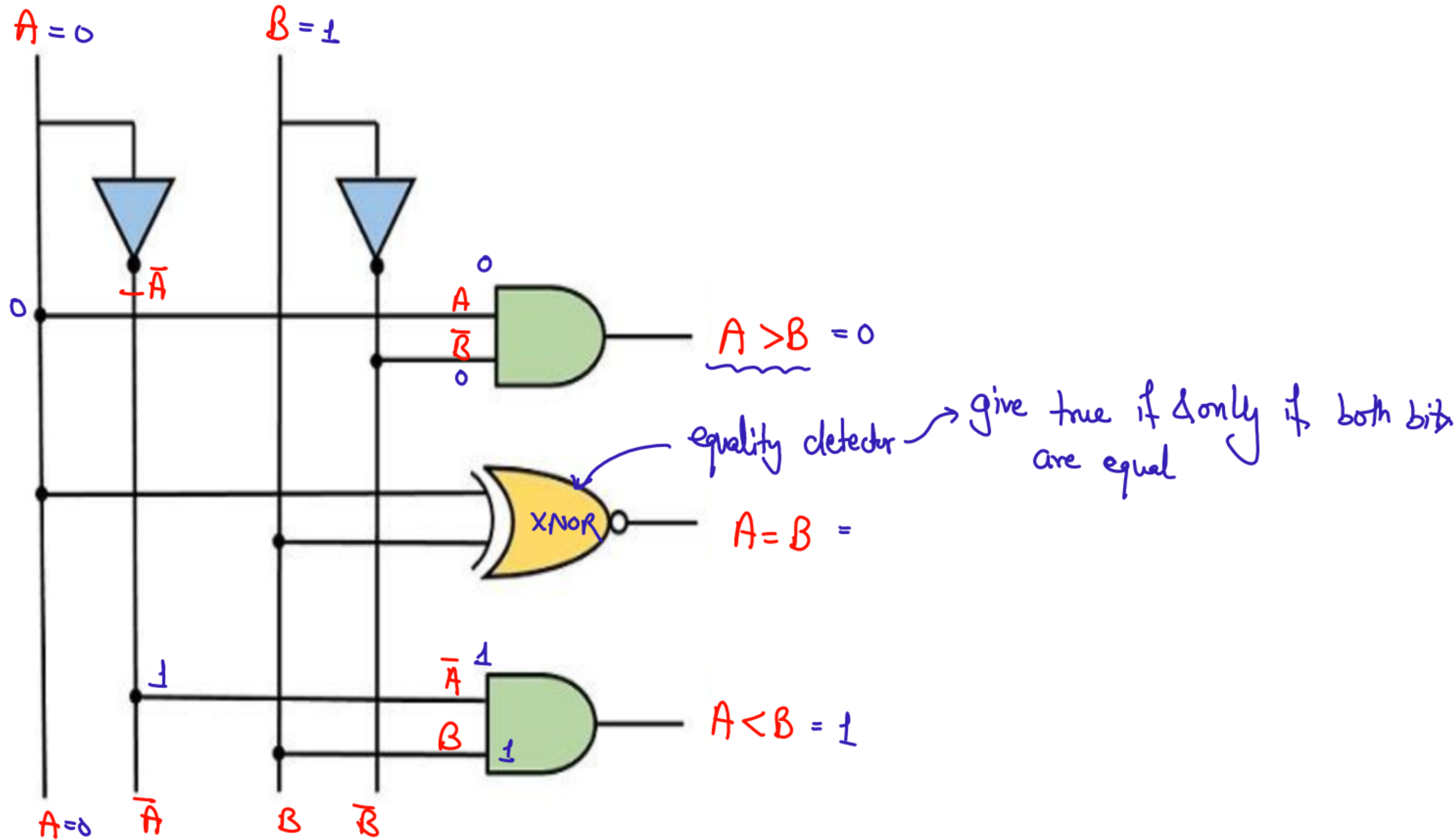

2 bit magnitude comparator

Compares two bit numbers

$A = A_1 A_0$ $B = B_1 B_0$

MSB

LSB

MSB

LSB

INPUT				OUTPUT		
A1	A0	B1	B0	A<B	A=B	A>B
0	0	0	0	0	1 _{m0}	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1 _{m5}	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1 _{m10}	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1 _{m15}	0

A > B

B1B0 \ A1A0	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
10	1	1	0	0

$$A_1 \bar{B}_1 + (A_1 \odot B_1) \cdot A_0 \bar{B}_0$$

A = B

B1B0 \ A1A0	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1

$$(A_1 \odot B_1) \cdot (A_0 \odot B_0)$$

A < B

B1B0 \ A1A0	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

$$\bar{A}_1 B_1 + (A_1 \odot B_1) \cdot \bar{A}_0 B_0$$

* Use these Expressions
to make logic
circuit

$$\underline{A = B}$$

$$A = A_1 A_0$$

$$B = B_1 B_0$$

$$(A_1 \odot B_1) \cdot (A_0 \odot B_0) \rightarrow \text{XNOR}$$

$A=B$ then $Y=1$

If $A_1=B_1$ & $A_0=B_0$

then we can say $A=B$

$$\underline{A > B}$$

$$A = A_1 A_0$$

$$B = B_1 B_0$$

$$A_1 \bar{B}_1 + (A_1 \odot B_1) \cdot A_0 \bar{B}_0$$

Check for
MSB
if $A > B$
O/P = 1

if A_1 is
not greater
than B_1 ,
then, compare
of equality

If equal
then we
check for
 $A_0 > B_0$

$$\underline{A < B}$$

$$A = A_1 A_0$$

$$B = B_1 B_0$$


$$\bar{A}_1 B_1 + (A_1 \odot B_1) \bar{A}_0 B_0$$

$A_1 < B_1$,
the
return True
(1)

If they
are equal
then
O/P = 1

Return
True if
 $A < B$
O/P = 1

2 bits magnitude comparator circuit

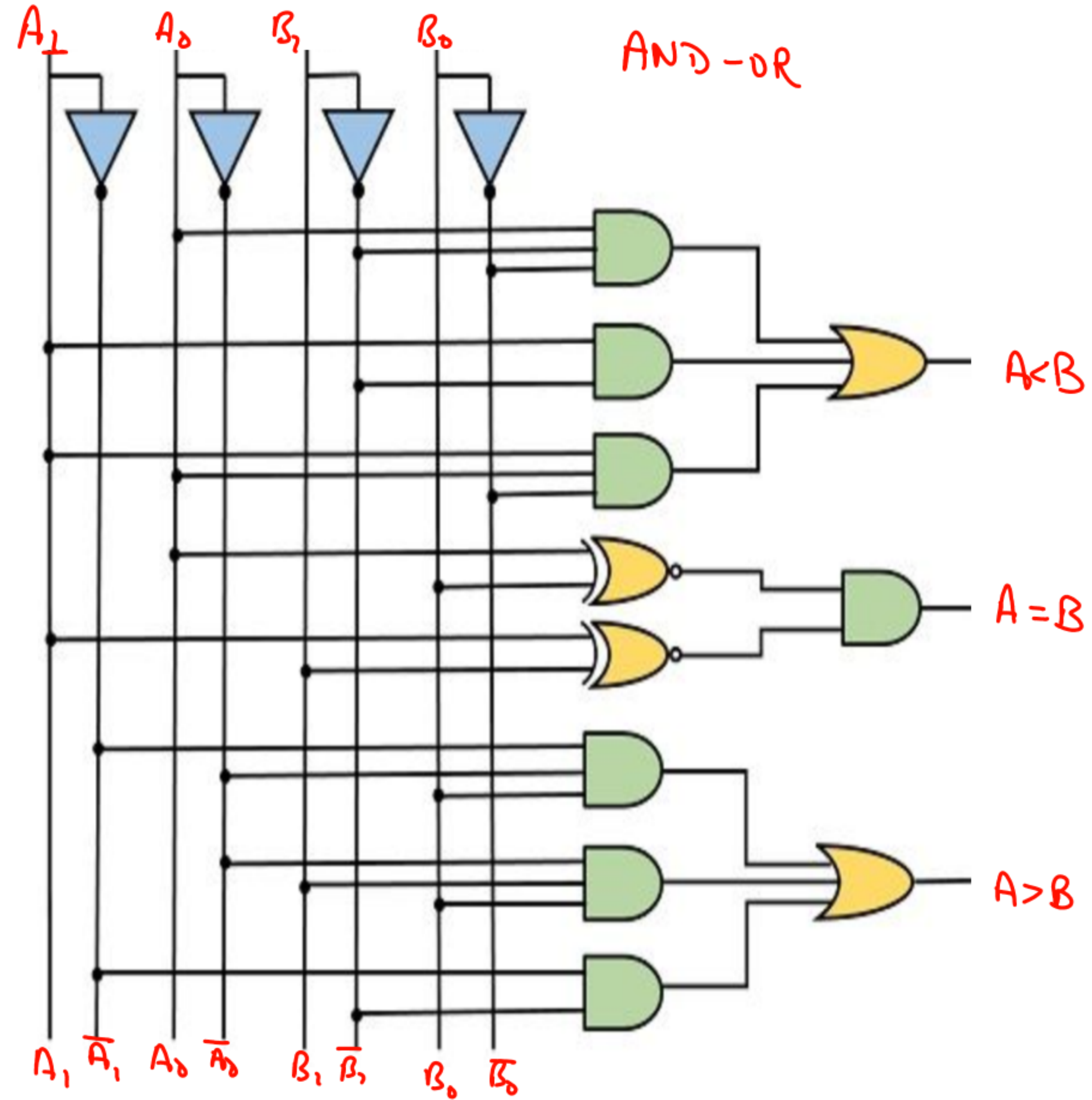

BCD to XS-3 Converter

BCD to XS-3 Converter (also called BCD to Excess-3 code converter) is a combinational circuit that takes a 4-bit Binary Coded Decimal (BCD) input and produces the corresponding Excess-3 code as output.

Excess-3 code is a non-weighted code used to express decimal numbers. It is derived by adding 3 (i.e., 0011_2) to the BCD number.

	BCD Code				Excess-3 Code			
	B ₃	B ₂	B ₁	B ₀	X ₃	X ₂	X ₁	X ₀
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10	1	0	1	0	X	X	X	X
11	1	0	1	1	X	X	X	X
12	1	1	0	0	X	X	X	X
13	1	1	0	1	X	X	X	X
14	1	1	1	0	X	X	X	X
15	1	1	1	1	X	X	X	X

$$\begin{aligned}
 X_3 &= \sum m(5, 6, 7, 8, 9) \\
 X_2 &= \sum m(1, 2, 3, 4, 9) \\
 X_1 &= \sum m(0, 3, 4, 7, 8) \\
 X_0 &= \sum m(0, 2, 4, 6, 8)
 \end{aligned}
 \left. \vphantom{\begin{aligned} X_3 \\ X_2 \\ X_1 \\ X_0 \end{aligned}} \right\} + d(10, 11, 12, 13, 14, 15)$$

don't care

X_3

$B_3 B_2$	$B_1 B_0$	00	01	11	10
00	0				
01	4	1	1	1	
11	12	X	X	X	X
10	8	1	1	X	X

Annotations: $B_2 B_1$ (green box), $B_2 B_0$ (blue box), B_3 (pink box).

$$X_3 = B_3 + B_2 B_1 + B_2 B_0$$

X_0

$B_3 B_2$	$B_1 B_0$	00	01	11	10
00	0	1			1
01	4	1			1
11	12	X	X	X	X
10	8	1		X	X

Annotation: B_0 (pink box).

$$X_0 = B_0$$

X_2

$B_3 B_2$	$B_1 B_0$	00	01	11	10
00	0		1	1	1
01	4	1			
11	12	X	X	X	X
10	8		1	X	X

Annotations: $B_2 B_1$ (green box), $B_2 \bar{B}_1 \bar{B}_0$ (green box), $B_2 B_1$ (yellow box), $B_0 \bar{B}_2$ (pink box).

$$X_2 = B_2 \bar{B}_1 \bar{B}_0 + B_0 \bar{B}_2 + B_1 \bar{B}_2$$


X_1

$B_3 B_2$	$B_1 B_0$	00	01	11	10
00	0	1		1	
01	4	1		1	
11	12	X	X	X	X
10	8	1		X	X

Annotations: $\bar{B}_1 \bar{B}_0$ (pink box), $B_1 B_0$ (pink box).

$$X_1 = \bar{B}_1 \bar{B}_0 + B_1 B_0 = B_1 \odot B_0$$

BCD to XS-3 Code Converter

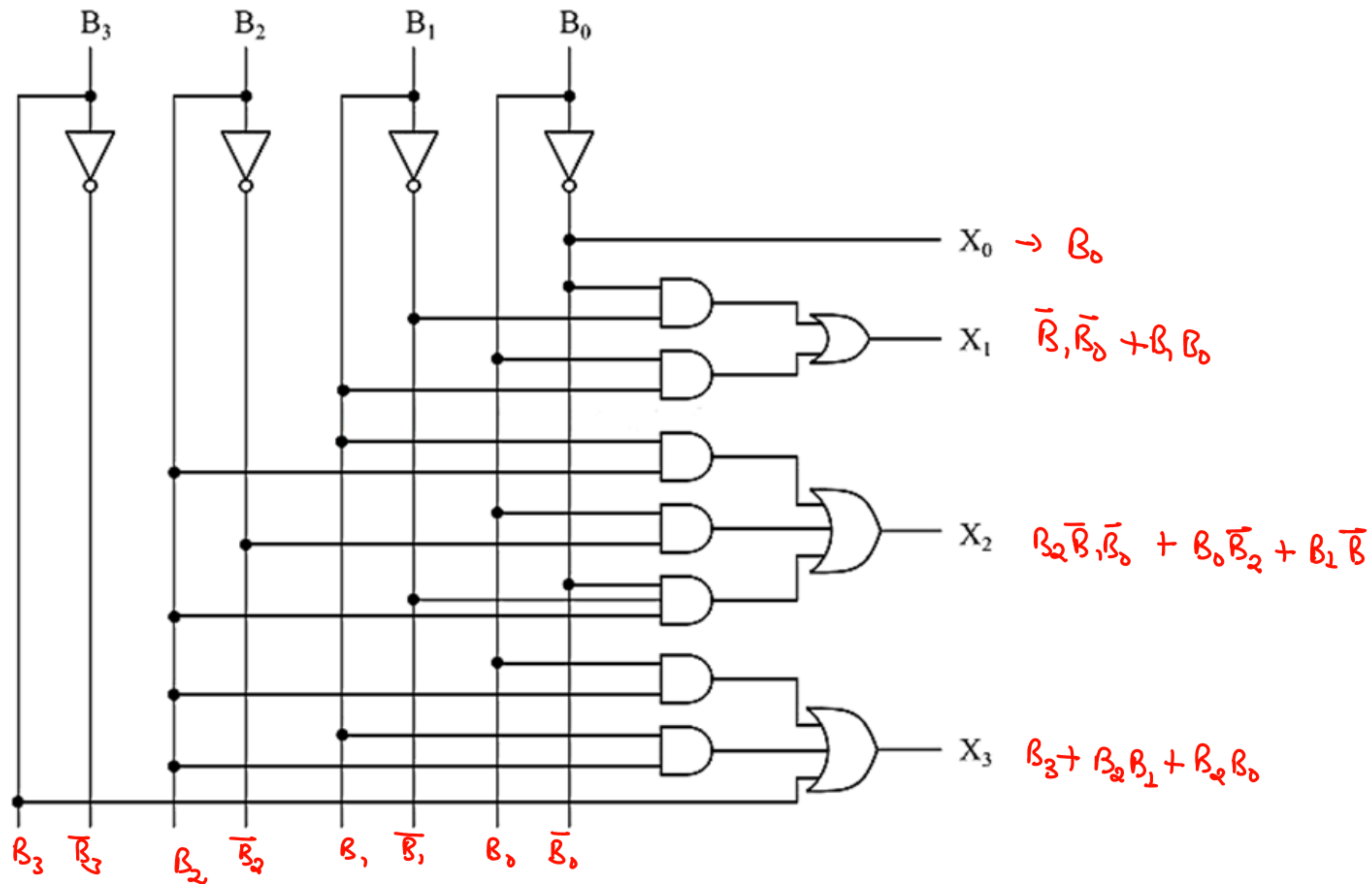

Binary to Gray Code

In Gray Code only one bit changes at a time.

In BCD, only 10 combinations can be made using 4 bits. (0 to 9).

For each Gray code output is D3, D2, D1 and D0.

	Binary Code				Gray Code			
	B3	B2	B1	B0	D3	D2	D1	D0
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1✓
2	0	0	1	0	0	0	1✓	1✓
3	0	0	1	1	0	0	1✓	0
4	0	1	0	0	0	1	1✓	0
5	0	1	0	1	0	1	1✓	1✓
6	0	1	1	0	0	1	0	1✓
7	0	1	1	1	0	1	0	0
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1✓
10	1	0	1	0	1	1	1✓	1✓
11	1	0	1	1	1	1	1✓	0
12	1	1	0	0	1	0	1✓	0
13	1	1	0	1	1	0	1✓	1✓
14	1	1	1	0	1	0	0	1✓
15	1	1	1	1	1	0	0	0

don't
care

$$D_3 = \sum m(8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$D_2 = \sum m(4, 5, 6, 7, 8, 9) + d(10, 11)$$

$$D_1 = \sum m(2, 3, 4, 5) + d(10, 11, 12, 13)$$

$$D_0 = \sum m(1, 2, 5, 6, 9) + d(10, 13, 14)$$

Binary to Gray Code

Q3

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	X	X	X	X
10	1	1	X	X

B_3

$$D_3 = B_3$$

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00		1		1
01		1		1
11		X		X
10		1		X

$$D_0 = \bar{B}_1 B_0 + B_1 \bar{B}_0$$

$$D_0 = B_1 \oplus B_0$$

Q2

$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	X	X

$$D_2 = \bar{B}_3 B_2 + B_3 \bar{B}_2$$

$$D_2 = B_3 \oplus B_2$$

Q1


$B_3 B_2$ \ $B_1 B_0$	00	01	11	10
00			1	1
01	1	1		
11	X	X		
10			X	X

$$D_1 = B_2 \bar{B}_1 + \bar{B}_2 B_1$$

$$D_1 = B_2 \oplus B_1$$

* XOR gate is used to Convert the straight Binary code to gray code

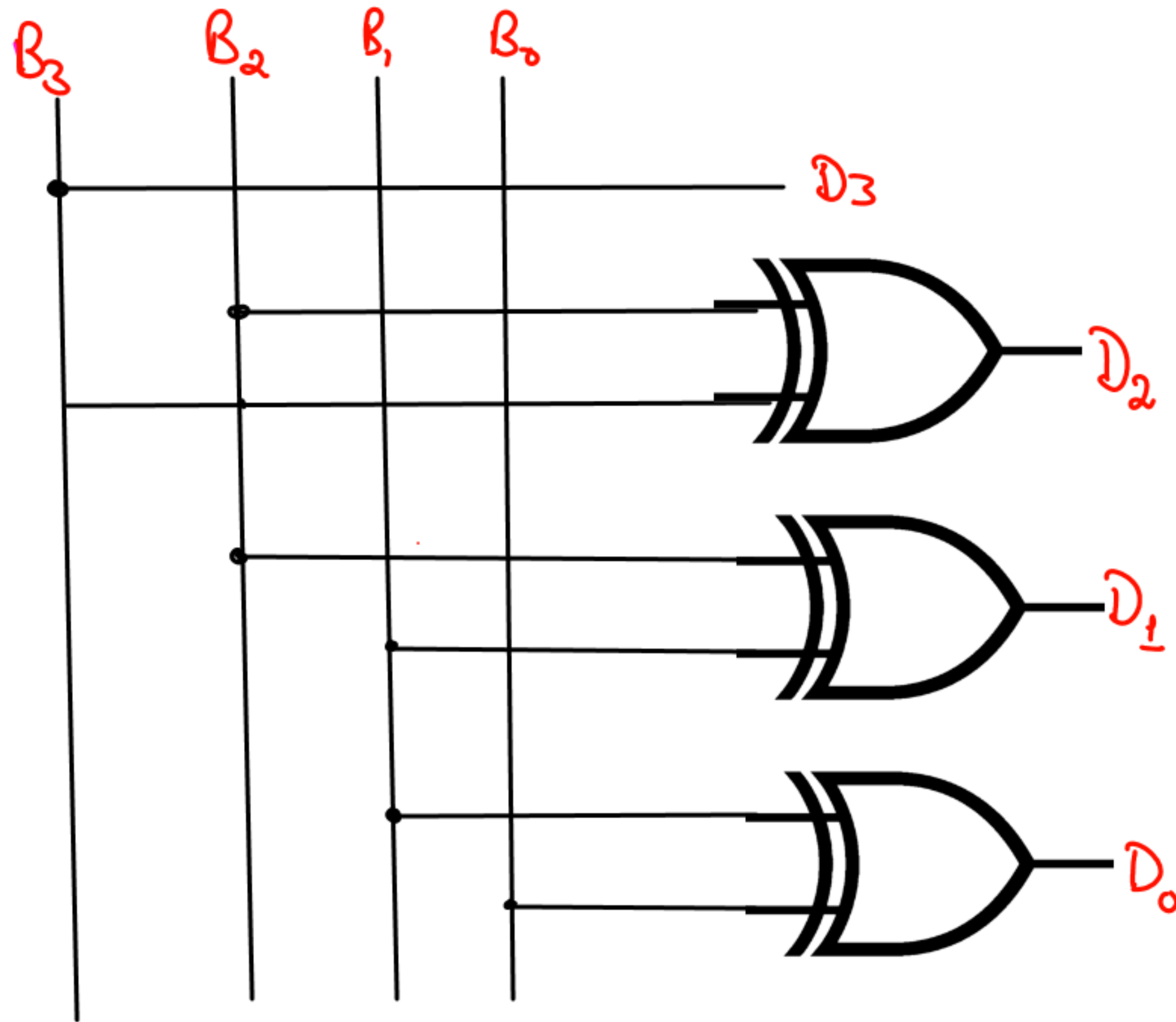Binary to Gray Code → It will also work for 4 Bit Binary to gray Code Converter
Not only BCD.



Parity Circuit

A circuit that is used to check that the number of 1's are even or odd.

--> It is used for error detection.

--> It can detect only one bit error.

Parity Generator



It accepts $n-1$ bits
and add 1 extra bit (at MSB)
Such that total number of
1's in the bit stream are even/odd

Parity Checker



Check that the data
sent by the sender is
Correct or NOT
↓
even parity / odd parity

Even Parity Generator

If number of 1's are even then Y=0 and Number of 1's are odd the Y = 1

3 Bit data

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$\rightarrow m_1$

$\rightarrow m_2$

$\rightarrow m_4$

$\rightarrow m_7$

$$f = \sum m(1, 2, 4, 7)$$

$$= A \oplus B \oplus C$$

$$f = \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$$

$$\bar{B}(\bar{A}C + A\bar{C}) + B(\bar{A}\bar{C} + AC)$$


$$\bar{B}(A \oplus C) + B(\overline{A \oplus C})$$

$$\bar{B}(\underbrace{A \oplus C}_x) + B(\underbrace{\overline{A \oplus C}}_{\bar{x}})$$

$$= \bar{B}x + B\bar{x} = B \oplus x$$

$$f = B \oplus A \oplus C$$

$$f = A \oplus B \oplus C$$

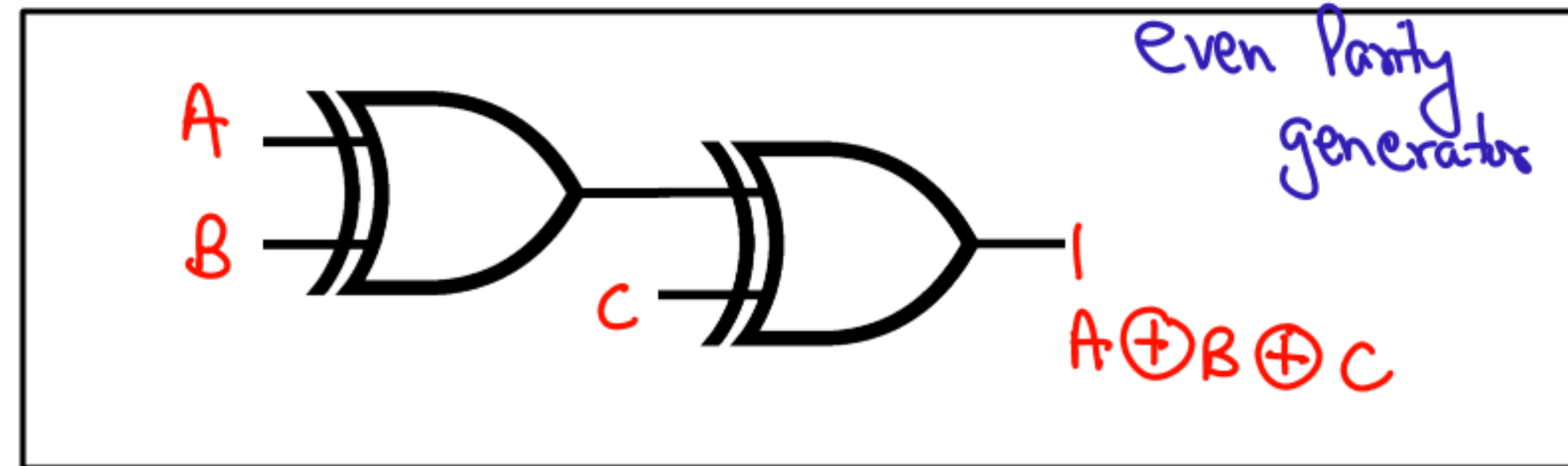


Odd Parity Generator

If number of 1's are odd then $Y=0$ and Number of 1's are even the $Y = 1$

$$f = \sum m(0, 3, 5, 6)$$

for even Parity, $A \oplus B \oplus C$ then for odd parity
the function will be $\overline{A \oplus B \oplus C}$

A	B	C	Y
0	0	0	1 $\rightarrow m_0$
0	0	1	0
0	1	0	0
0	1	1	1 $\rightarrow m_3$
1	0	0	0
1	0	1	1 $\rightarrow m_5$
1	1	0	1 $\rightarrow m_6$
1	1	1	0

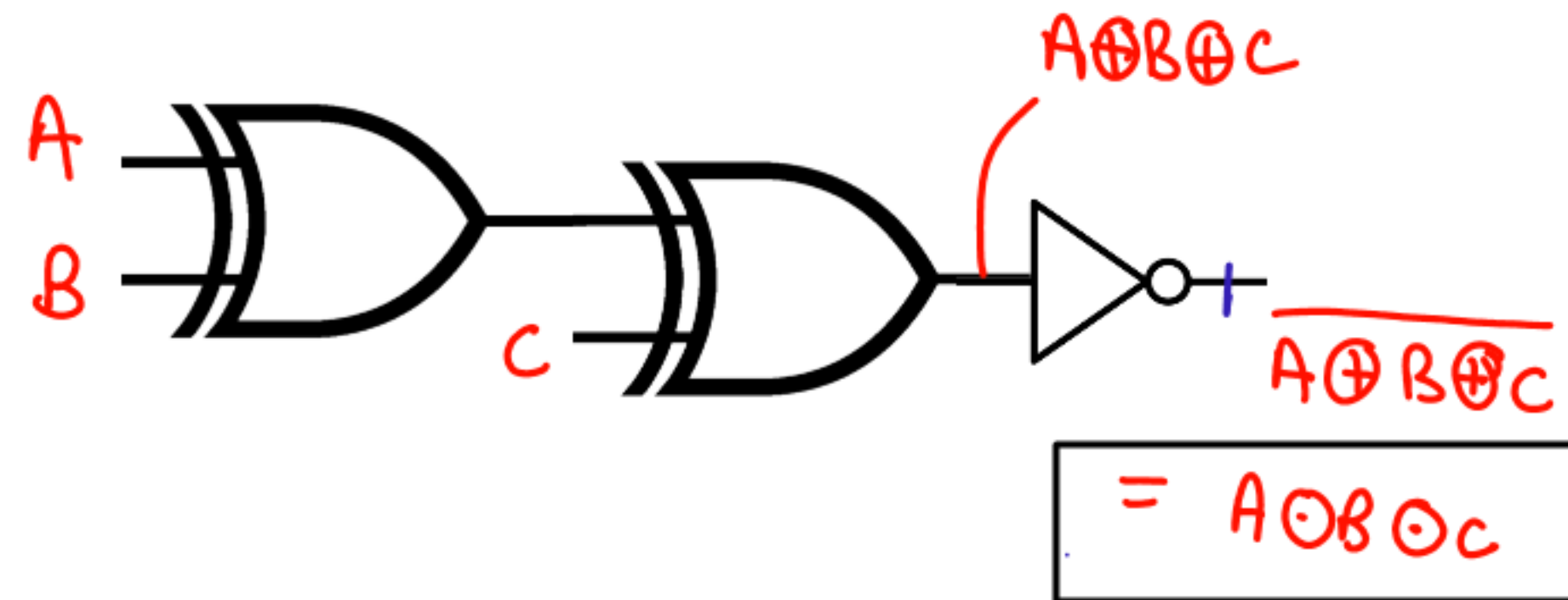

Parity Check

A B C	P _{even}	P _{odd}
0 0 0	1	0
0 0 1	0	1
0 1 0	0	1
0 1 1	1	0
1 0 0	0	1
1 0 1	1	0
1 1 0	1	0
1 1 1	0	1

$$P_{\text{even}} = \sum m(0, 3, 5, 6) \rightarrow \text{Kmap}$$

$$P_{\text{odd}} = \sum m(1, 2, 4, 7) \rightarrow \text{Kmap}$$

Take 4 Bits for Parity Check
↓
4-Variable Kmap