

MULTIPLEXERS


(PART - 03)

HALF ADDER USING 4:1 MUX

MSB A	LSB B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

2 Mux
Sum
Carry

4 input lines

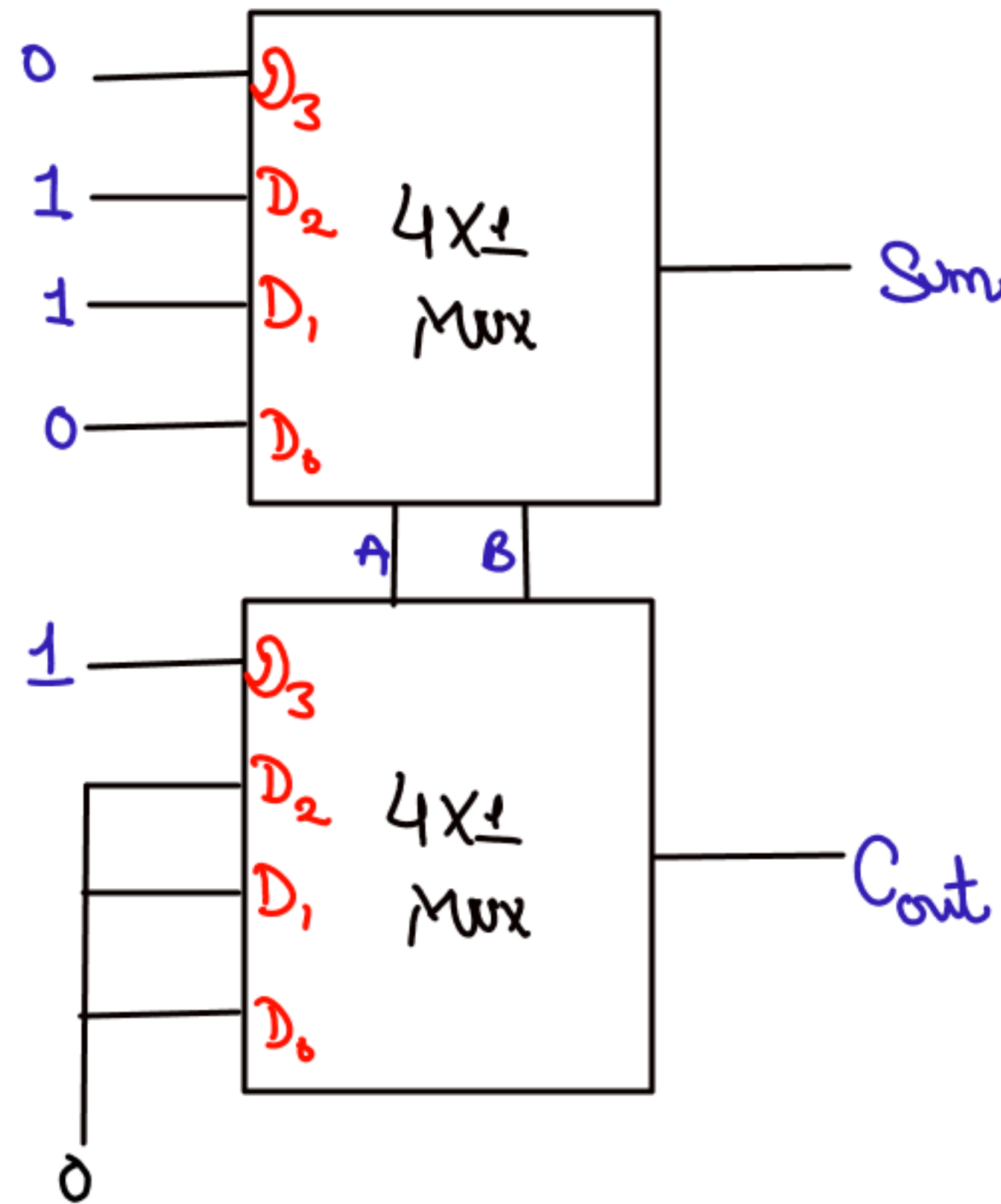

HALF ADDER USING 2:1 MUX

A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

for half Adder:


$$\text{Sum} = A \oplus B$$

$$\text{Carry} = AB$$

XOR
AND

let A be the input line & B be the select line

We can implement this Inverter using mux

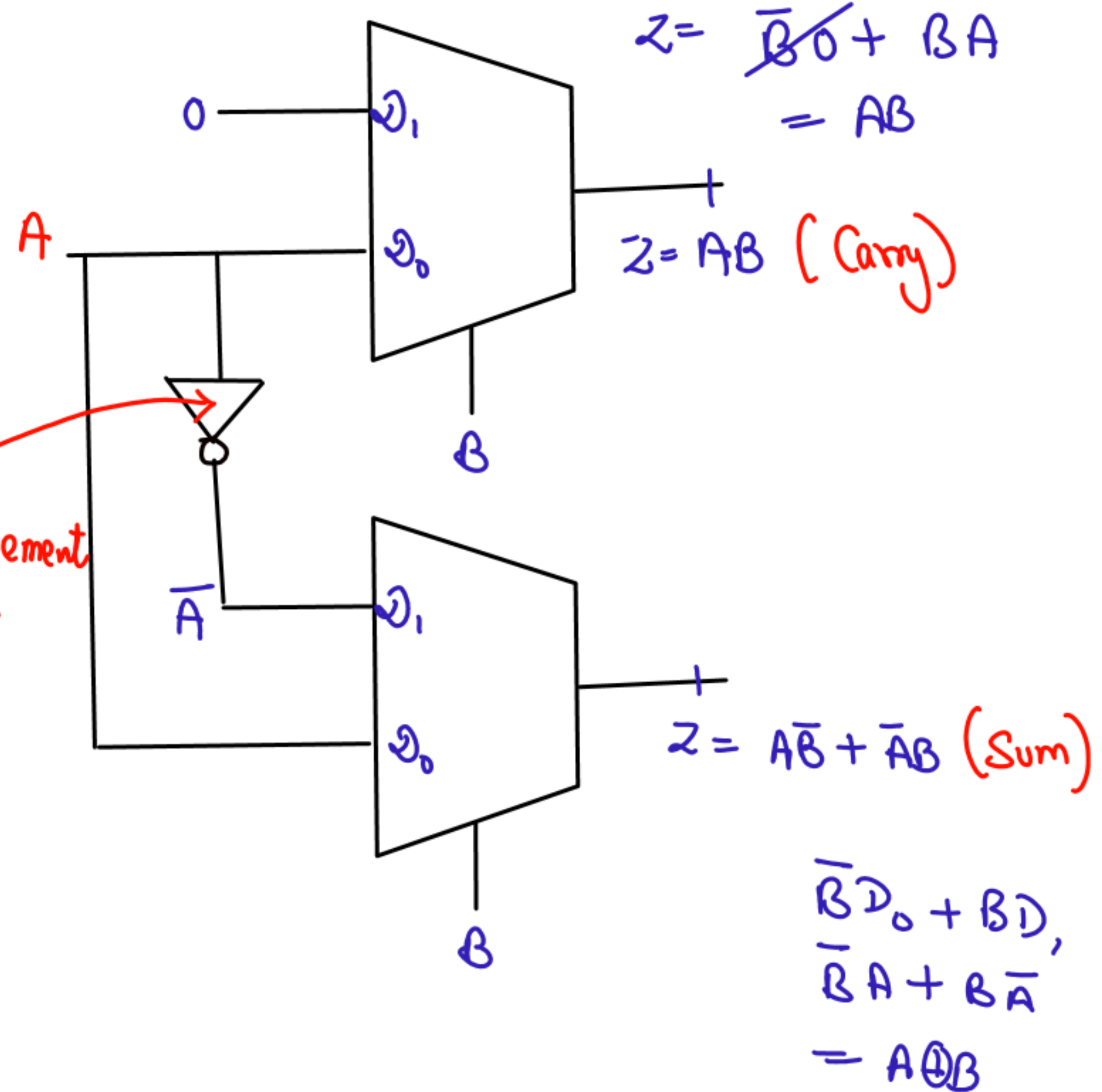


HALF SUBTRACTOR USING 2:1 MUX

A	B	Difference (D)	Borrow (B)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

for half subtractor

$$\text{Difference (D)} = A \oplus B$$

$$\text{Borrow} = \bar{A}B$$

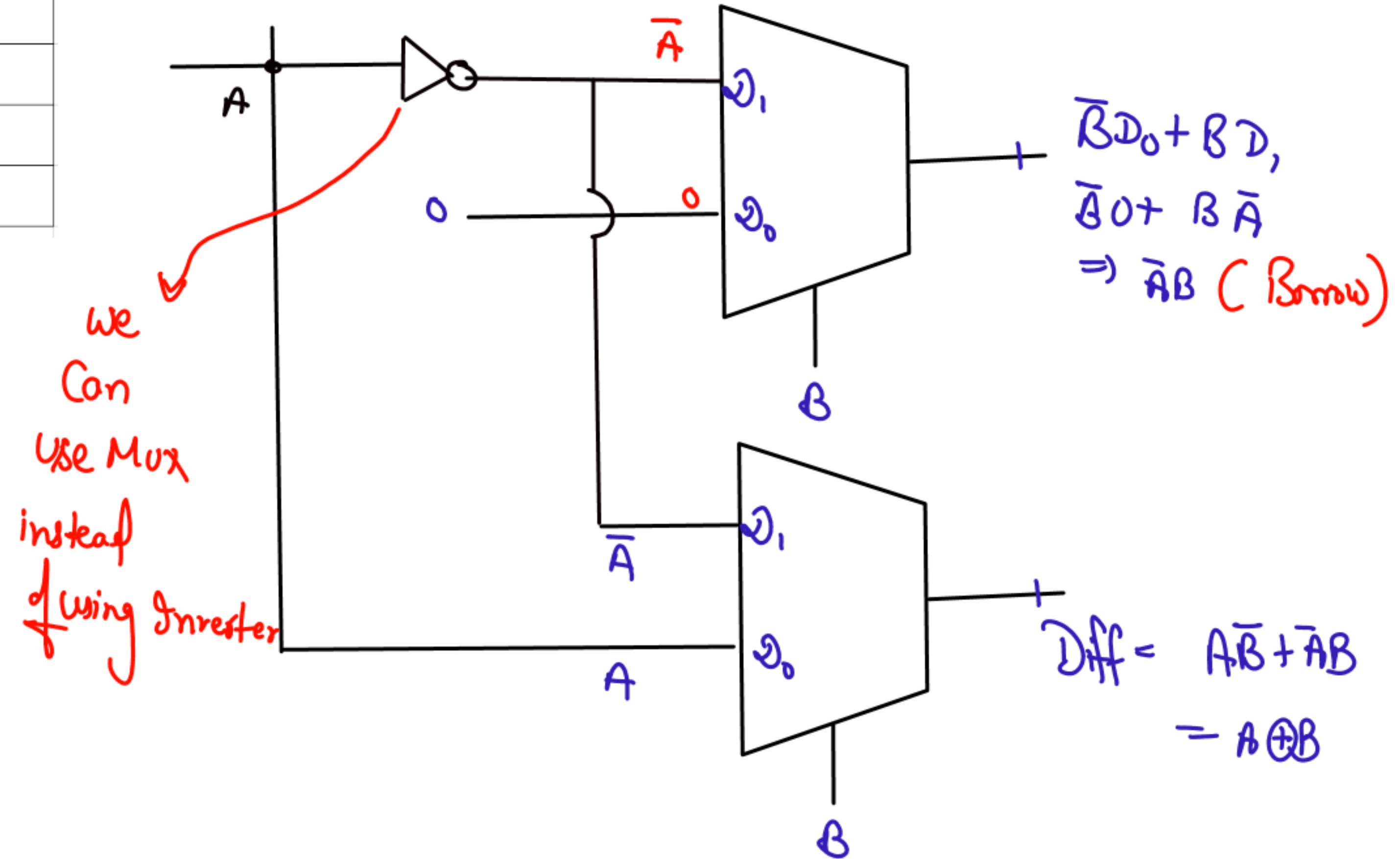

FULL ADDER USING 4:1 MUX

TRUTH TABLE					
	A	B	Cin	SUM	CARRY
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

let Input Variable = A
& BC_{in} be the select line

$$Sum = \sum m(1, 2, 4, 7)$$


$$Carry = \sum m(3, 5, 6, 7)$$

for Sum

		$BC \rightarrow$			
		00	01	10	11
\bar{A}	0	0 000	1 001	2 010	3 011
A	1	4 100	5 101	6 110	7 111
		A D_0	\bar{A} D_1	\bar{A} D_2	A D_3

for Carry

		$BC \rightarrow$			
		00	01	10	11
\bar{A}	0	0 000	1 001	2 010	3 011
A	1	4 100	5 101	6 110	7 111
		0 D_0	A D_1	A D_2	1 D_3

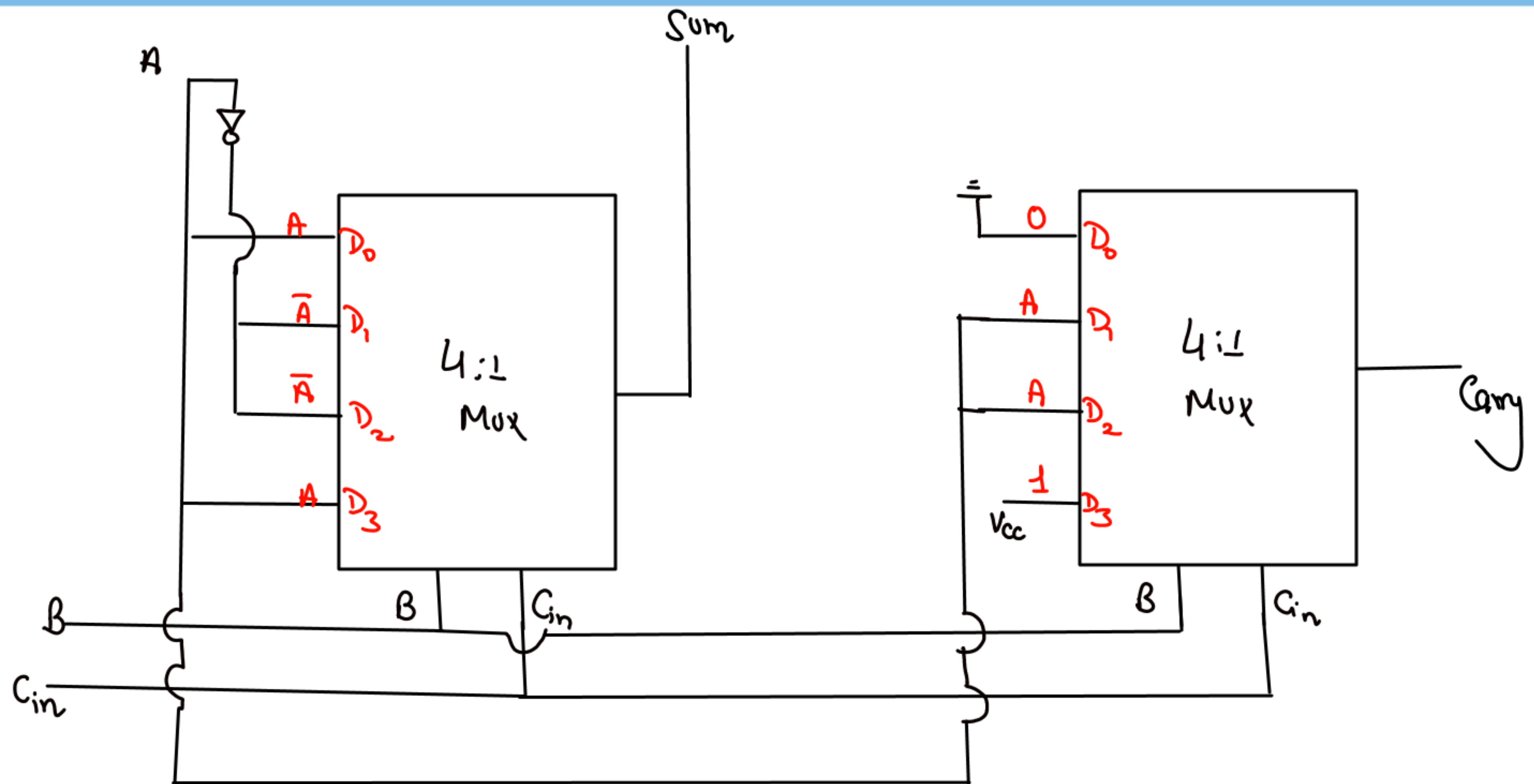


FULL SUBTRACTOR USING 4:1 MUX


TRUTH TABLE					
	A	B	Bin	Diff	Bout
0	0	0	0	0	0
1	0	0	1	1	1
2	0	1	0	1	1
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	0
6	1	1	0	0	0
7	1	1	1	1	1

Let Input Variable = A
& BC_{in} be the select line

$$\text{Sum} = \sum m(1, 2, 4, 7)$$

$$\text{Bout} = \sum m(1, 2, 3, 7)$$

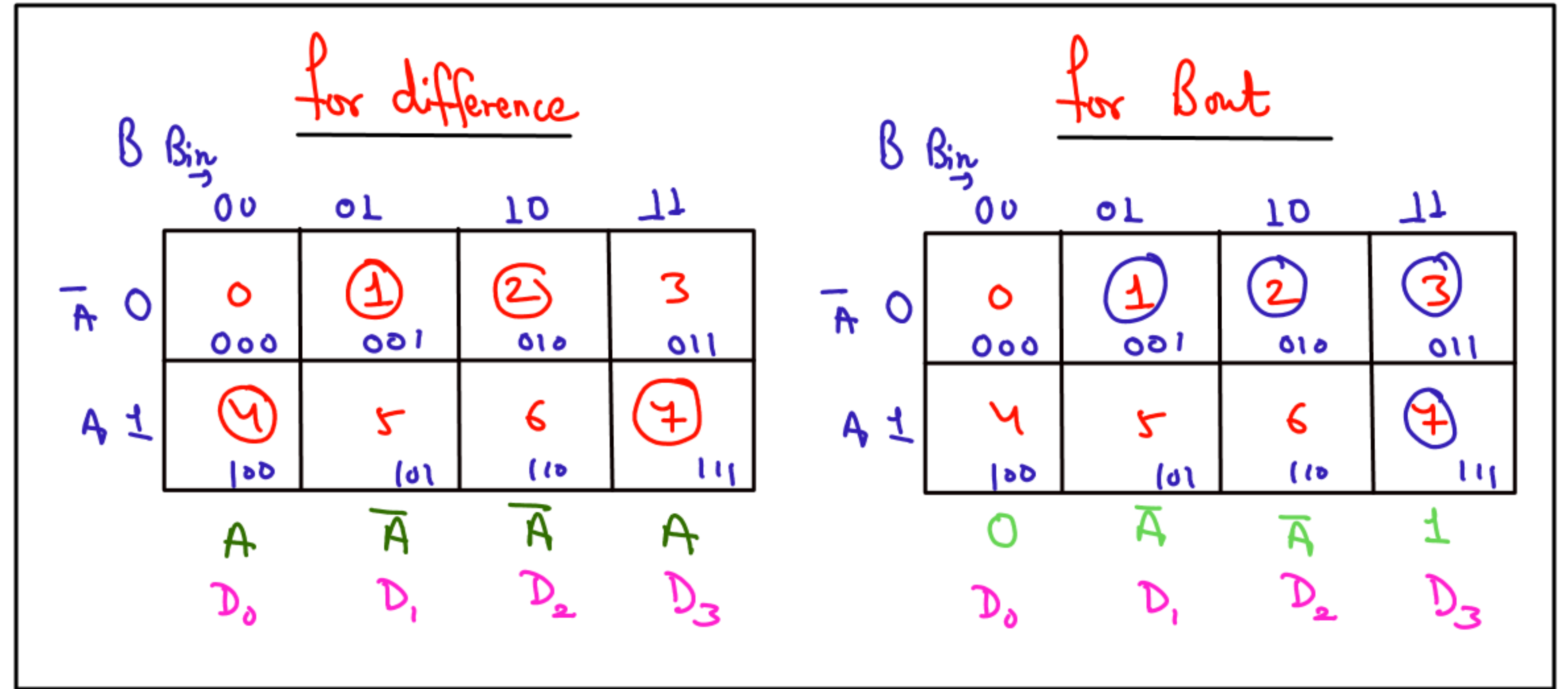

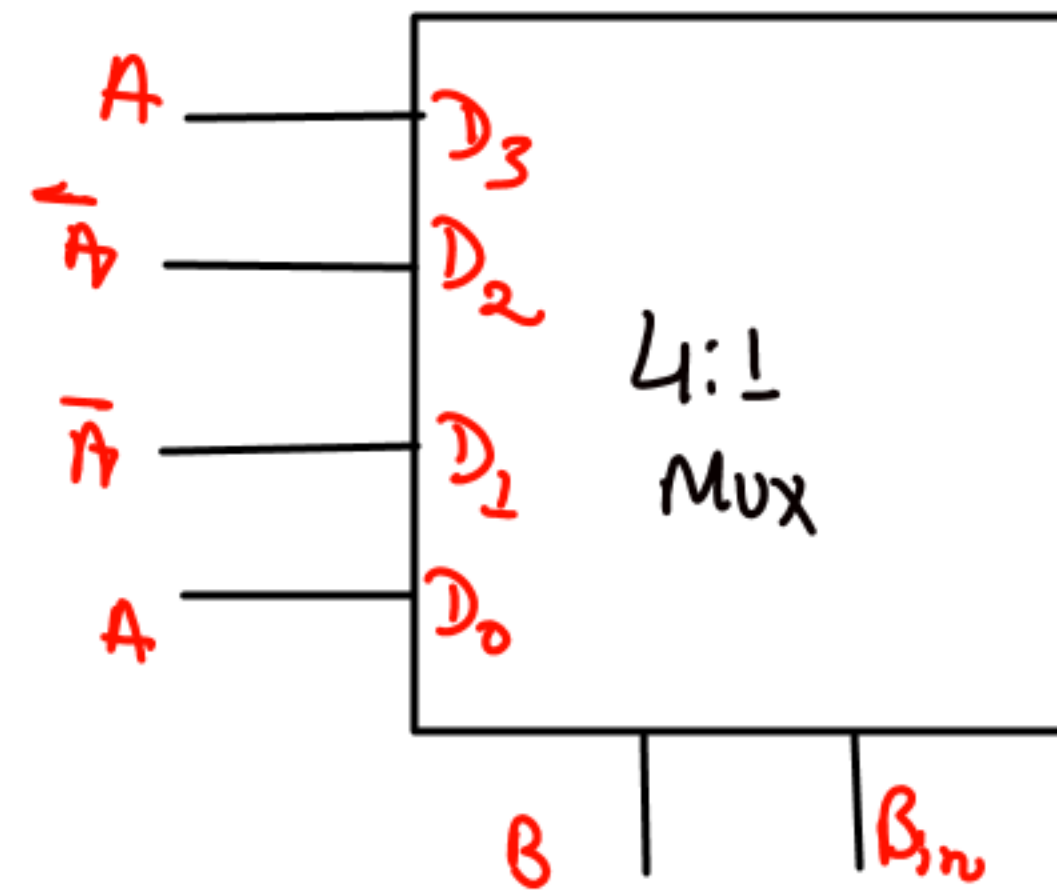

$$Z = D_0 \cdot \bar{B} \bar{B}_i + D_1 \bar{B} B_i + D_2 B \bar{B}_i + D_3 B B_i$$


$$\Rightarrow \underline{A \bar{B} \bar{B}_i} + \underline{\bar{A} \bar{B} B_i} + \underline{\bar{A} B \bar{B}_i} + \underline{A B B_i}$$

$$\Rightarrow \bar{B}_i (A \bar{B} + \bar{A} B) + B_i (\bar{A} \bar{B} + A B)$$

$$\text{Let } \underline{A \bar{B} + \bar{A} B} = x = A \oplus B \quad \downarrow \quad A \oplus B = \overline{A \oplus B}$$

$$\Rightarrow \bar{B}_i x + B_i \bar{x}$$
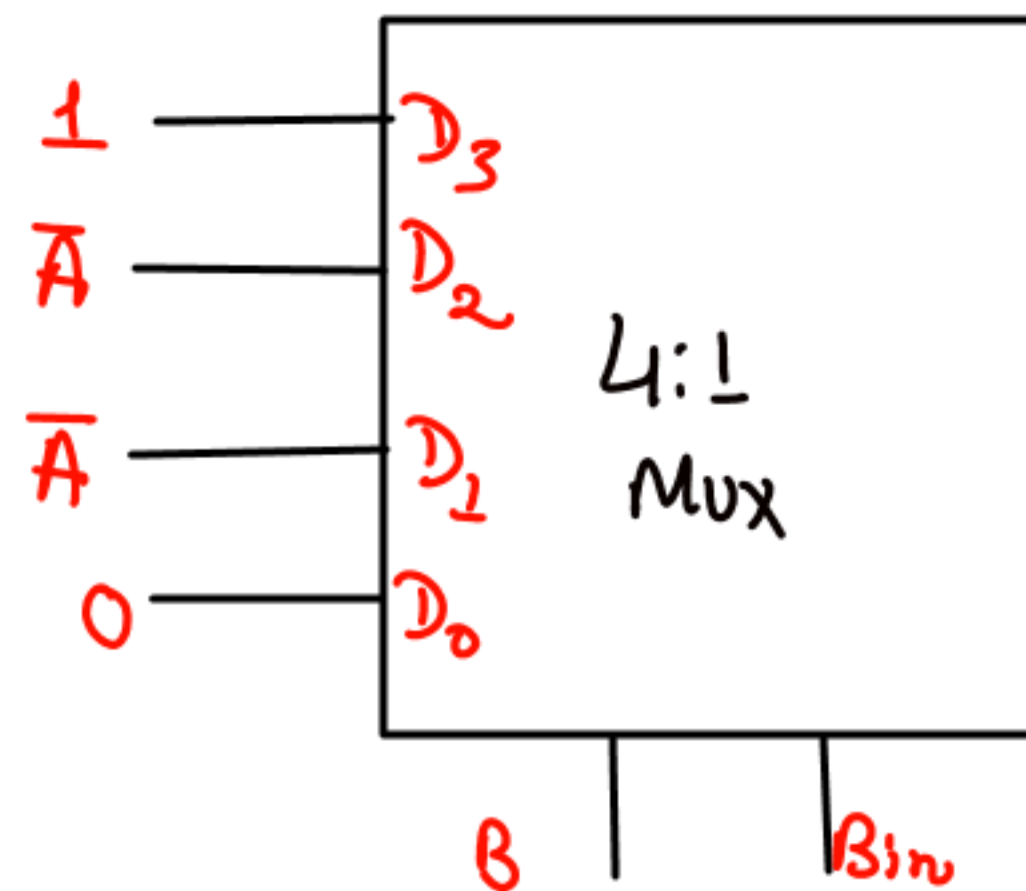
$$\Rightarrow B_i \oplus x \rightarrow \boxed{B_i \oplus A \oplus B}$$



$$Z = D_0 \cdot \bar{B} \bar{B}_i + D_1 \bar{B} B_i + D_2 B \bar{B}_i + D_3 B B_i$$

$$\cancel{0 \cdot \bar{B} \bar{B}_i} + \bar{A} \bar{B} B_i + \bar{A} B \bar{B}_i + 1 B B_i$$


$$\bar{A} \bar{B} B_i + \bar{A} B \bar{B}_i + B \cdot B_i$$

$$\bar{A} (\bar{B} B_i + B \bar{B}_i) + B \cdot B_i$$

$$\boxed{\bar{A} (B \oplus B_i) + B \cdot B_i}$$

IMPLEMENTATION OF HIGH ORDER MUX TO LOWER ORDER MUX





4 : 1 MUX using 2 : 1 MUX

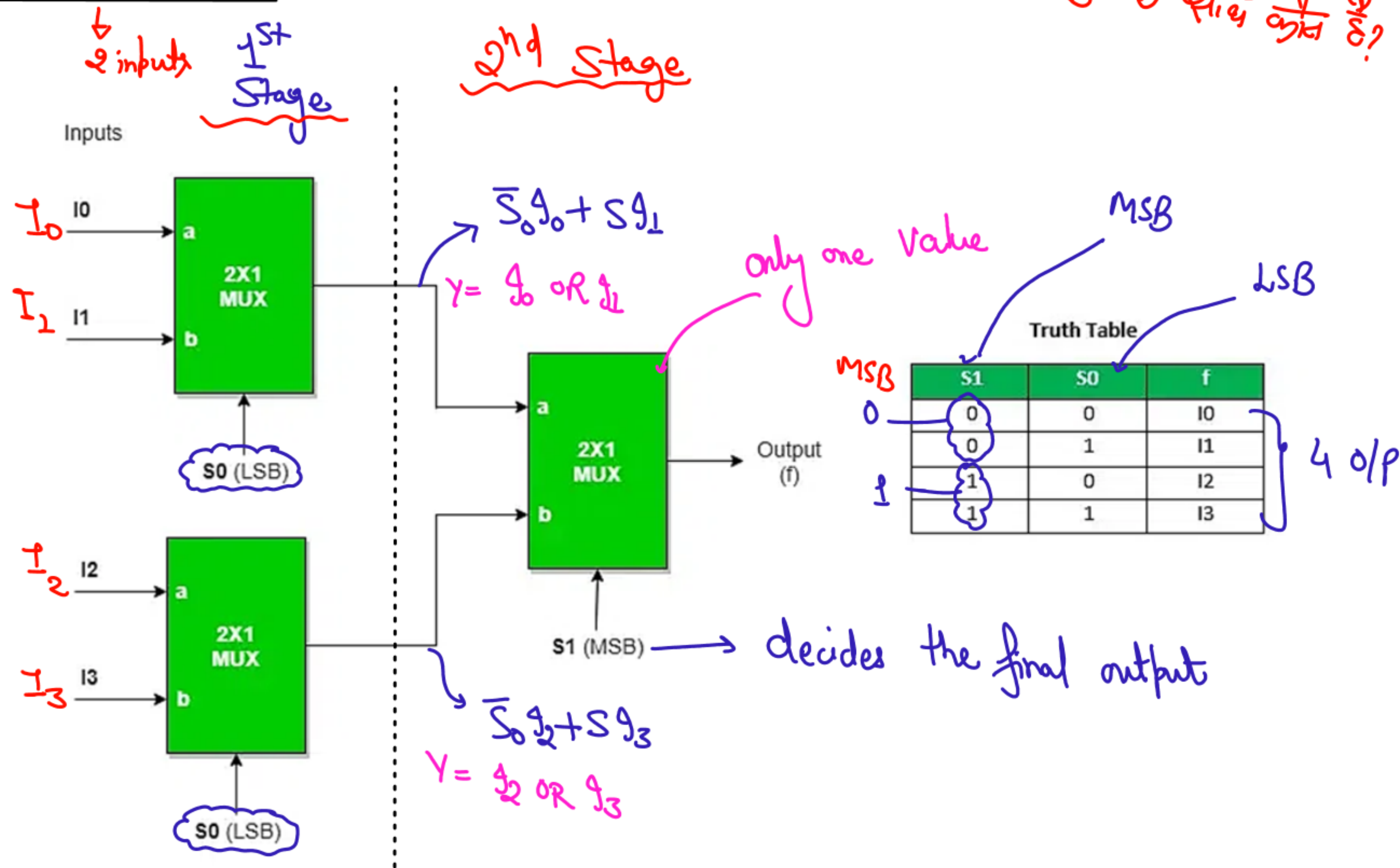

IMPLEMENTATION OF HIGH ORDER MUX TO LOWER ORDER MUX

16 : 1 MUX using 4 : 1 MUX

1st Stage

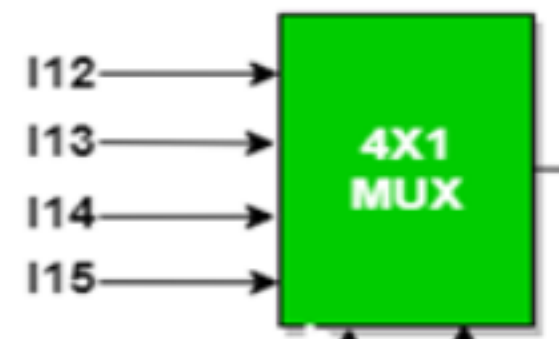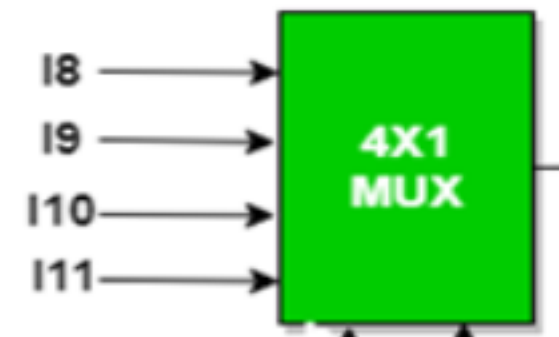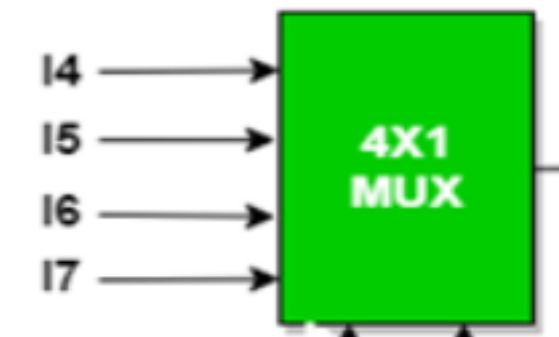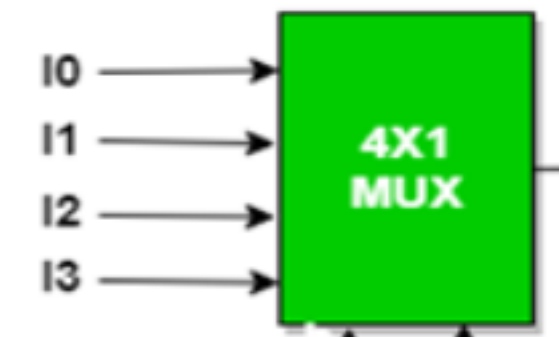

S1 S0

2nd Stage

lower Significance

$$f(s_3 s_2 s_1 s_0) = \sum m(\dots)$$

2nd Stage (MSB)

1st Stage (LSB)




Output (f)

S3 S2

MSB

General formula to implement B:1 mux from A:1 Mux

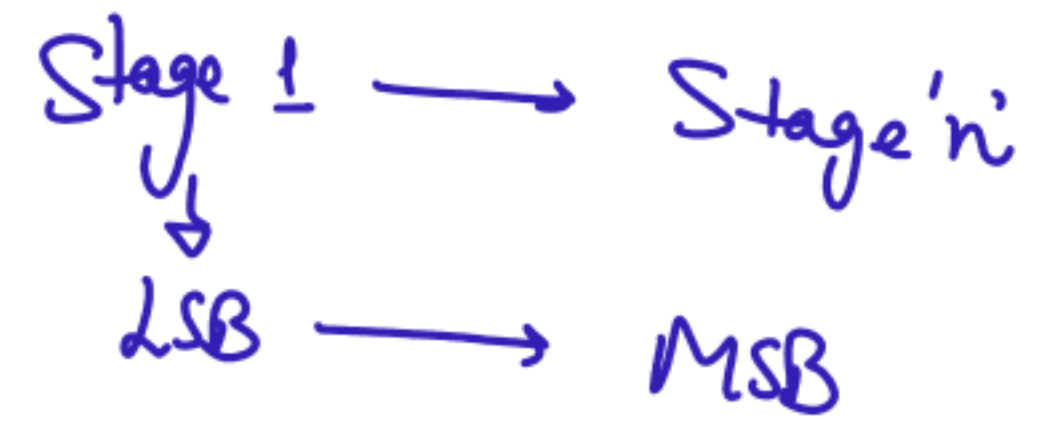for implementing B:1 mux using A:1 Mux
we have to follow the following sequence



$$B/A = K_1 \text{ (K}_1 \text{ are the number of Mux at first stage)}$$

$$K_1/A = K_2 \text{ (No of mux at 2nd stage)}$$

$$K_2/A = K_3 \text{ (3rd stage)}$$

\vdots

$$\frac{K_{n-1}}{A} = K_n = 1 \text{ (till we get 1)}$$

$$\text{Total Mux Required} = K_1 + K_2 + K_3 + \dots + K_n \Rightarrow \sum_{K=1}^n K_i$$

\downarrow
[set less significant
bits as select line]

$$\text{If } \frac{K_{n-1}}{A} = K_n \neq 0$$


Q. design 16:1 mux using 8:1 mux
 $B:1$ $A:1$

$$B/A \Rightarrow \frac{16}{8} = 2 \text{ (first stage = 2 mux)}$$

$2/8 = ?$ take 2:1 mux at 2nd stage

let

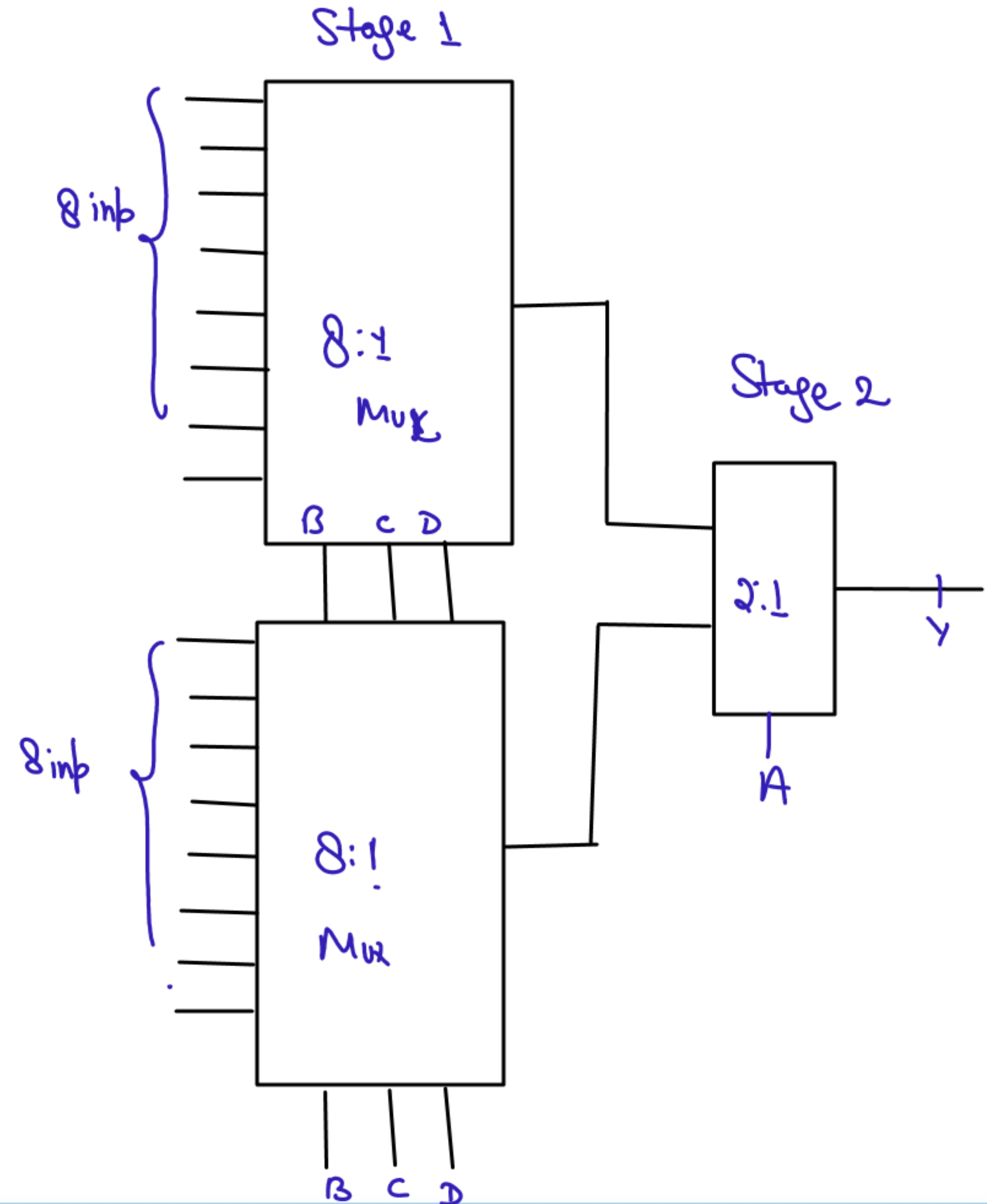Select lines be (A, B, C, D)
 $\underbrace{\hspace{1cm}}_{\text{MSB}} \quad \underbrace{\hspace{1cm}}_{\text{LSB}}$



IMPLEMENTATION OF HIGH ORDER MUX TO LOWER ORDER MUX

How many 4:1 mux are required to implement a 64:1 mux?

A:1

B:1

$$64/4 = 16 \text{ (Stage 1)}$$

$$16/4 = 4 \text{ (Stage 2)}$$

$$4/4 = 1 \text{ (Stage 3)}$$

$$\begin{aligned} \text{Total Mux required} \\ &= 16 + 4 + 1 \\ &= 21 \text{ mux} \end{aligned}$$