

Lecture - 16




Universal Gate &

Switch Representation of Logical functions

UNIVERSAL GATES




- A universal gate is a gate, which can implement any Boolean function without need to use any other gate.
- ✓ - The NAND and NOR are universal gates.
- These gates are economical and easier to fabricate, and are the basic gates used in all Integrated Circuit (IC).
- In fact, an AND gate is typically implemented as a NAND gate + inverter.
- Likewise, an OR gate is typically implemented as NOR gate + inverter.
- The circuit which is designed by universal gates, are also called as Universal logic circuit.

NAND is a Universal Gate

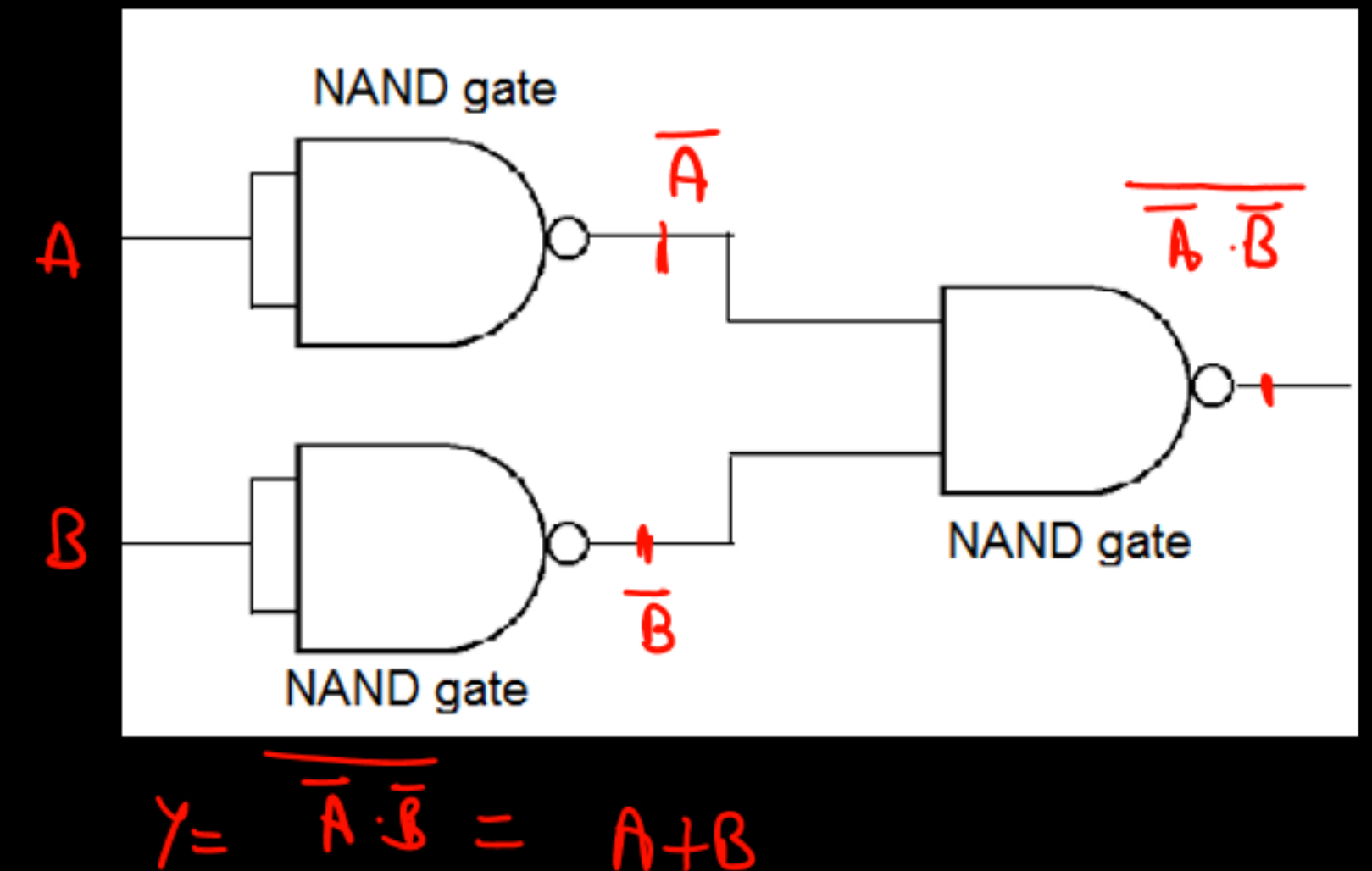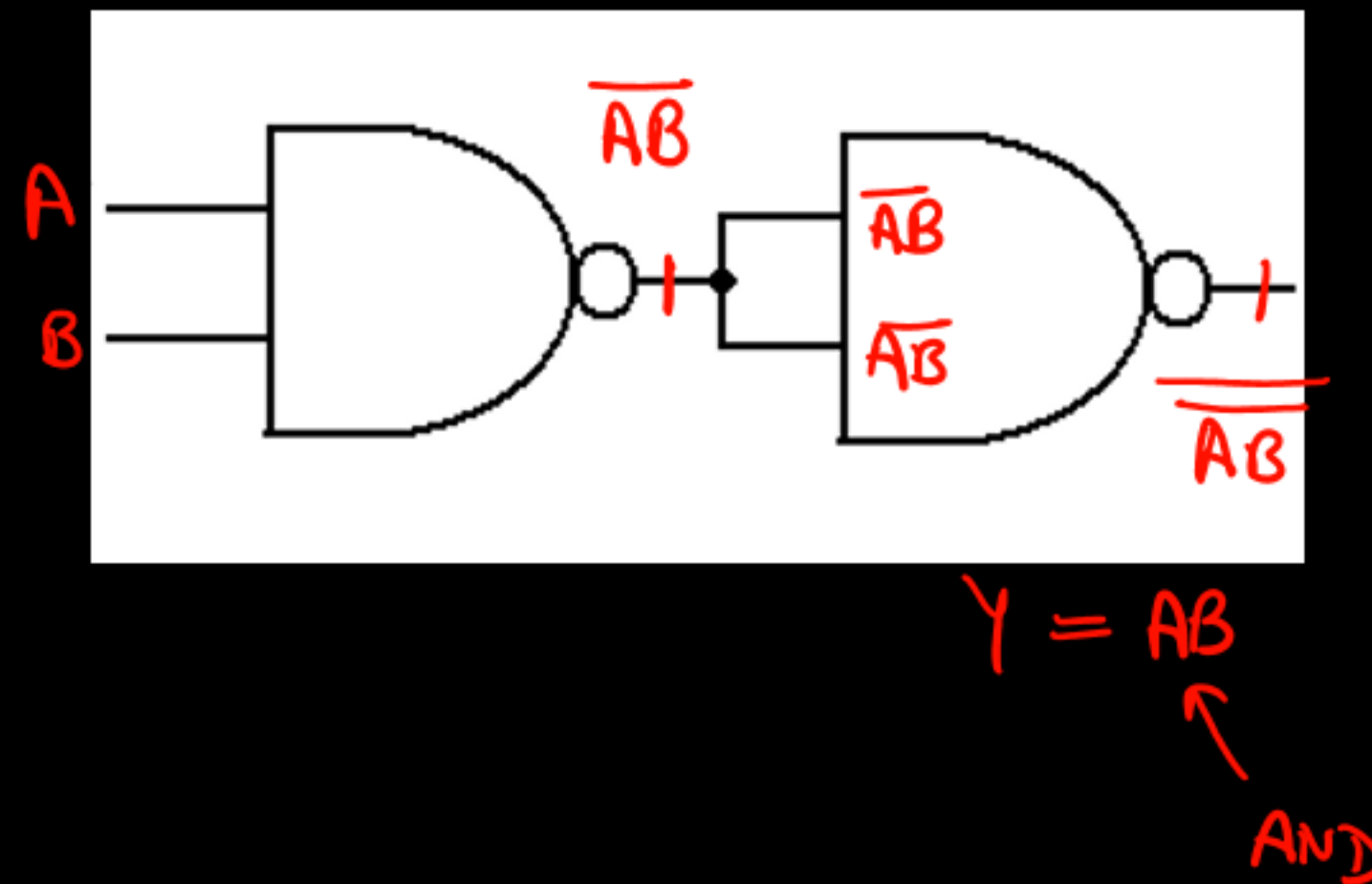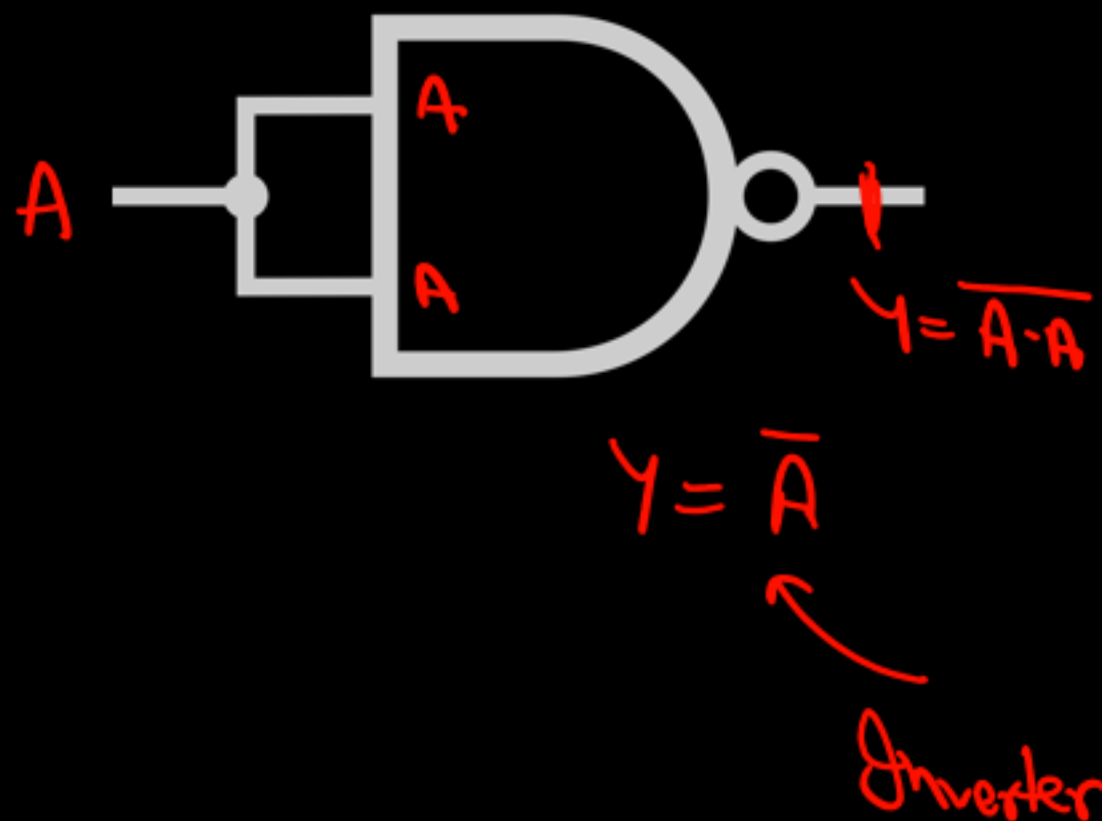


UNIVERSAL GATES

NAND is a Universal Gate

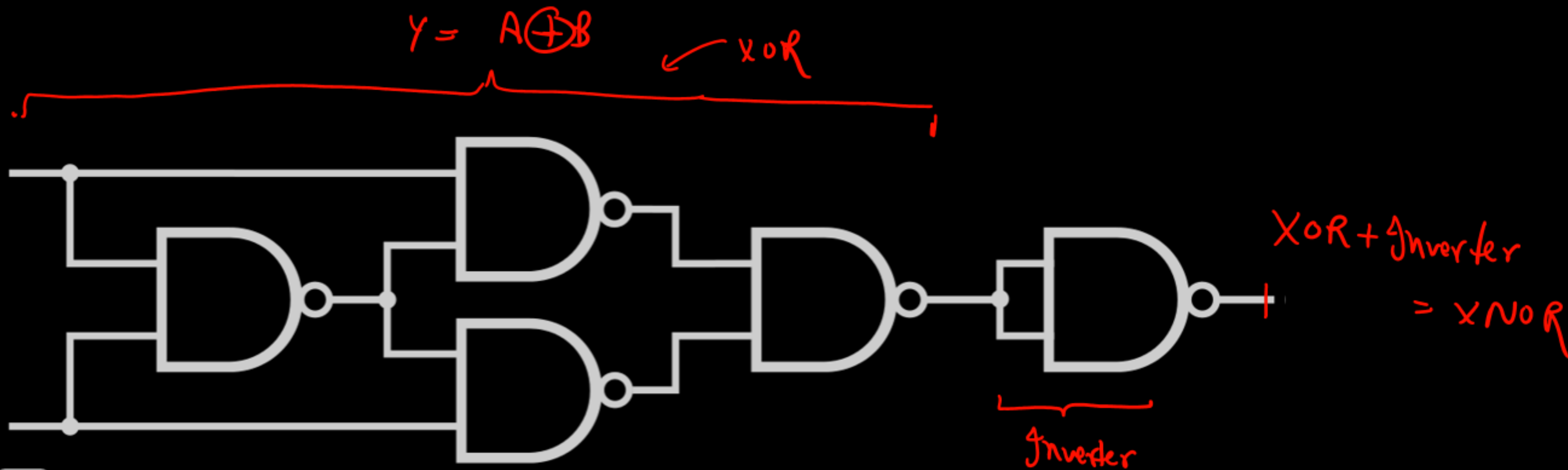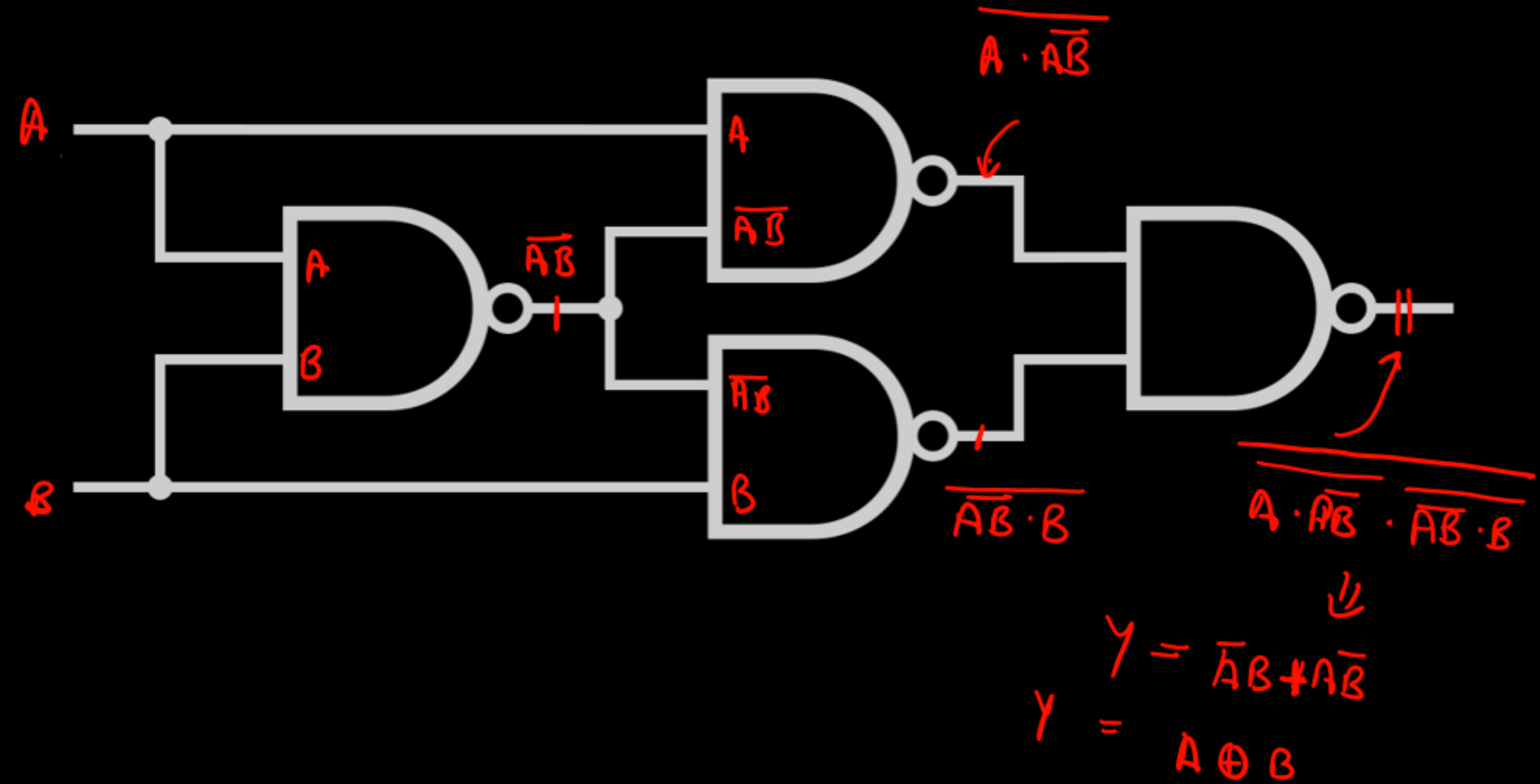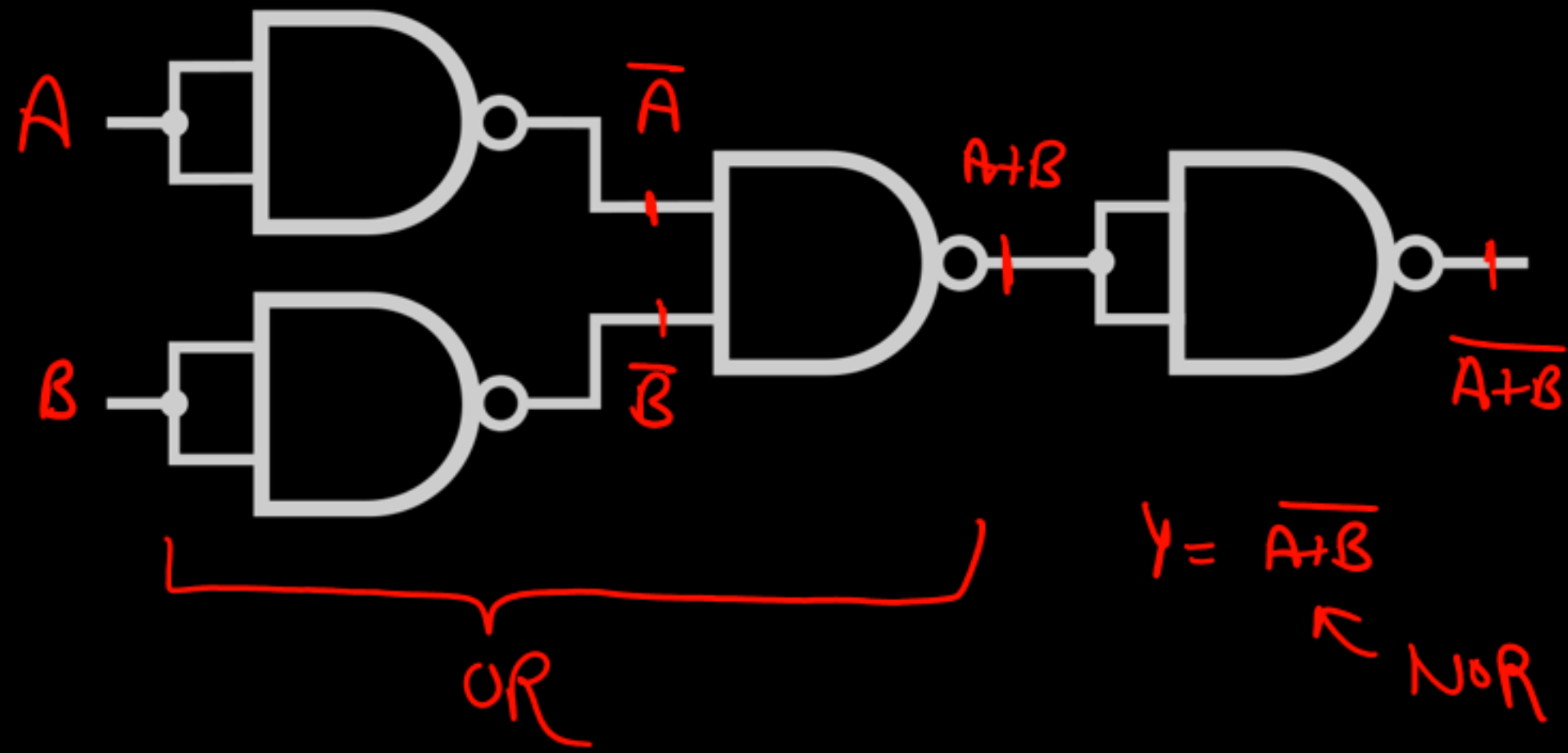

NOR is a Universal Gate ✓

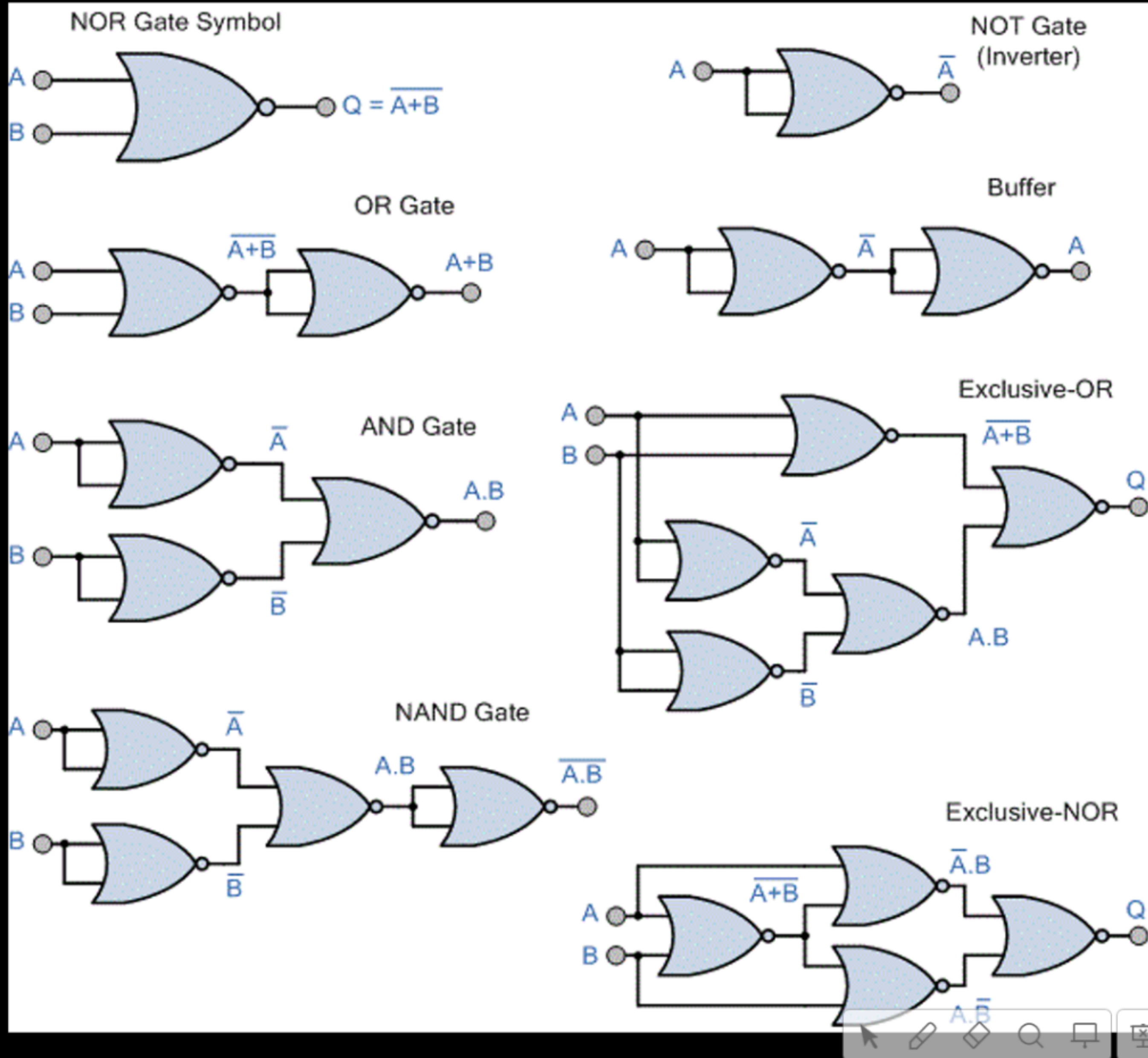

✓ Number of Universal gates required


Gate	NAND	NOR
NOT	1	1
AND	<u>2</u>	<u>3</u>
OR	<u>3</u>	<u>2</u>
NAND	<u>1</u>	<u>4</u> ✓
NOR	<u>4</u>	<u>1</u>
XOR	<u>4</u>	<u>5</u>
XNOR	<u>5</u>	<u>4</u>

Switch representation of logical function

→ Circuit + switches

a) Buffer


$$Y = A$$

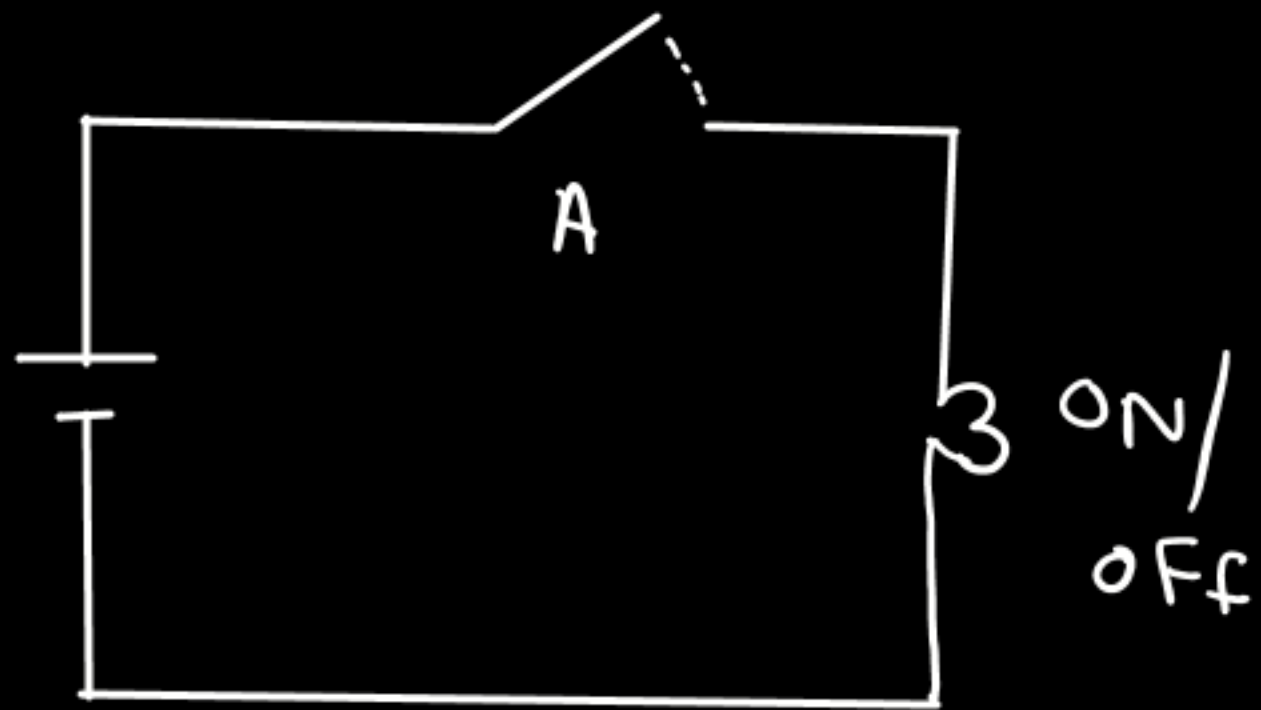

A = OFF Bulb = OFF

A = ON Bulb = ON

b) Inverter $Y = \overline{A}$

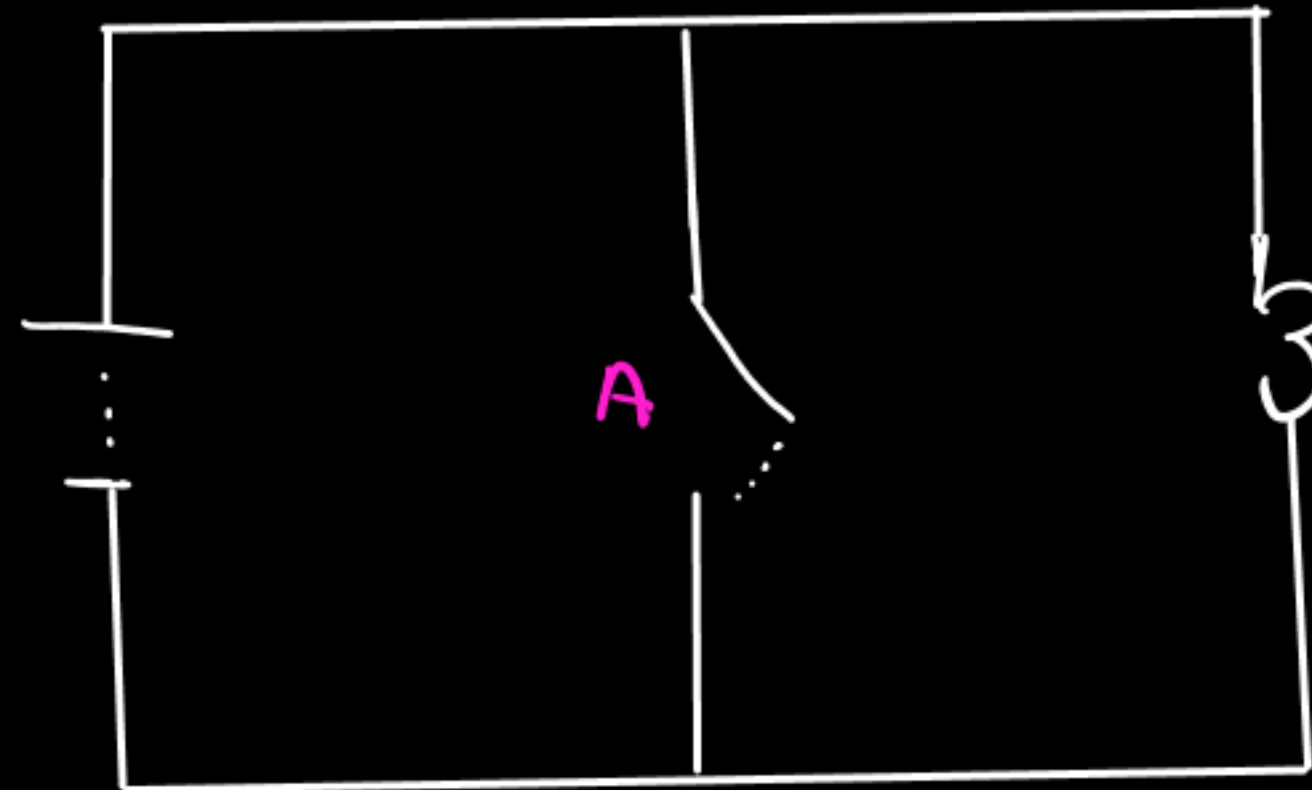


A = ON

Bulb = OFF

A = OFF

Bulb = ON

c) AND

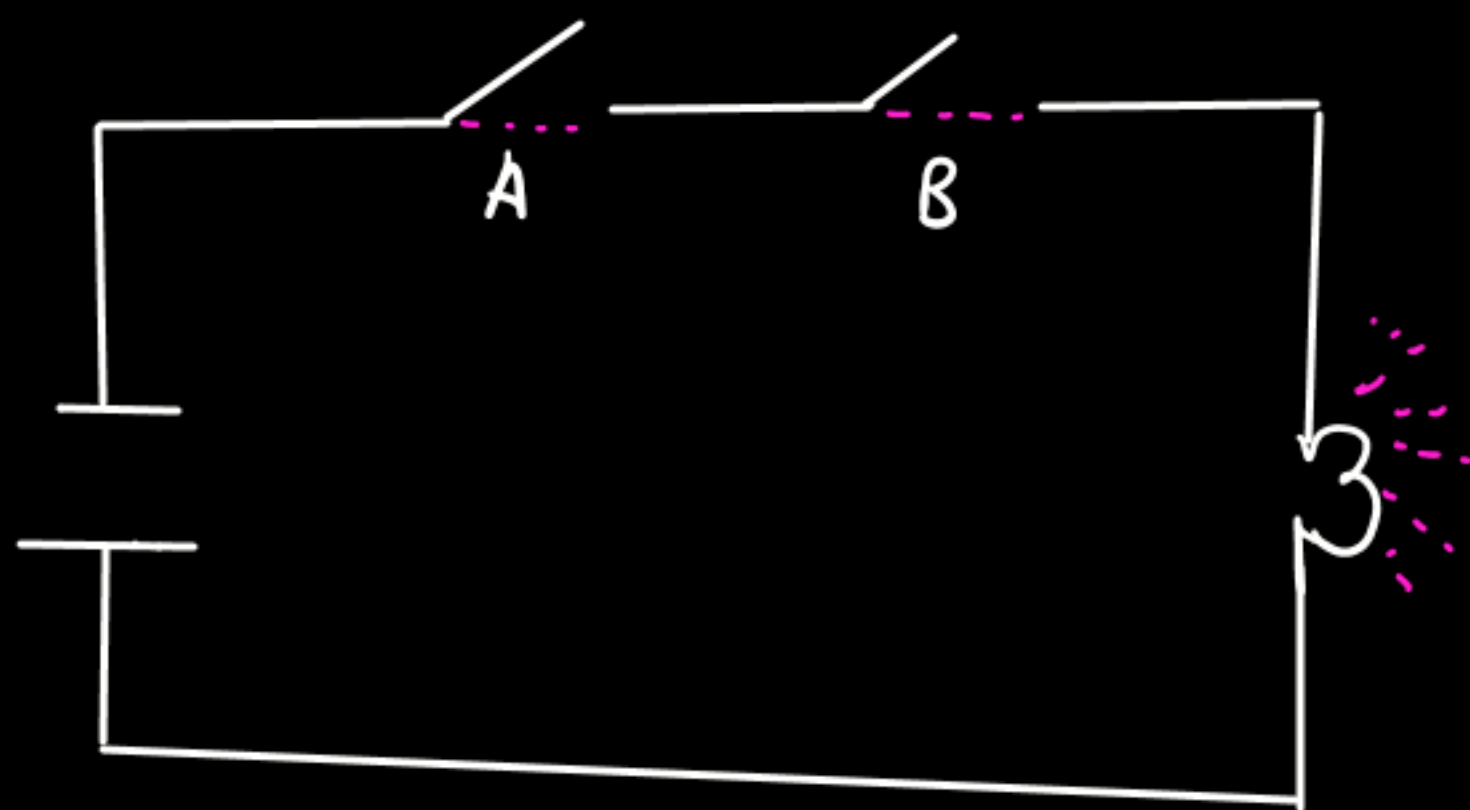


A = ON Bulb = OFF

B = ON & A = OFF \Rightarrow Bulb = OFF

A & B = ON \Rightarrow Bulb = ON

d) OR

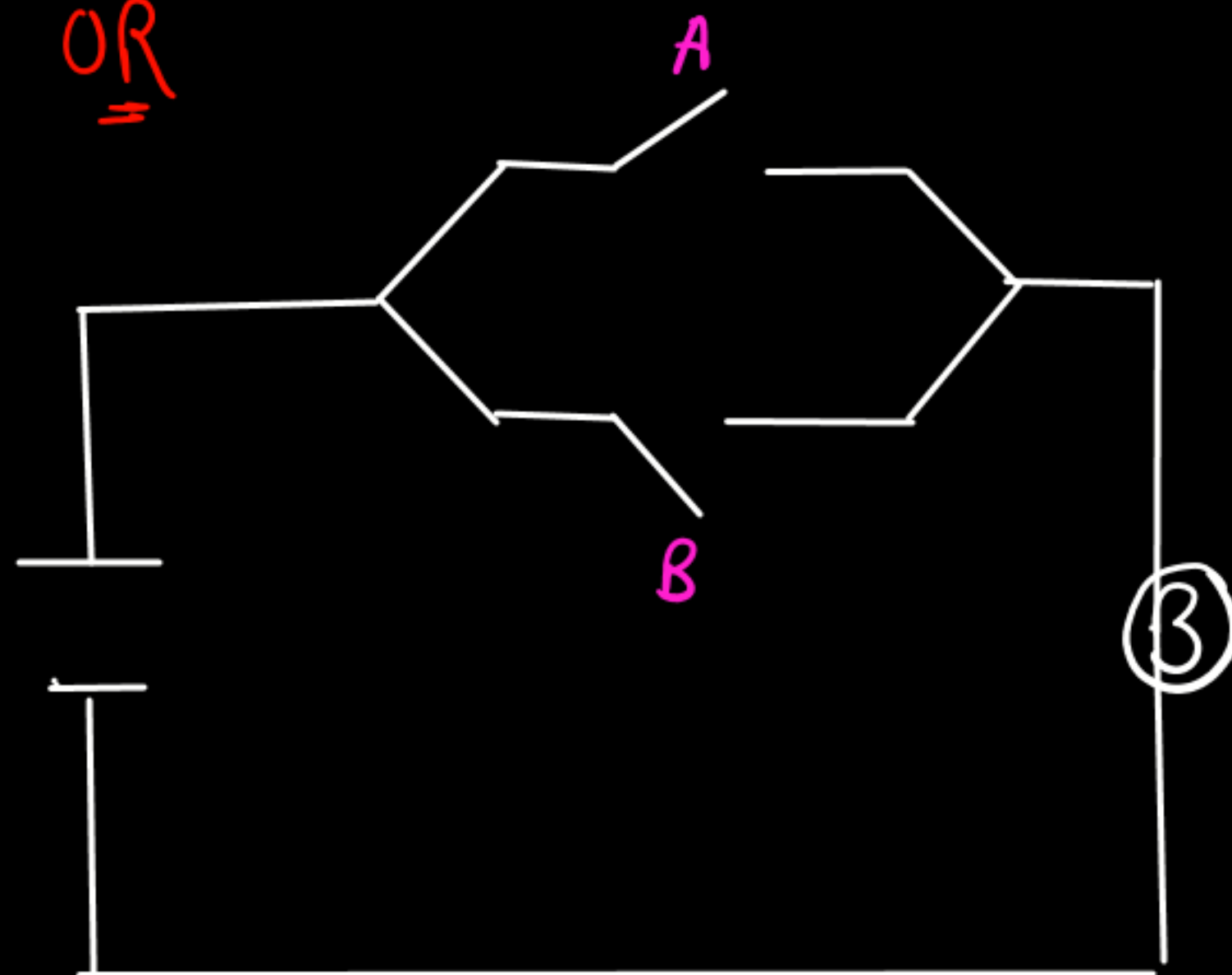


A = ON Bulb = ON

B = ON Bulb = ON

A, B = ON Bulb = ON

A, B = OFF Bulb = OFF

e) NAND Gate:

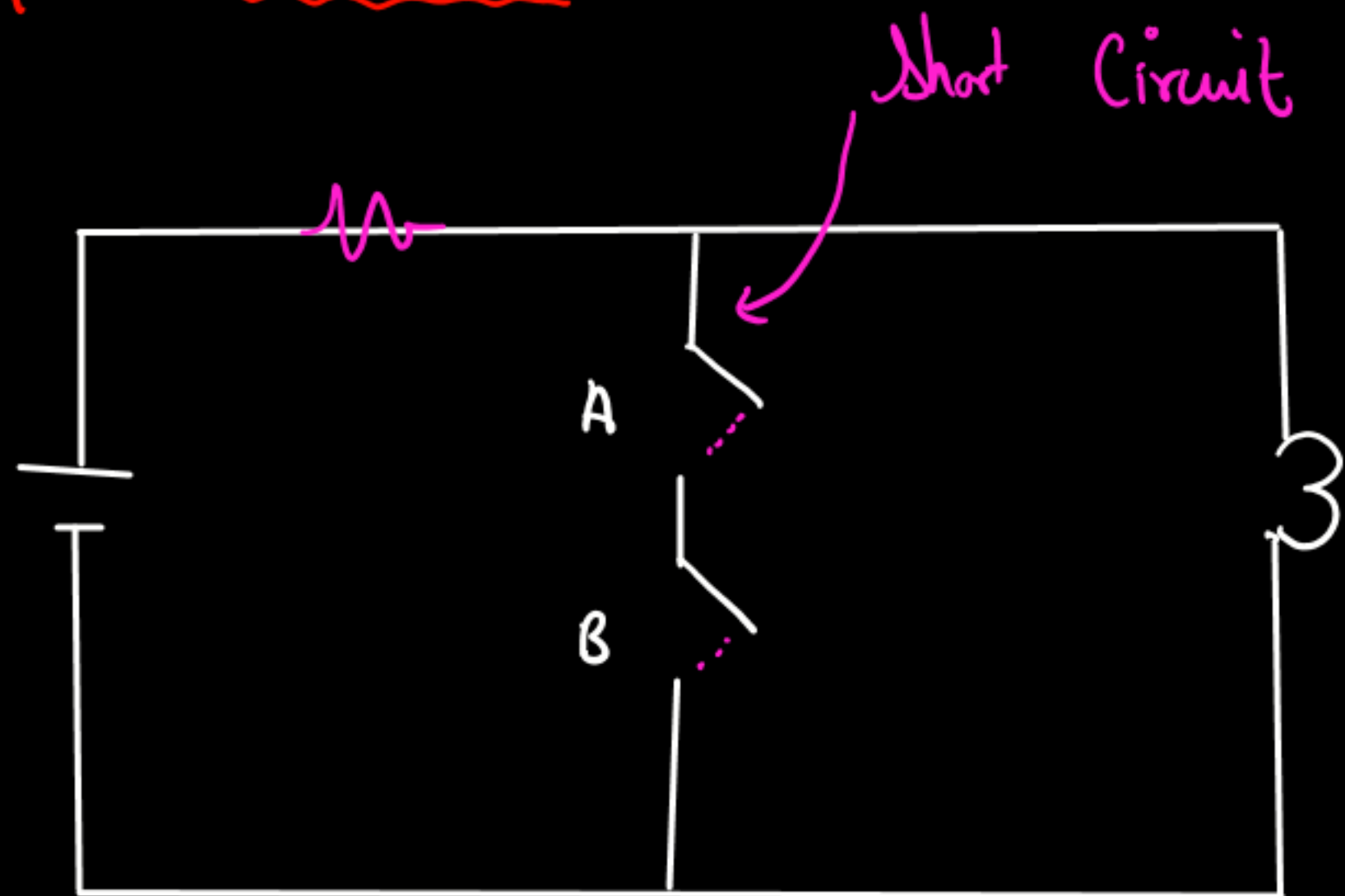


$A = \text{ON}$
 $B = \text{ON}$ } Bulb = off

ON = 1
 OFF = 0

$$Y = \overline{AB}$$

A	B	AB	\overline{AB}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

f) NOR Gate

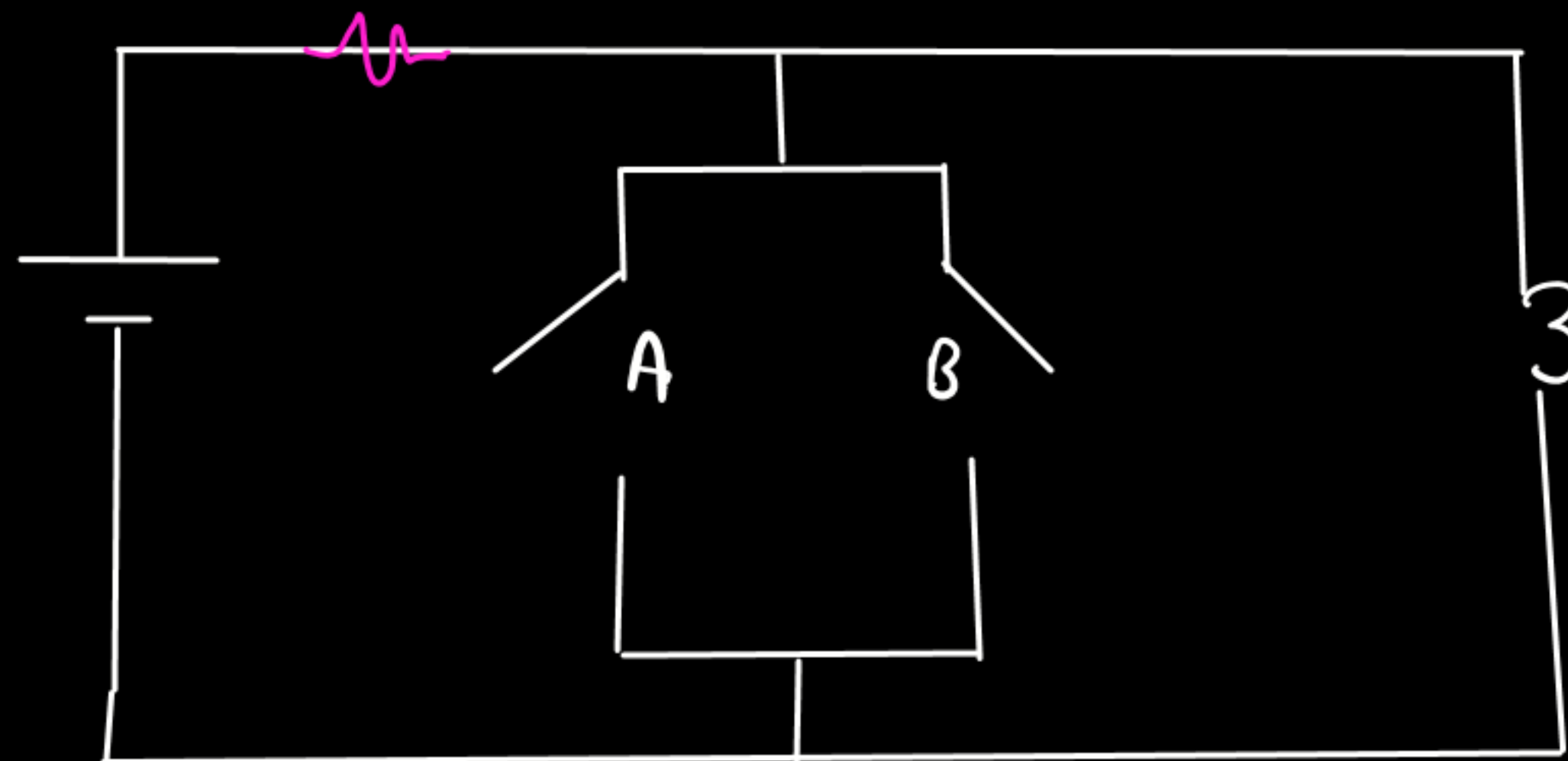

$A = \text{ON}$, Bulb = OFF

$B = \text{ON}$, Bulb = OFF

$A, B = \text{OFF} = \text{Bulb} = \text{ON}$

$$Y = \overline{A+B}$$


ON = 1
 OFF = 0

A	B	A+B	$\overline{A+B}$
0	0	0	1 — High
0	1	1	0
1	0	1	0
1	1	1	0

low ←

low


⑨ XOR \Rightarrow Inequality detector

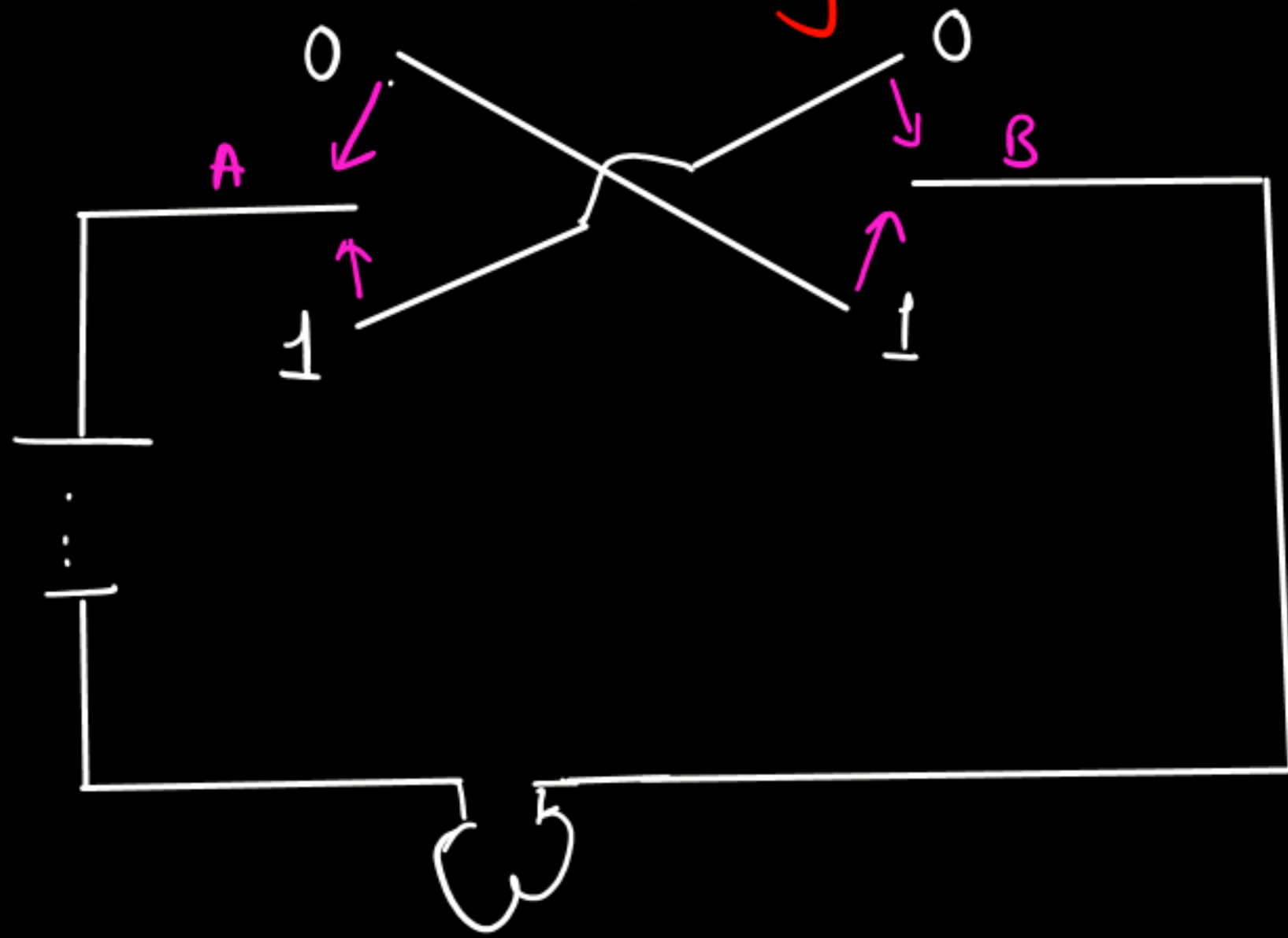

$A=0, B=1 \Rightarrow \text{Bulb} = \text{ON}$

$A=1, B=0 \Rightarrow \text{Bulb} = \text{ON}$

⑩ XNOR \rightarrow Equality Detector

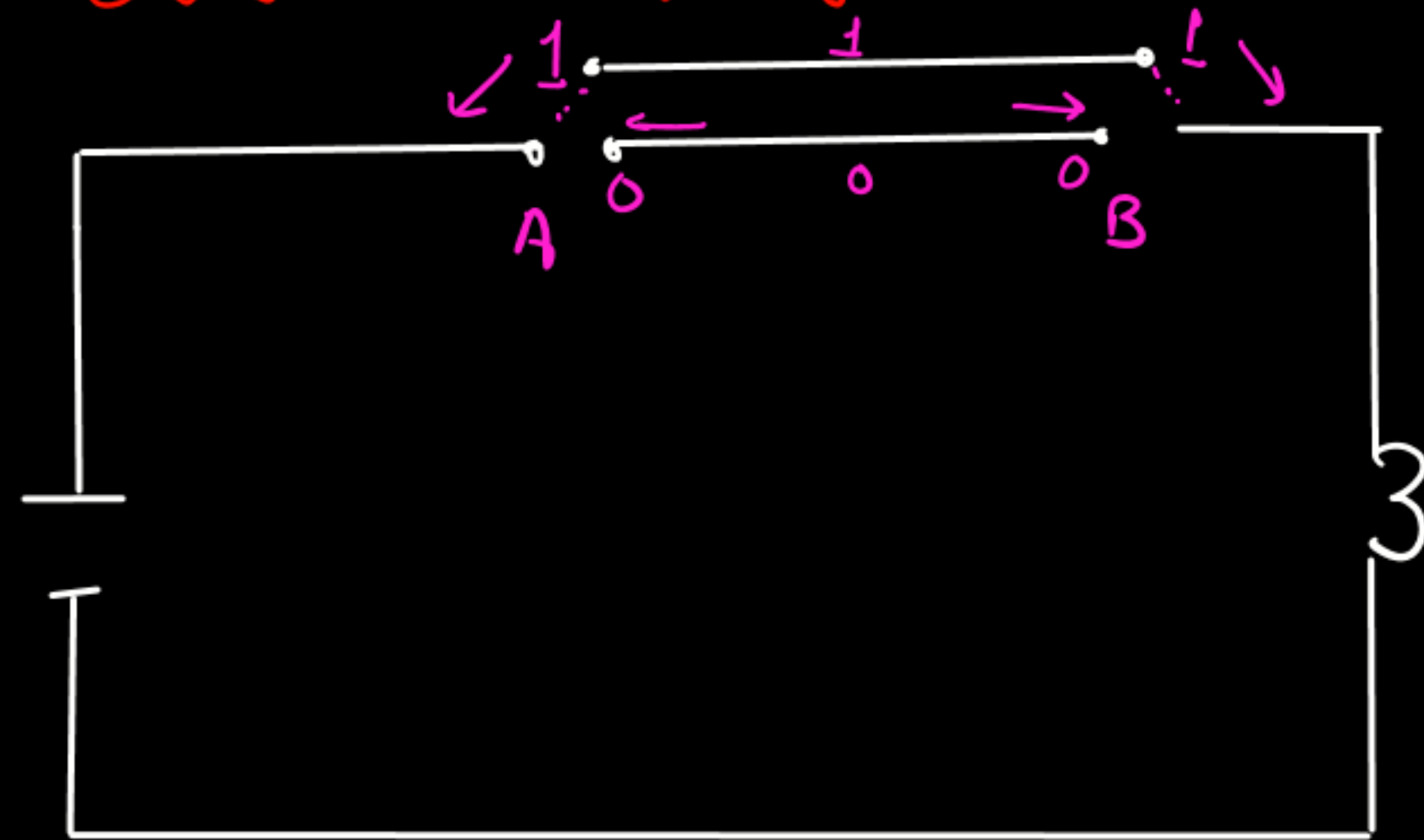

$A=1, B=1, \text{Bulb} = \text{glow (ON)}$

$A=0, B=0, \text{Bulb} = \text{ON}$

\Rightarrow Boolean Algebra \checkmark