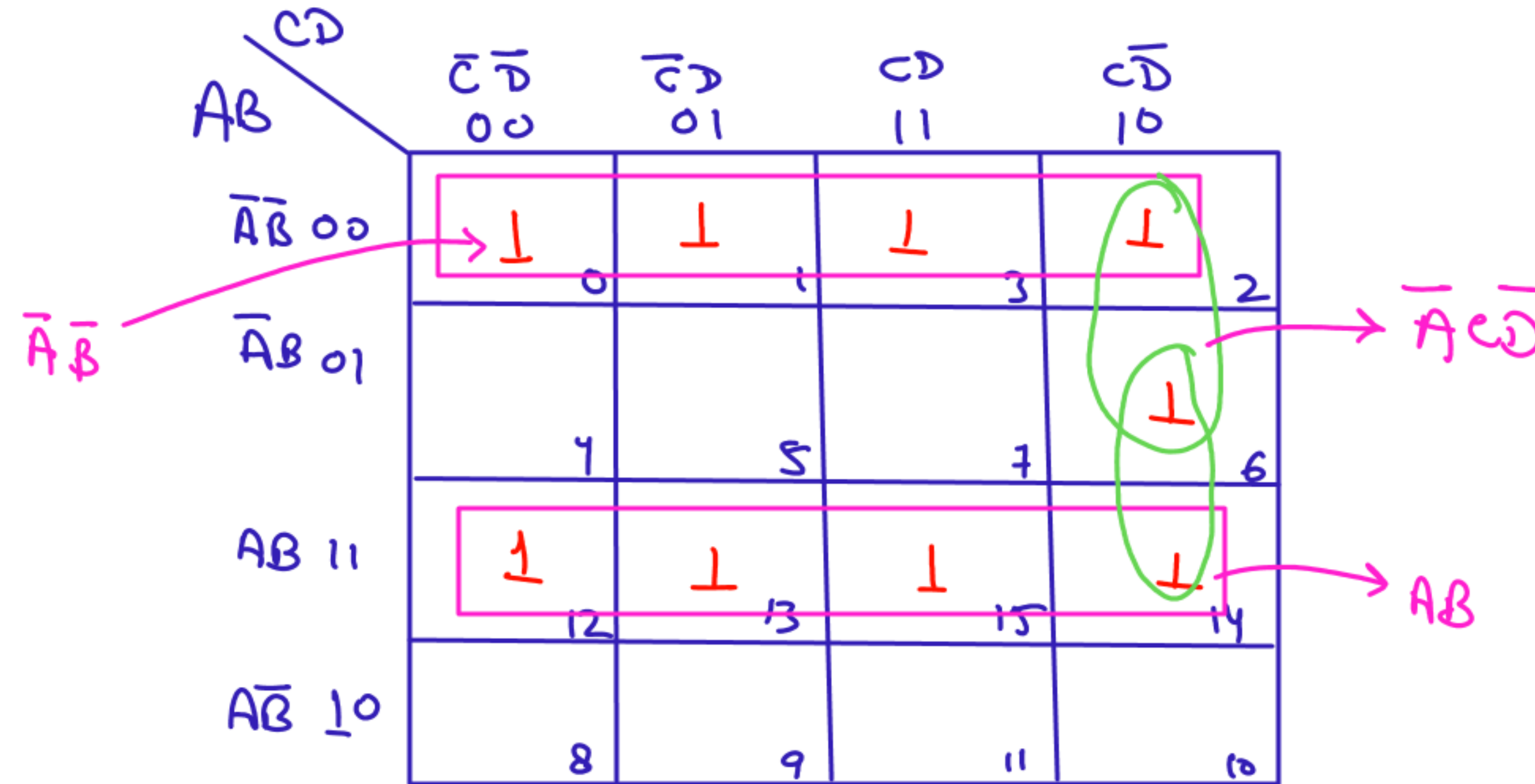


DPP on Boolean Algebra

The simplified expression/s of the following boolean function: $F(A,B,C,D) = \sum(0,1,2,3,6,12,13,14,15)$ is/are:

- A) $A'B' + AB + A'C'D'$
- ✓ B) $A'B' + AB + A'CD'$
- C) $A'B' + AB + BC'D'$
- D) $A'B' + AB + BCD'$



The boolean expression: $AB + AB'$ + $A'C + AC$ is unaffected by the value of the boolean variable _____.

A) A

☒ B) B

C) C

D) A,B,C

$$A(\cancel{B+B'}) + C(\cancel{A+A'})$$

$$\boxed{A+C}$$

The Boolean expression $A'B + AB' + AB$ is equivalent to:

A) $(A+B)'$

☒ B) $A+B$

C) AB

D) $A'B$

$$\bar{A}B + A(\bar{B} + B)$$

$$A + \bar{A}B \Rightarrow A + B$$

$$x + \bar{x}y = x + y$$

The Binary operator \neq is defined by the following truth table. Which one of the following is true about \neq operator?

- ☒ A) Both Commutative and Associative
- ☐ B) Commutative but not Associative
- ☐ C) Not Commutative but Associative
- ☐ D) Neither Commutative Nor Associative

p	q	$p \neq q$
0	0	0
0	1	1
1	0	1
1	1	0

} XOR


Consider the following boolean function with four variables:

$F(w,x,y,z) = \sum(1,3,4,6,9,11,12,14)$ the function is:

- A) Independent of one variable
- ☒ B) Independent of two variables
- C) Independent of three variables
- D) Depends on all variables

$$f = x\bar{z} + \bar{x}z$$

$$= x \oplus z$$

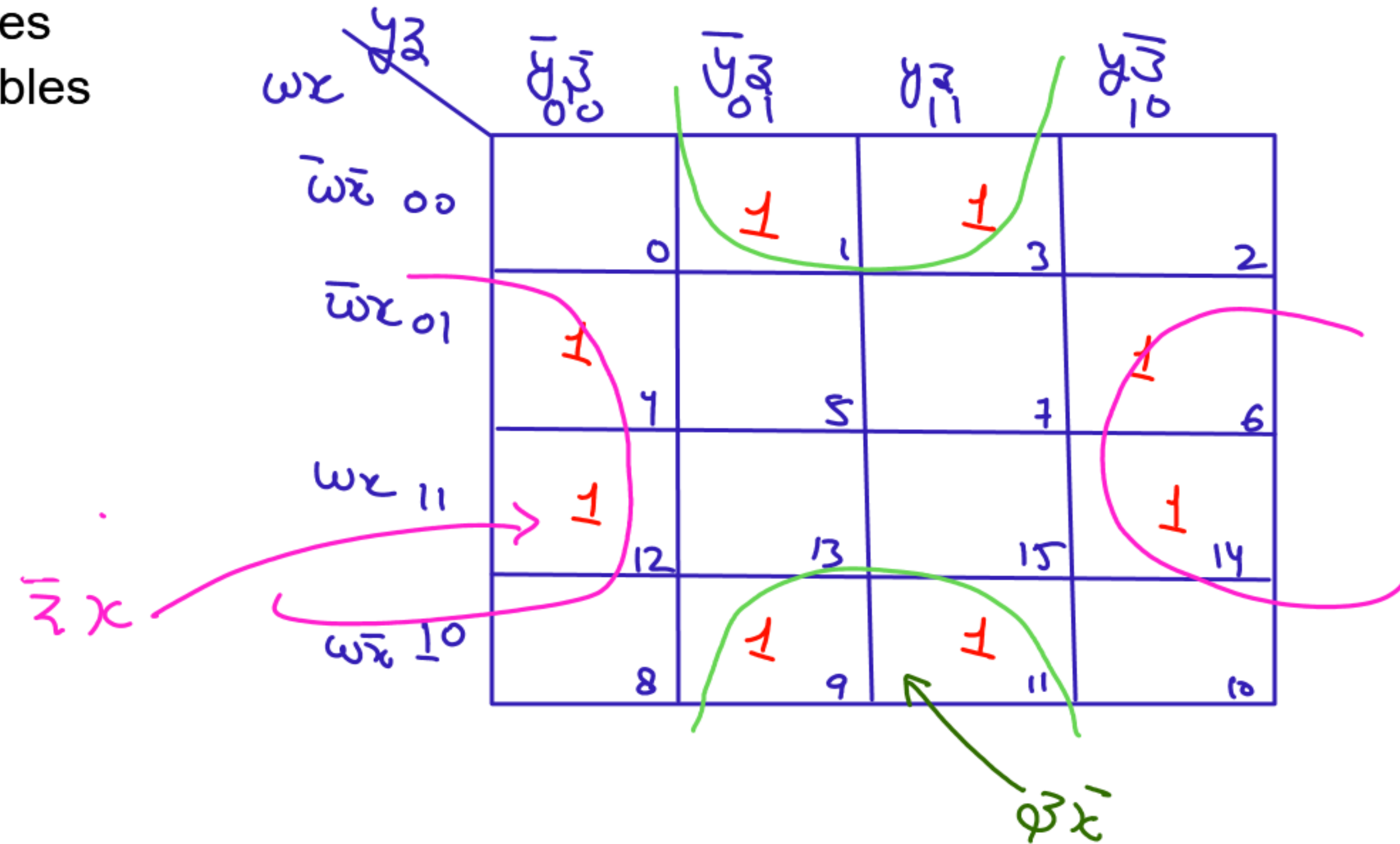


Given f_1 , f_3 and f in canonical SOP form (in decimal) for the circuit.

$$f_1 = \sum m(4,5,6,7,8)$$

$$f_3 = \sum m(1,6,15)$$

$$f = \sum m(1,6,8,15)$$

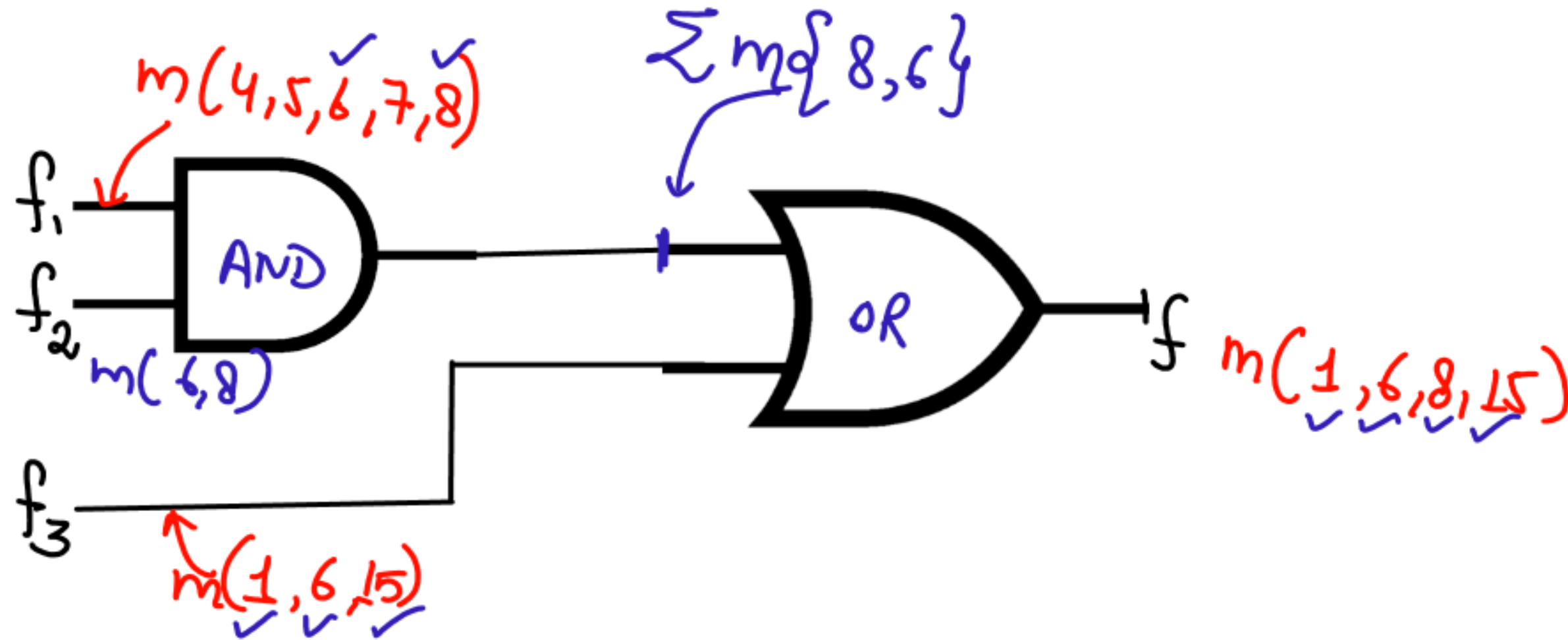

a) $\sum m(4,6)$

b) $\sum m(4,8)$

☒ c) $\sum m(6,8)$

d) $\sum m(4,6,8)$

AND: Intersection of minterms

Common minterms are selected for output

OR: Union of minterms

All minterms for function A & B are selected for output

The simplified SOP form of the Boolean Expression is:

$$(P + \bar{Q} + \bar{R}) \cdot (P + \bar{Q} + R) \cdot (P + Q + \bar{R})$$

- A. $(P'Q+R')$
- ~~B. $(P+Q'R')$~~
- C. $(P'Q+R)$
- D. $(PQ+R)$

$$(P + \bar{Q} + \bar{R}) \cdot (P + \bar{Q} + R) \cdot (P + Q + \bar{R})$$

$$((P + \bar{Q}) \cdot (P + \bar{Q})) + R(P + \bar{Q}) + \bar{R}(P + \bar{Q}) + \cancel{R\bar{R}})(P + Q + \bar{R})$$

$$(\underline{P + \bar{Q}} + \underline{PR} + \underline{R\bar{Q}} + \underline{\bar{R}P} + \underline{\bar{R}\bar{Q}})(P + Q + \bar{R})$$

$$\Rightarrow (P + \bar{Q} + PR + \bar{R} + \bar{Q}R + \bar{Q}\bar{R})(P + Q + \bar{R})$$

$$((P + \bar{Q} + \cancel{P(R + \bar{R})} + \bar{Q}(\cancel{R + \bar{R}})))(P + Q + \bar{R})$$

$$(P + \bar{Q} + \bar{Q})(P + Q + \bar{R}) \Rightarrow (P + \bar{Q})(P + Q + \bar{R})$$


$$\begin{aligned} & PP + PQ + P\bar{R} + P\bar{Q} + \cancel{Q\bar{Q}} + \bar{Q}\bar{R} \\ & P + PQ + \underline{P\bar{R} + P\bar{Q}} + \bar{Q}\bar{R} \\ & \Rightarrow P + \bar{Q}R \end{aligned}$$

Consider the logic circuit shown in the figure below. The functions f1, f2 and f (in canonical SOP form) are:

$$f1(w,x,y,z) = \sum m(8,9,10)$$

$$f2(w,x,y,z) = \sum m(7,8,12,13,18,15)$$

$$f3(w,x,y,z) = \sum m(8,9)$$

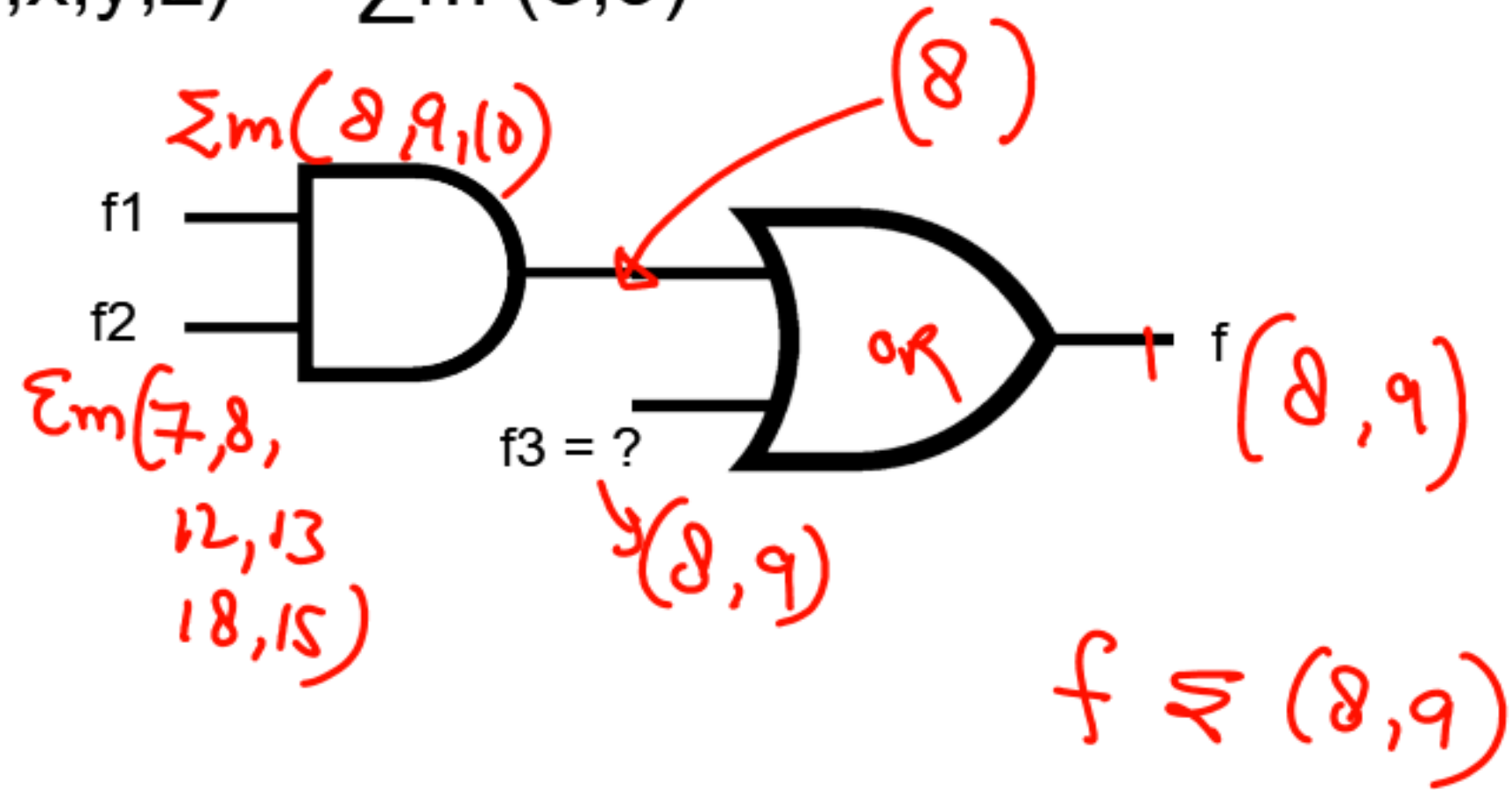

The function f3 is:

A. $\sum 9,10$

☒ B. $\sum 9,8$

C. $\sum 1,8,9$

D. $\sum 8,10,15$

What happens when a bit string is XORed with itself n-times as shown:

$[B \oplus (B \oplus (B \oplus B \dots n \text{ times}))]$

- (a) Complements when n is even
- (b) Complements when n is odd
- (c) Divides by 2^n always
- ☒ (d) Remains unchanged when n is even

$$B \oplus B = 0$$

$$B \oplus 0 = B$$

$n = 2$ (even)

$$B \oplus (B \oplus B) = \underline{B}$$

↓
If no of
XOR gates
are even

$n = 3$ (odd)

$$B \oplus (B \oplus (B \oplus B))$$

$$B \oplus (B \oplus 0)$$

$$B \oplus B \\ = 0$$

* If the number of XOR gate is odd then it's stuck at 0

The function represented by the map given below is:

		BC			
		$\overline{B}\overline{C}$ 00	01	BC 11	10
\overline{A} A 0	0	1		1	
	1	1		1	

Handwritten annotations: Pink circles group the 1s in the first and third columns. Arrows point from these circles to $\overline{B}\overline{C}$ and BC respectively.

(a) $A.B$

(b) $AB + BC + CA$

☒ (c) $(B \oplus C)'$

(d) $A.BC$

$$\begin{aligned} f &= BC + \overline{B}\overline{C} \\ \Rightarrow B \odot C &\leftarrow \overline{B \oplus C} \end{aligned}$$

$f(A, B) = A' + B$. Simplified expression for function $f(f(x+y, y), z)$ is

- (a) $x' + z$
- (b) xyz
- ☒ (c) $xy' + z$
- (d) None of these

$$f(A, B) = \bar{A} + B$$

$$f(x+y, y)$$

$$= \overline{x+y} + y$$

$$\bar{x} \cdot \bar{y} + y$$

$$\boxed{\bar{x} + y}$$

$$\leftarrow \text{RLR } (A + \bar{A}B = A + B)$$

$$f(\bar{x} + y, z) \Rightarrow \overline{\bar{x} + y} + z$$

$$= \bar{\bar{x} + y} + z$$

$$z + x\bar{y}$$


Which are the essential prime implicants of the following Boolean function?

$$f(a, b, c) = a'c + ac' + b'c$$

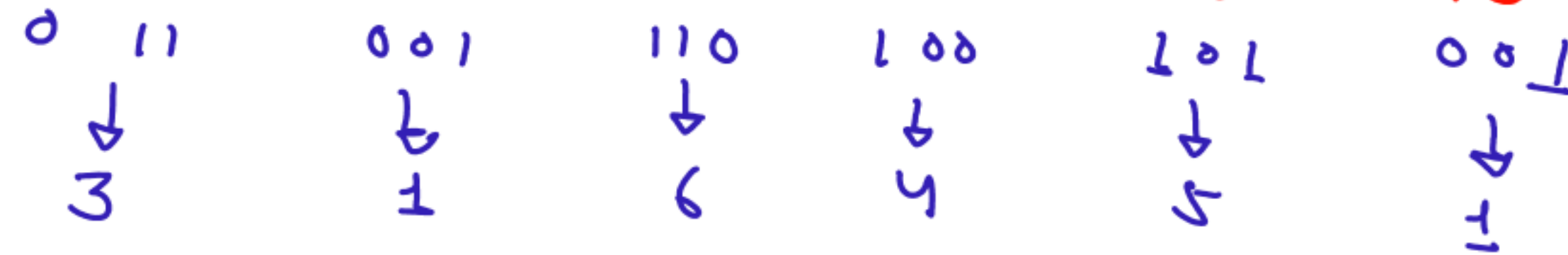- (a) $a'c$ and ac'
- (b) $a'c$ and $b'c$
- (c) $a'c$ only
- (d) ac' and bc'


$$\Rightarrow \bar{a}c \cdot (b + \bar{b}) + a\bar{c} \cdot (b + \bar{b}) + \bar{b}c \cdot (a + \bar{a})$$

$$\Rightarrow \bar{a}bc + \bar{a}\bar{b}c + a\bar{b}\bar{c} + a\bar{b}c + a\bar{b}c + \bar{a}\bar{b}c$$



$$f = \sum m(1, 3, 4, 5, 6)$$

$$f = \bar{A}\bar{B} + \bar{A}C + AC$$

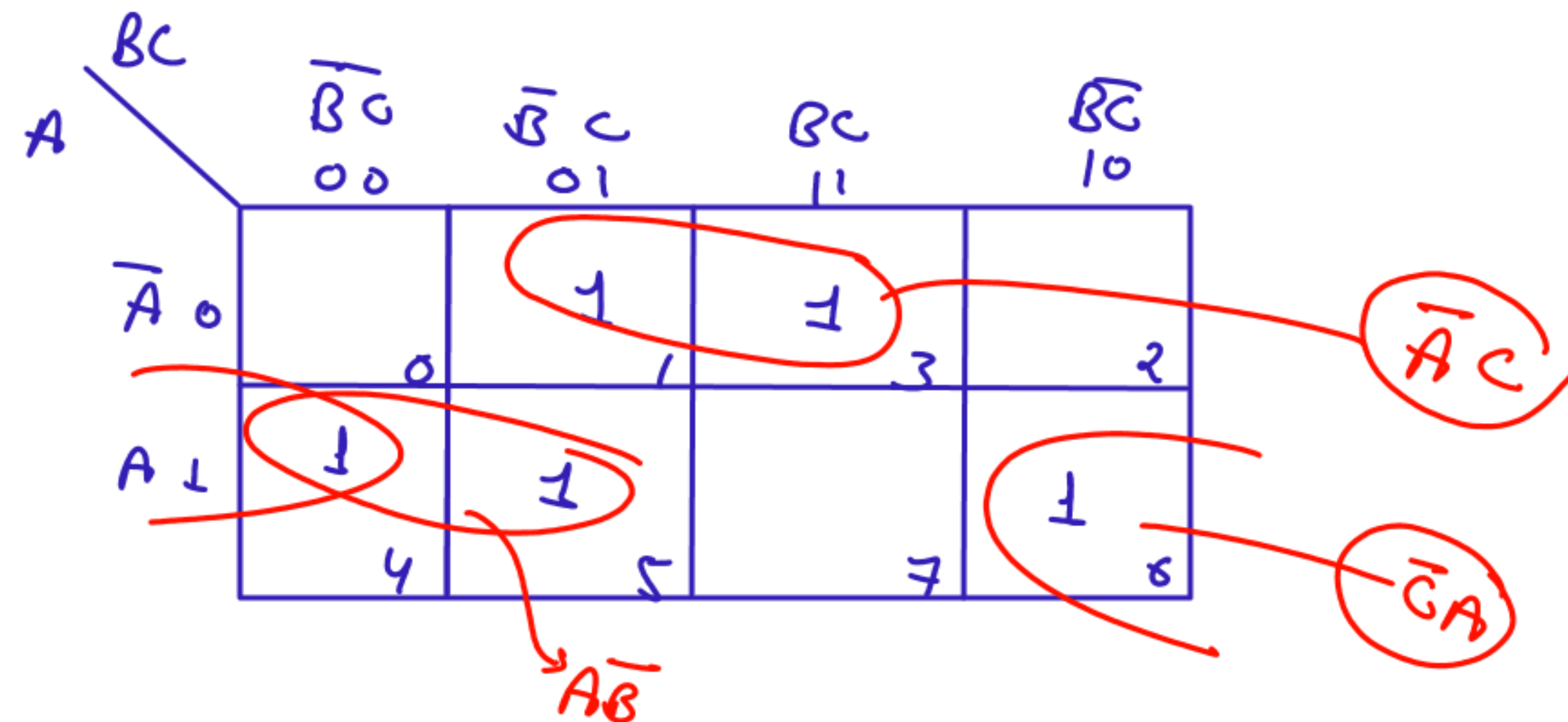

Which of the following expressions is equivalent to $A \oplus B \oplus C$?

(a) $(A+B+C) (A' + B' + C')$ ← 2 Max

(b) $(A+B+C) (A' + B' + C)$ ← 2 Max

(c) $ABC + A' (B \oplus C) + B' (A \oplus C)$

(d) None of these

$$ABC + \bar{A}(B\bar{C} + \bar{B}C) + \bar{B}(A\bar{C} + \bar{A}C)$$

$$\Rightarrow ABC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C$$

\downarrow
 111 010 001 100 001

⇒

XOR → If there are 3 inputs
 XOR Searches for odd number
 of 1's or
 Even no of zeroes

$\Pi M(1, 3, 5, 6)$


$\Sigma m(1, 2, 4, 7)$

	A	B	C	$A \oplus B \oplus C$
0	0	0	0	0 (M)
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0 (M)
4	1	0	0	1
5	1	0	1	0 (M)
6	1	1	0	0 (M)
7	1	1	1	1

The switching expression corresponding to $f(A,B,C,D) = \sum m(1,4,5,9,11,12)$ is

- ~~(a) $BC'D' + A'C'D + AB'D$~~
 (b) $ABC' + ACD + B'C'D$
 (c) $ACD' + A'BC' + AC'D'$
 (d) $A'BD + ACD' + BCD'$
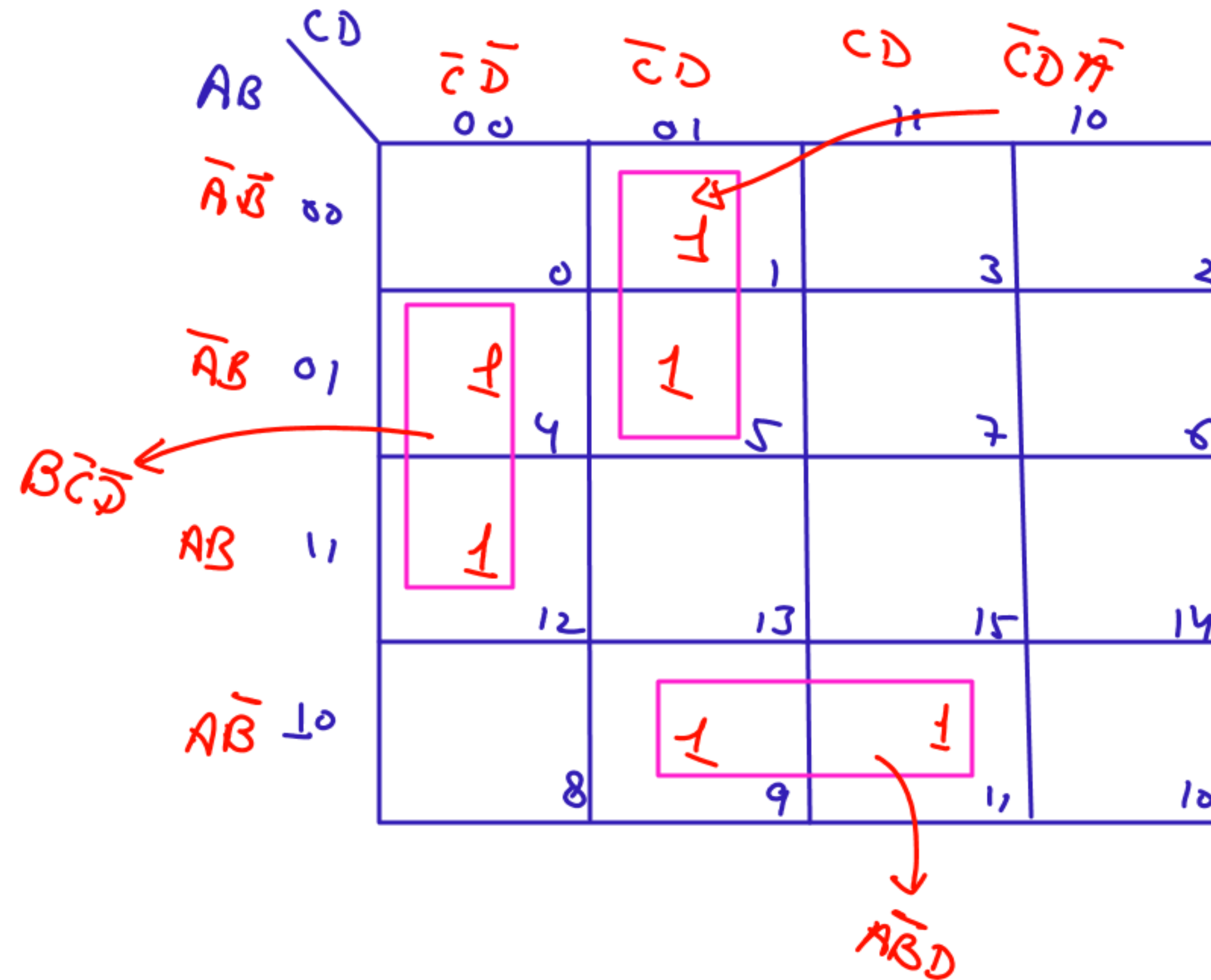
$$f = A\bar{B}D + B\bar{C}\bar{D} + \bar{A}\bar{C}D$$



What is maximum number of different Boolean functions involving in 'n' Boolean variables?

(a) n^2

(b) 2^n

(c) 2^{2^n}

(d) 2^{n^2}

for n variables there are 2^n combinations

for n combinations we can define 2^n functions

\Rightarrow for ' n ' variables = 2^{2^n} combinations (REMEMBER)

Consider the following Boolean function of four variables $f(w,x,y,z) = \sum m(1,3,4,6,9,11,12,14)$

The function is

- (a) independent of one variable
- (b) independent of two variables
- (c) independent of three variables
- (d) dependent on all the variables

"do yourself"

The following expression was to be realized using 2-input AND and OR gates. However, during the fabrication all 2-input AND gates were mistakenly substituted by 2-input NAND gates.

What is the function finally realized?

- (a) 1
- (b) $a' + b' + c' + d'$
- ☒ (c) $a' + b + c' + d'$
- (d) $a' + b' + c + d'$

$$f = (a.b).c + (a'.c).d + (b.c).d + a.d$$

$$f = \overline{a \cdot b \cdot c} + \overline{a' \cdot c \cdot d} + \overline{b \cdot c \cdot d} + \overline{a \cdot d}$$

$$\Rightarrow \overline{\overline{a} \cdot \overline{b} \cdot \overline{c}} + \overline{\overline{a} \cdot \overline{c} \cdot \overline{d}} + \overline{\overline{b} \cdot \overline{c} \cdot \overline{d}} + \overline{\overline{a} \cdot \overline{d}}$$

$$\Rightarrow ab + \overline{c} + ac + \overline{d} + bc + \overline{d} + \overline{a} + \overline{d}$$

$$\Rightarrow ab + \overline{c} + ac + \overline{d} + bc + \overline{a}$$

$$ab + \overline{c} + \overline{a} + \overline{d} + \overline{d} + bc + \overline{a}$$

$$ab + \overline{c} + \overline{d} + bc + \overline{a}$$

$$ab + \overline{d} + \overline{c} + b + \overline{a}$$

$$b(a+1) + \overline{c} + \overline{d} + \overline{a}$$

$$= b + \overline{c} + \overline{d} + \overline{a}$$

$$\overline{a \cdot b} = \overline{a} + \overline{b}$$

$$A + \overline{A}B$$

$$\overline{C} + ca$$

$$\overline{C} + a$$


$$\overline{C} + cb$$

$$\overline{C} + b$$

The line T in the following figure is permanently connected to the ground.

Which of the following inputs (X1,X2,X3,X4) will detect the fault?

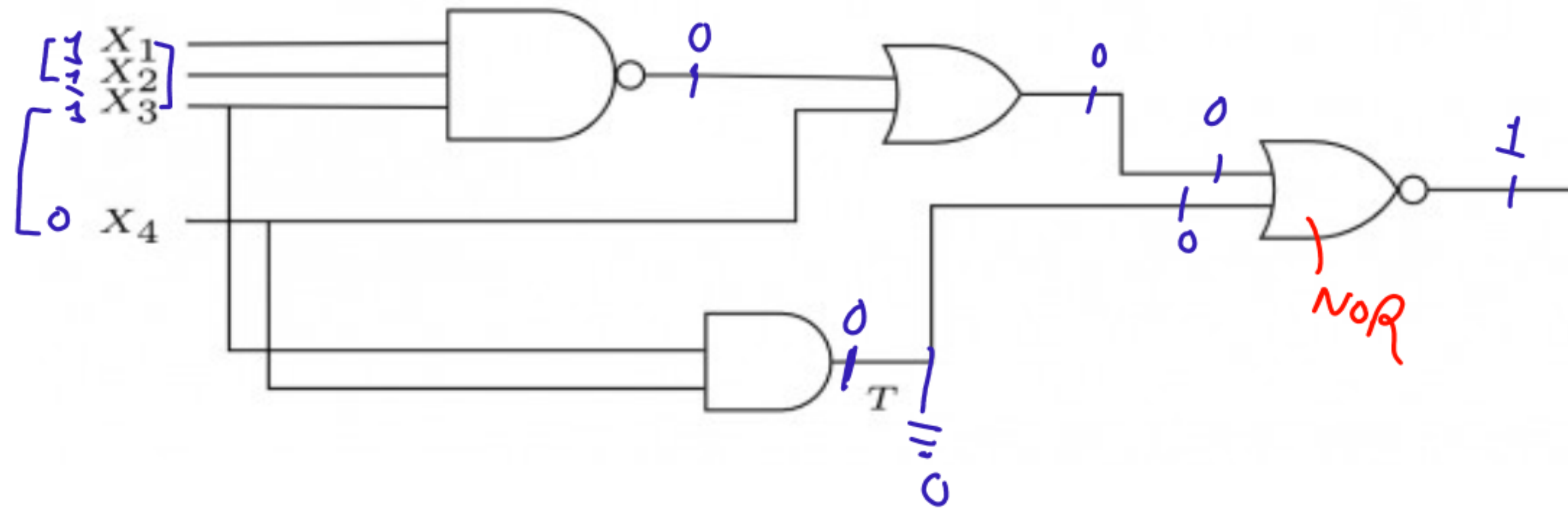- (a) 0000
- (b) 0111
- (c) 1111
- ☒ (d) None of these



A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

* It is not possible to detect the fault.

The total number of prime implicants of the function $f(w,x,y,z) = \sum m(0,2,4,5,6,10)$ is _____.

↓
Do yourself (H.W)