

Recall \rightarrow 4 steps

1) Identify the Problem Statement & I/O

2) Design the Truth Table

3) Write the Expression in form of Minterm or Maxterm, & Simplify using K-Maps


4) Design the logical Circuit.

Arithmetic Circuit

→ Half adder: A circuit which add two bits.

• A half adder is defined as a basic four terminals digital device which add two Binary digits'.
4 Input/outputs

S _{no}	A	B	A+B	Decimal o/p	Binary o/p	Sum	Carry
0	0	0	0+0	0	0	0	0
1	0	1	0+1	1	1	$1 \bar{A}B$	0
2	1	0	1+0	1	1	$1 A\bar{B}$	0
3	1	1	1+1	2	10	0	$1 AB$

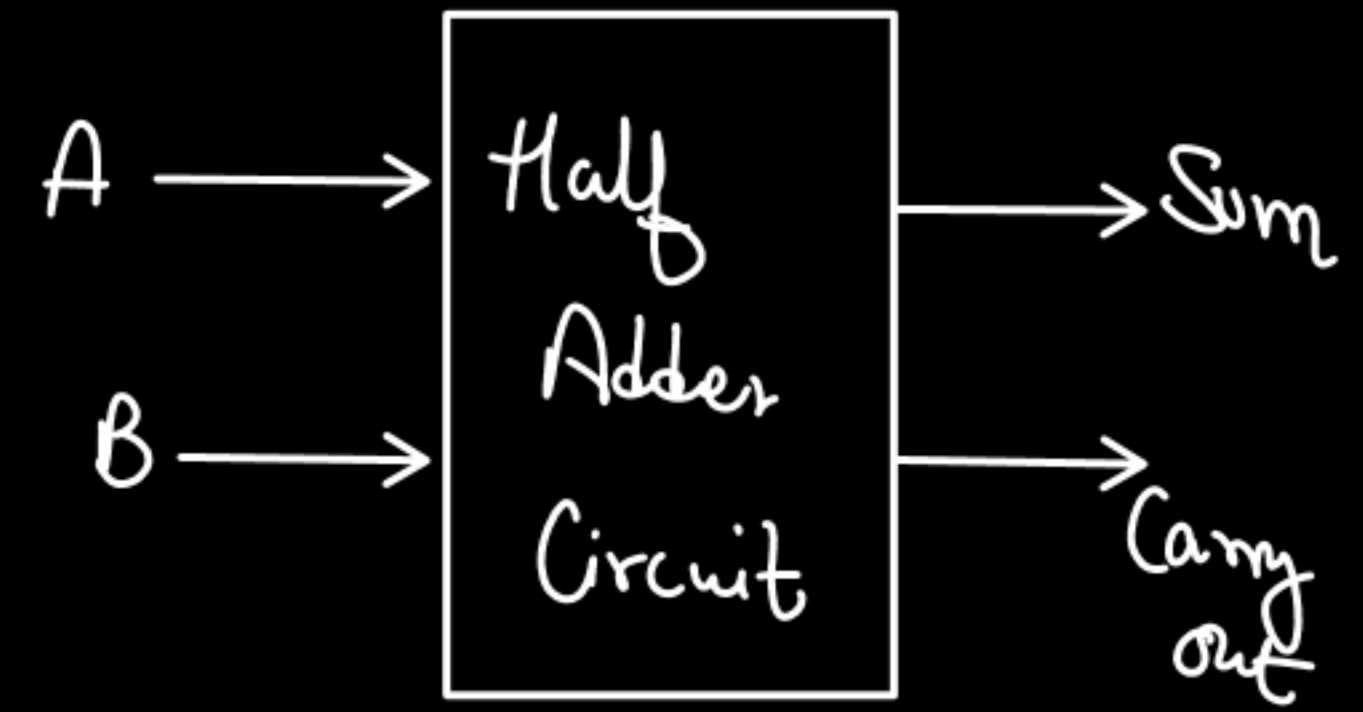


$$\text{Sum} = \bar{A}B + A\bar{B} = A \oplus B$$
$$\text{Carry}_{\text{out}} = AB$$

AND

$$\text{Sum} = \bar{A}B + A\bar{B} = A \oplus B$$

$$\text{Carry} = AB$$

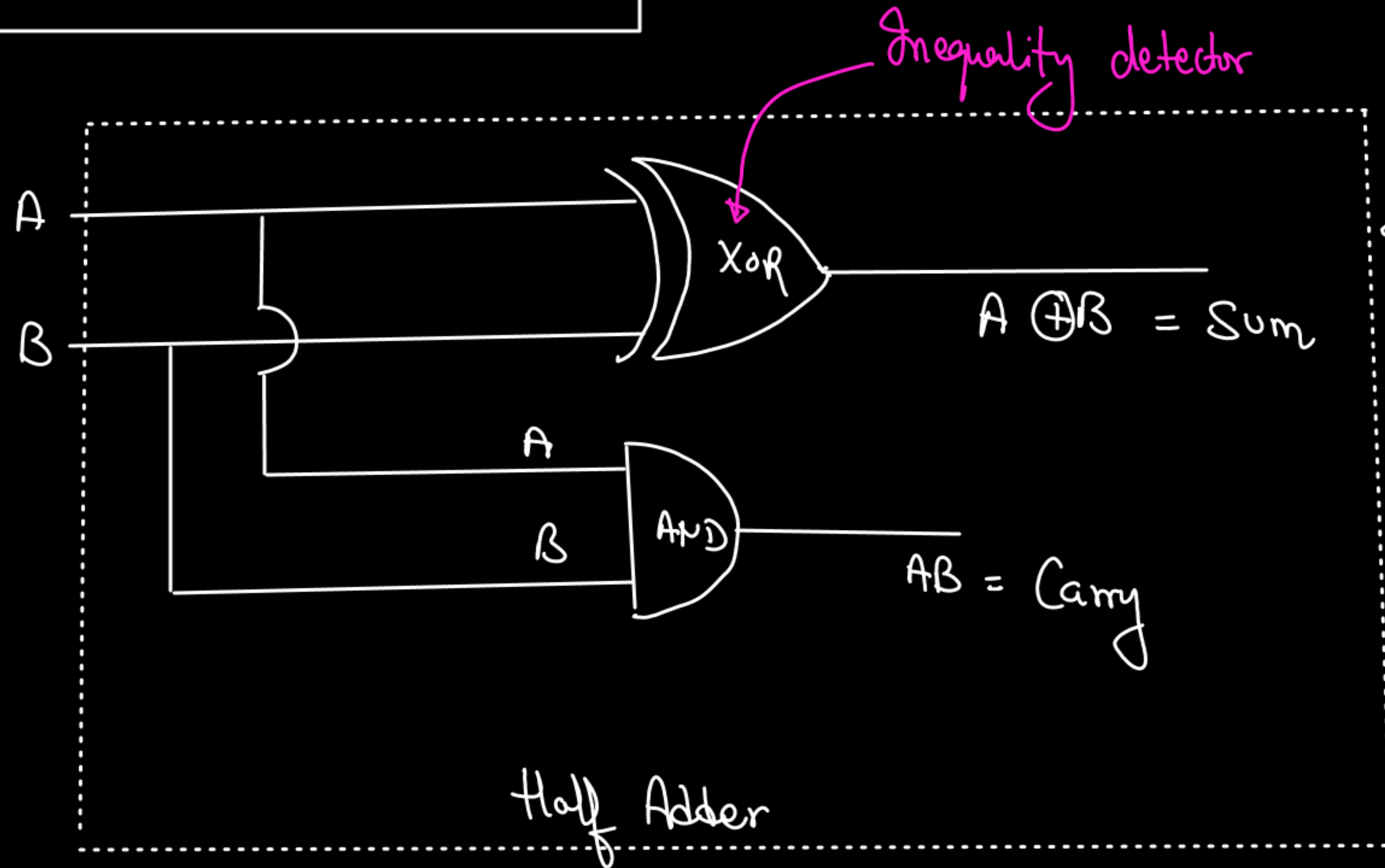Task: → Make Half Adder
using NAND & NOR
gate



* Half adder
requires 5 NAND
OR 5 NOR gates



Half Subtractor:

→ Is a circuit that subtracts two bits
→ No. of I/P = 2 & o/p = 2 (4 terminals)

S.No	A	B	difference	Borrow
0	0	0	0	0
1	0	1	<u>1</u> $\bar{A}B$	<u>1</u> $\bar{A}B$
2	1	0	1 $A\bar{B}$	0
3	1	1	0	0

$$\begin{aligned}\text{difference} &= A\bar{B} + \bar{A}B \\ &= A \oplus B\end{aligned}$$
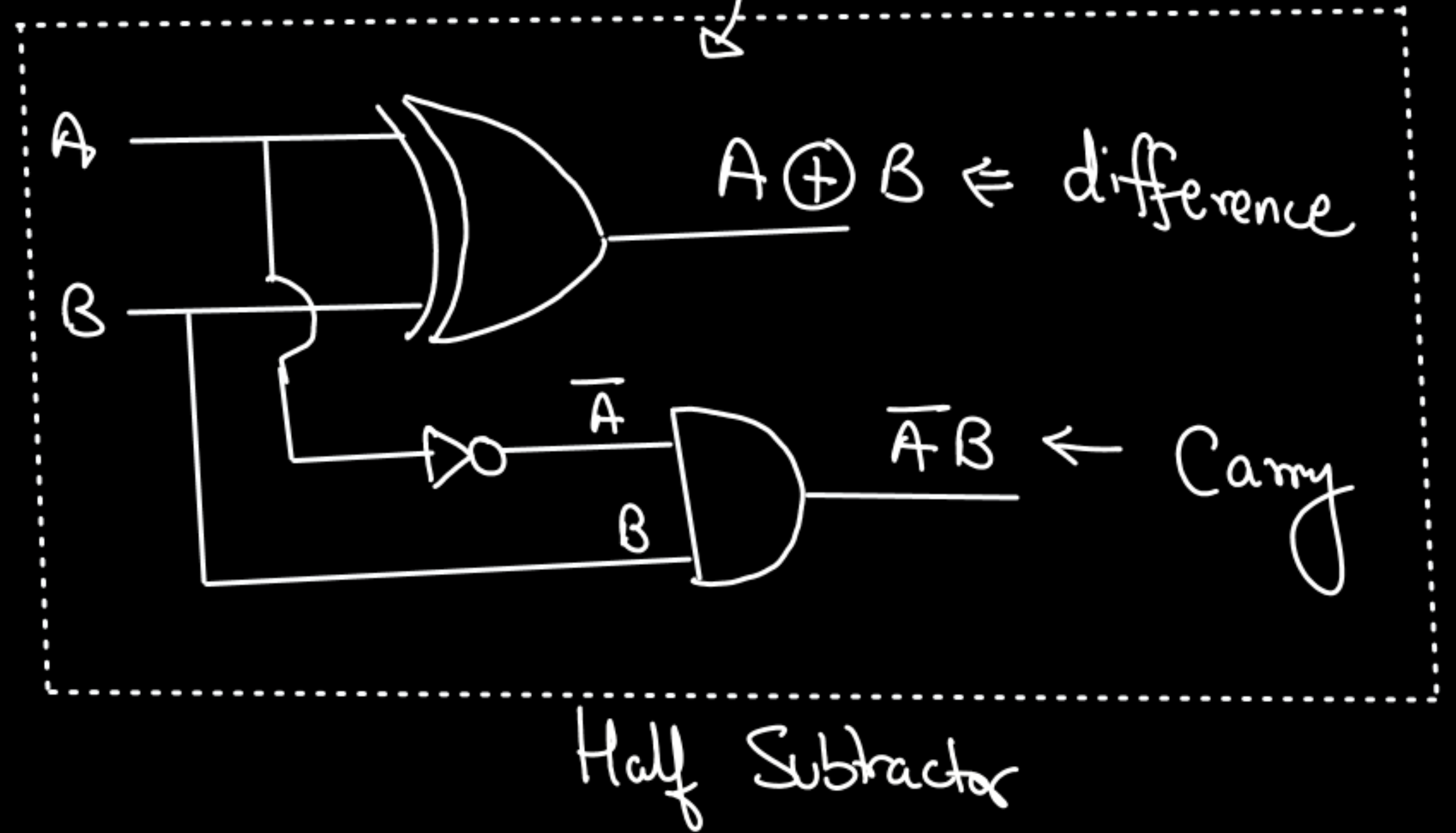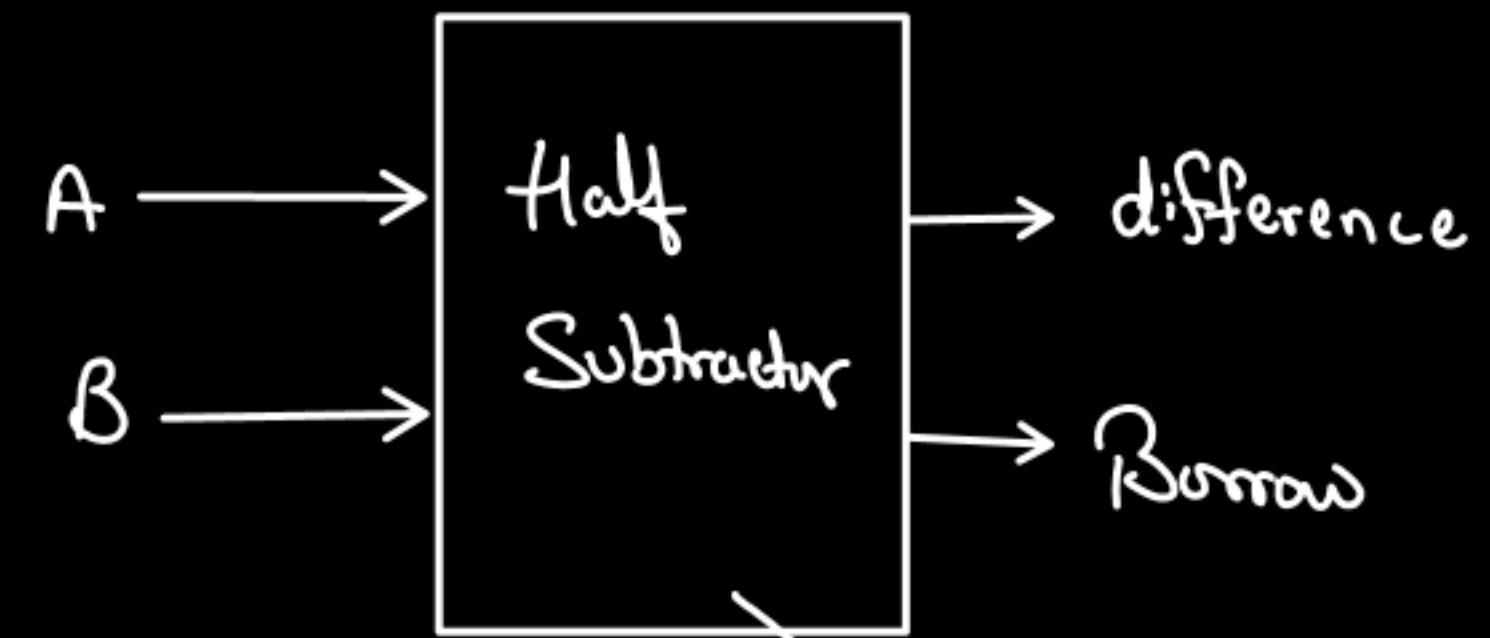
$$\begin{aligned}\text{Carry} &= \bar{A}B \\ &\downarrow \\ &\text{AND}\end{aligned}$$




* Difference of half subtractor is same as sum in a half adder.
but in Borrow, we have to take the complement of Minuend.

Full Adder Concept:

* It has three inputs & produce two outputs. first two I/Ps are A, B but the third input represented as C_{in} .

	A	B	C_{in}	Sum	Carry
0	0	0	0	0	0
1	0	0	1	1 $\bar{A}\bar{B}C$	0
2	0	1	0	1 $\bar{A}B\bar{C}$	0
3	0	1	1	0	1 $\rightarrow \bar{A}BC$
4	1	0	0	1 $A\bar{B}\bar{C}$	0
5	1	0	1	0	1 $\rightarrow A\bar{B}C$
6	1	1	0	0	1 $\rightarrow AB\bar{C}$
7	1	1	1	1 ABC	1 $\rightarrow ABC$

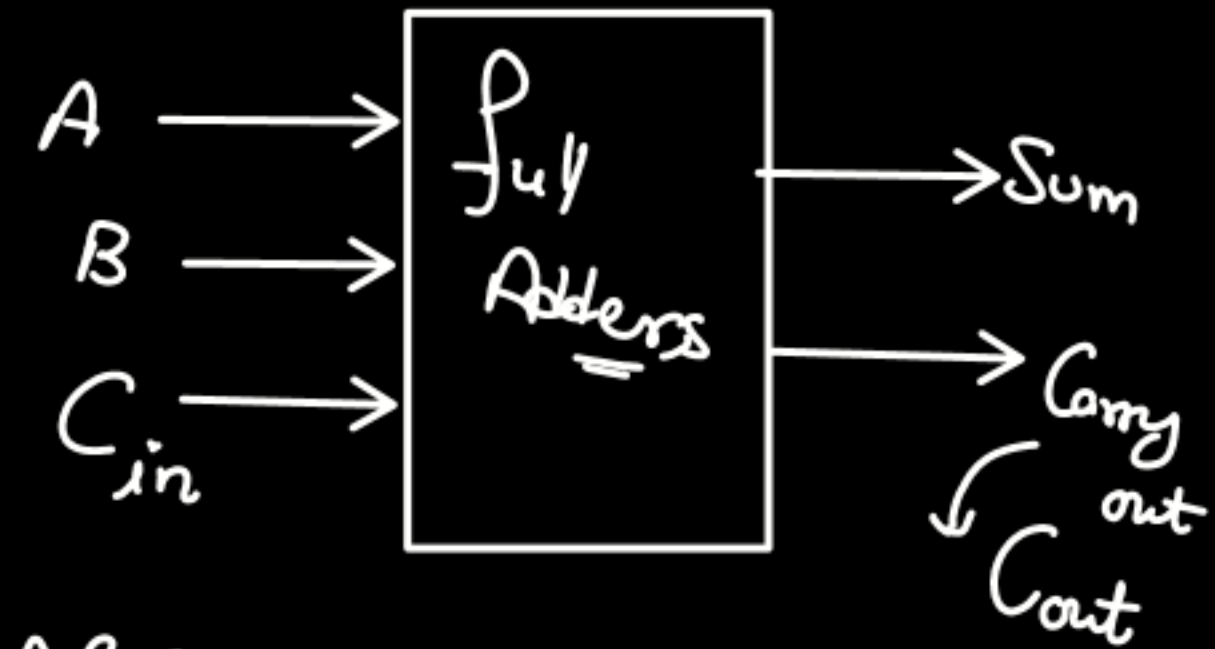

for Sum:

$$f = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$f(A, B, C_{in}) = \sum m(1, 2, 4, 7)$$

for Carry: $f = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$

$$f(A, B, C_{in}) = \sum m(3, 5, 6, 7)$$

for Sum:

$$f(A, B, C) = \sum m(1, 2, 4, 7)$$

A \ BC				
	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	BC 11	$B\bar{C}$ 10
\bar{A} 0	0	1	3	1
A 1	1	5	1	6

⇒ No grouping possible

XOR & XNOR

→ In this case, all minterms has odd no. of 1's as input by using, XOR property for multiple inputs,

$$f(A, B, C) = \sum m(1, 2, 4, 7) = A \oplus B \oplus C_{in}$$

← Pattern

for Carry Out:

$$f(A, B, C) = \sum m(3, 5, 6, 7)$$

A \ BC				
	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	BC 11	$B\bar{C}$ 10
\bar{A} 0	0	1	1	2
A 1	4	1	1	1

AC (red box), BC (blue box), AB (yellow box)

(out = f = $AB + BC + AC$ (Simplified) AND-OR

$$f = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC \text{ (Complex) (SOP)}$$

$$C(\bar{A}B + A\bar{B}) + AB(C + \bar{C})$$

$$\Rightarrow AB + (A \oplus B)C_{in}$$

Revision

Let $y = A \oplus B \oplus C$

↳ 3 input XNOR Gate is same as 3 input XOR operation

* for multiple inputs, XOR searches for odd number of 1's

But XNOR gate searches for even number of 0's

$A \oplus B \oplus C$
if no. of 1's
are odd the
o/p = 1

* for odd number of inputs

↳ odd number of 1's will be same as even no. of zeros

$$\boxed{XNOR = XOR}$$

✓

* for even number of input,

$$\boxed{XNOR = \overline{XOR}}$$

✓

for Sum

$$f(A, B, C) = \sum m(1, 2, 4, 7) \\ = A \oplus B \oplus C_{in}$$

for Carry

$$\Rightarrow AB + (A \oplus B) C_{in}$$

