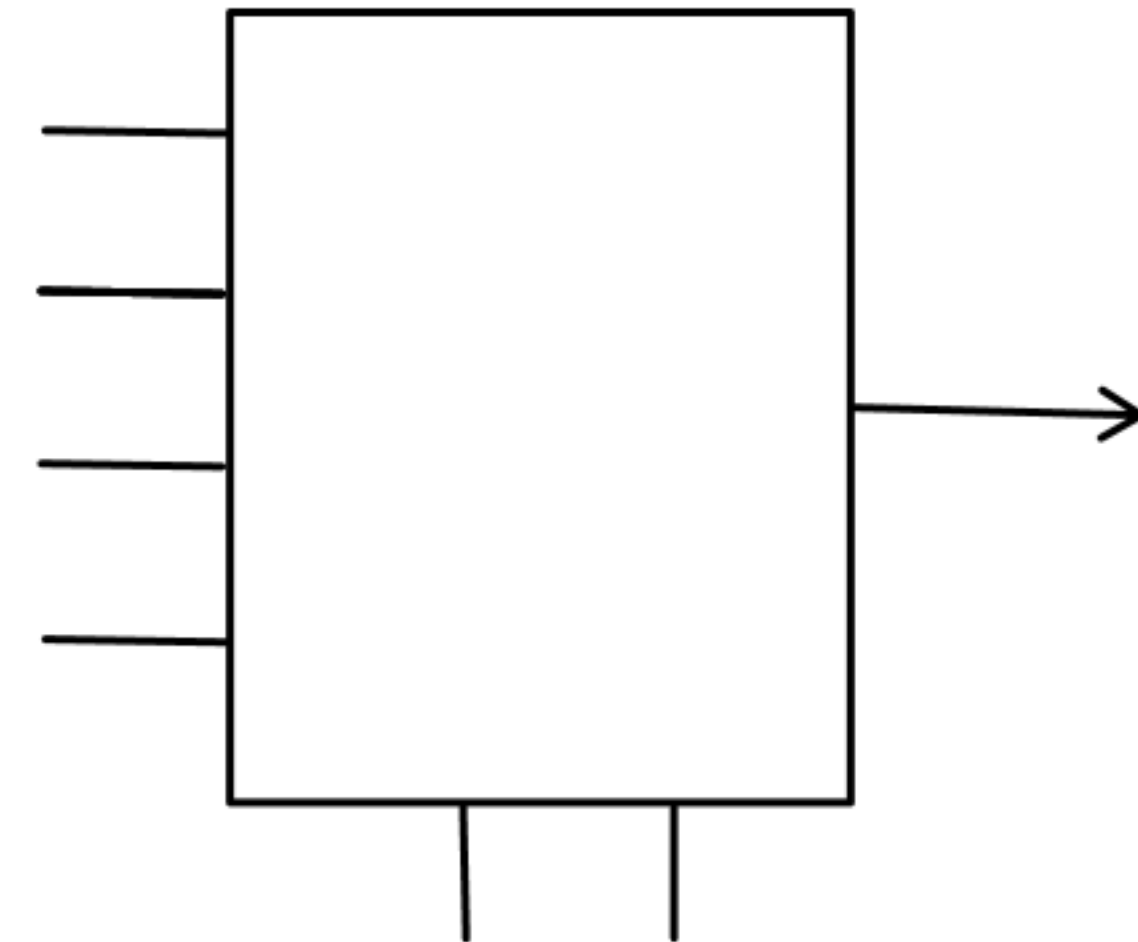


# IMPLEMENTATION OF BOOLEAN FUNCTIONS USING MULTIPLEXER



## IMPLEMENTATION OF BOOLEAN FUNCTIONS USING MULTIPLEXER


- Set the Number of variables (n) = Number of select lines
- All variables are connected to the select lines
- The desired output is connected to the input line in the same order of MSB to LSB

Example: Implement  $f(A,B) = \sum(1,3)$  using MUX

MSB LSB

	A	B	Y
$m_0$	0	0	0
$m_1$	0	1	1
$m_2$	1	0	0
$m_3$	1	1	1

# method 1:  
↓  
less effective

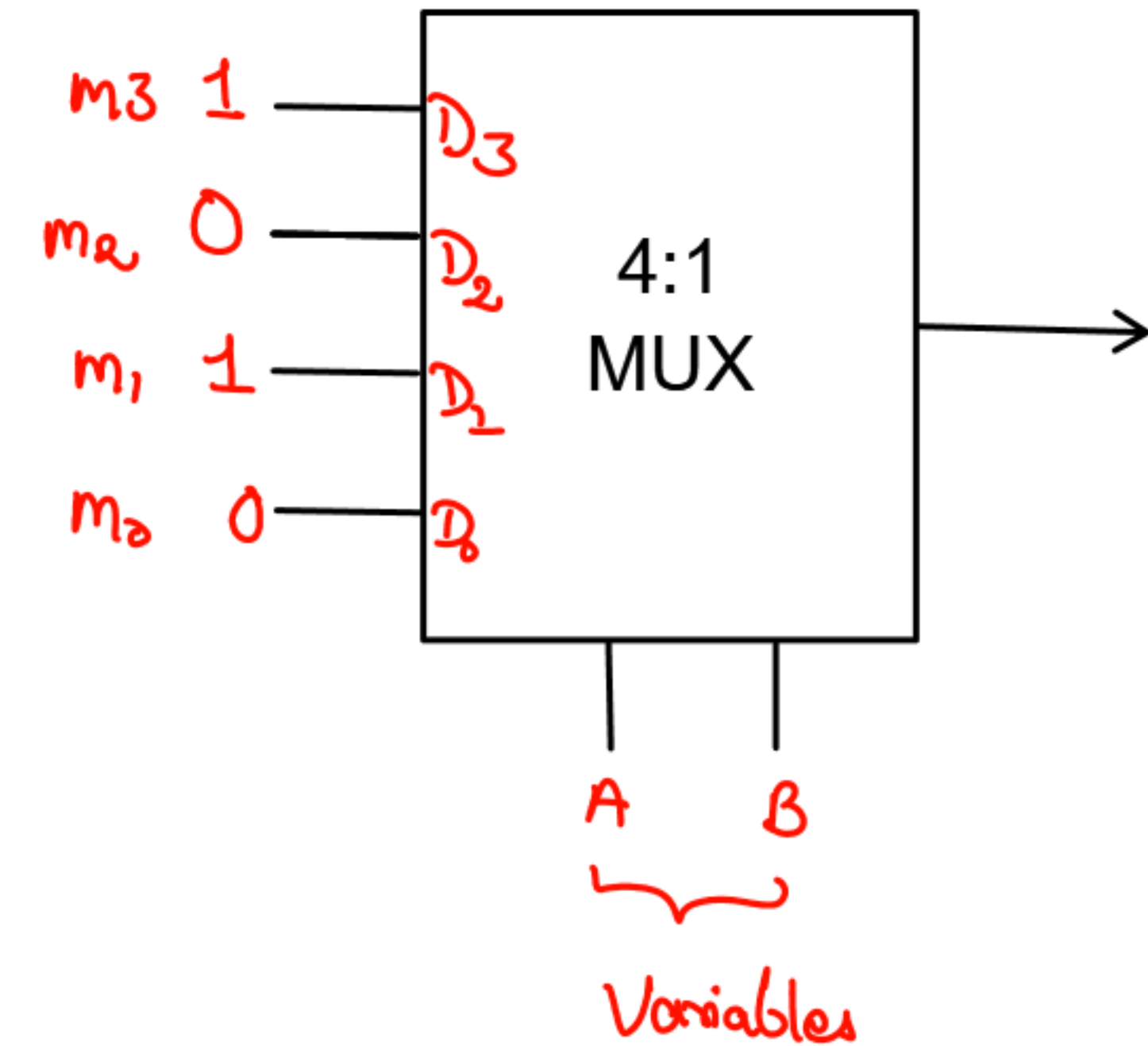

## IMPLEMENTING FUNCTION KEEPING N-1 VARIABLES AS SELECT LINE MUX


- STEP 1 - Draw the truth table for given number of variable function
- STEP 2 - Consider one variable as input and another variables as select lines
  - From the Implementation table where select lines of mux are columns and one input variable and its components are rows.
- STEP 3 - Find AND between rows on the basis of the truth table.
- STEP 4 - So the outcome are considered as input lines for MUX.


Example: Implement  $f(A,B,C) = \sum(0,1,4,7)$  using 4:1 MUX

TRUTH TABLE				
	A	B	C	Y
0	0	0	0	1
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

let A & B are the  
Select line and C  
is Input Variable

2 Select  
lines

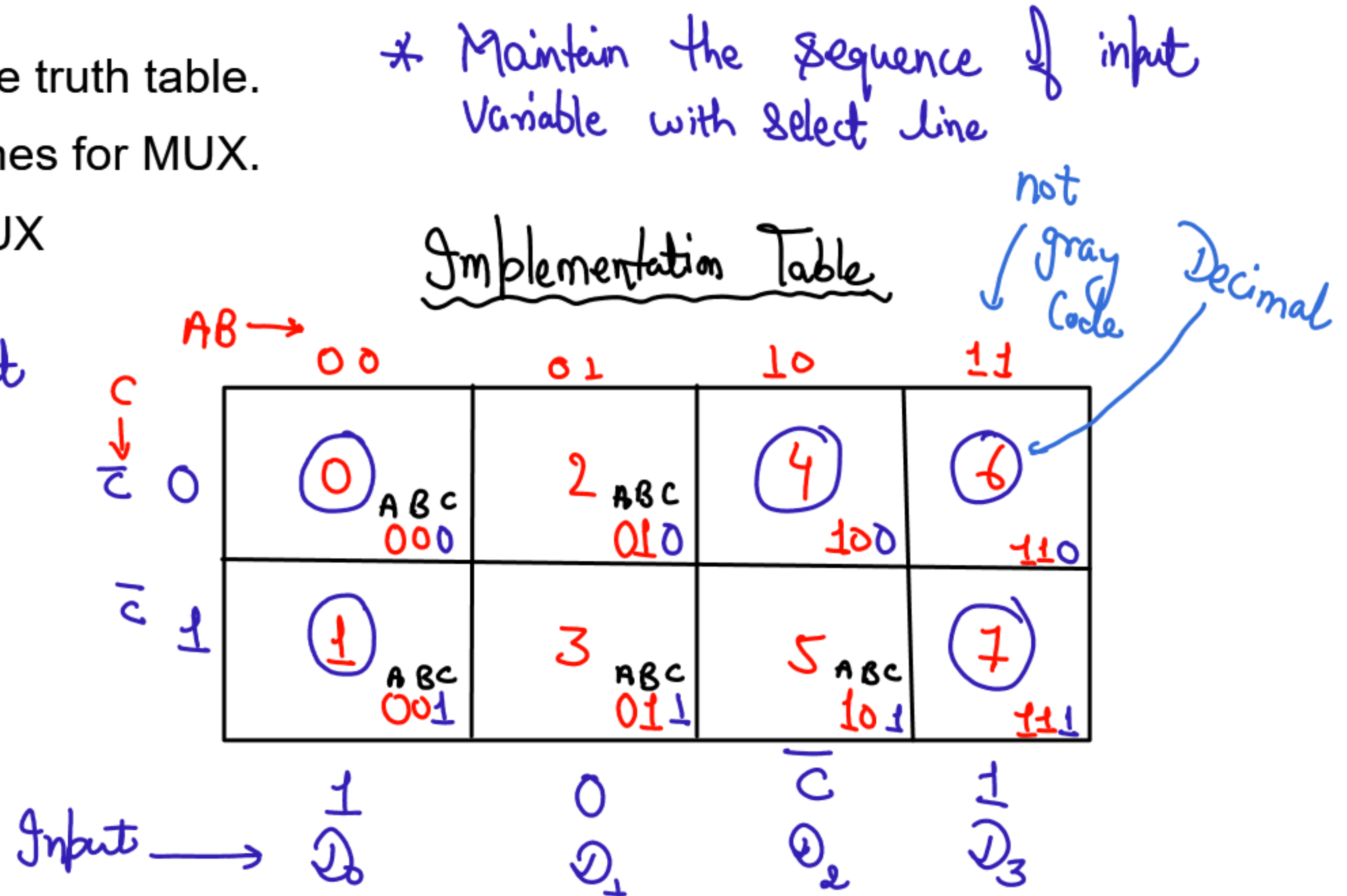

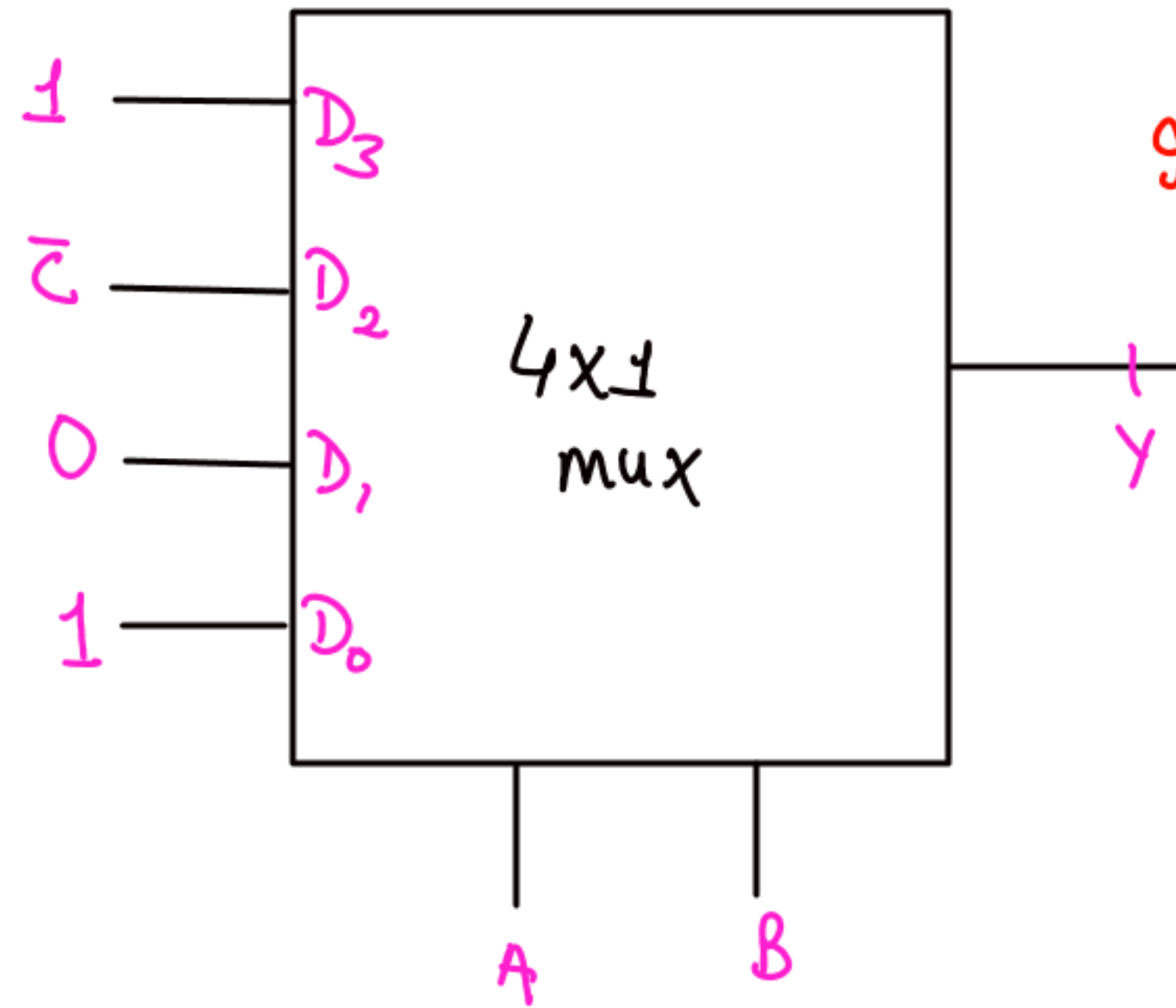

\* Implementation table is NOT a K-map.


taking A as input line and BC as a select line.  
 $f(ABC) = \sum m(0, 1, 4, 6, 7)$

SL  $\rightarrow$  9/p  $\rightarrow$  A  $\downarrow$   $\bar{A}$  0

	BC $\rightarrow$ 00	01	10	11
A $\downarrow$ 0	0 000	1 001	2 010	3 011
A 1	4 100	5 101	6 110	7 111
	1 $D_0$	$\bar{A}$ $D_1$	A $D_2$	A $D_3$

Straight Binary Code

B	C	Y
0	0	1 $D_0$
0	1	$\bar{A}$ $D_1$
1	0	A $D_2$
1	1	A $D_3$

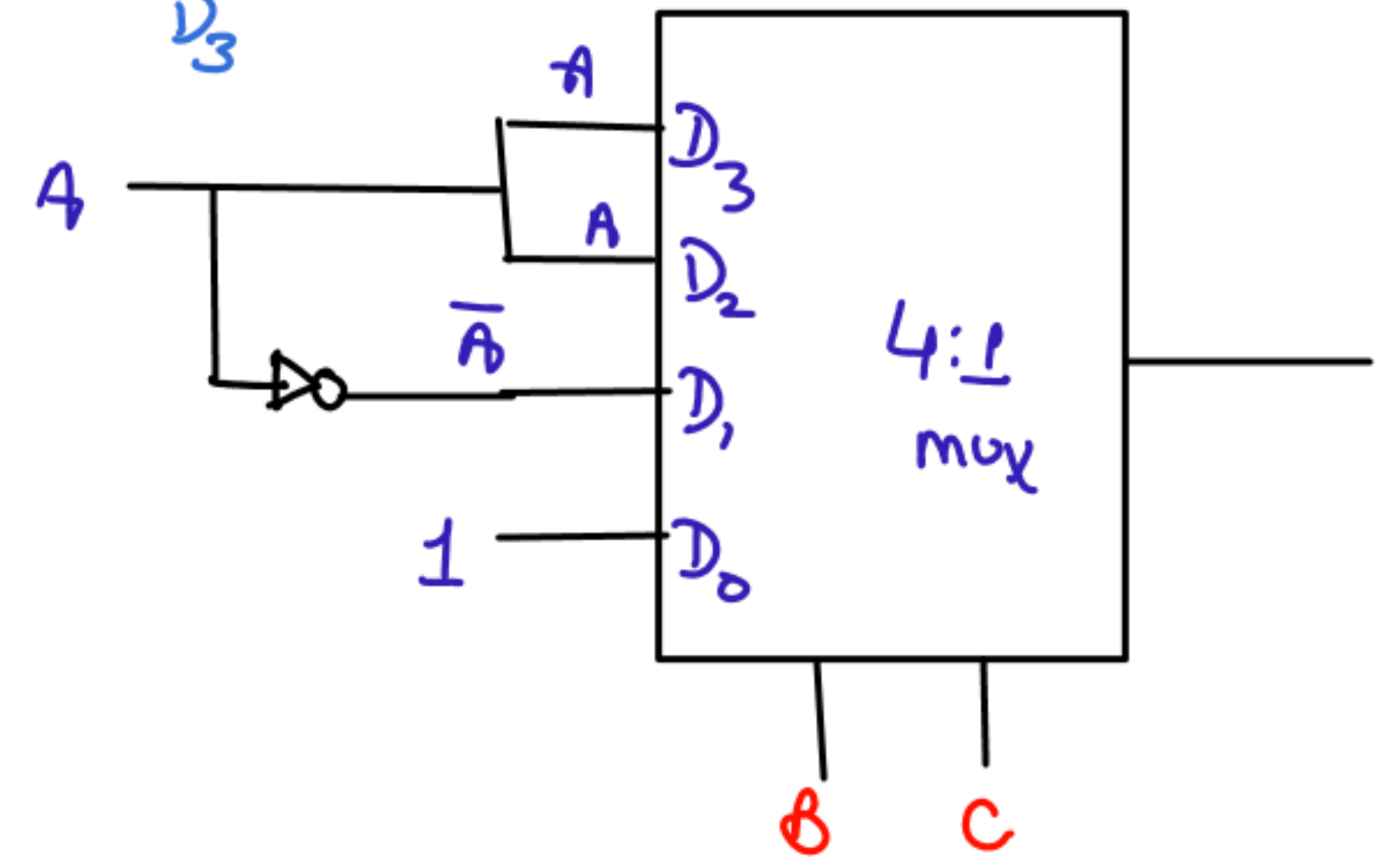



$$f(ABC) = \sum m(0, 1, 4, 6, 7)$$

$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\underline{B\bar{C}} + \underline{ABC} \leftarrow \text{SOP form}$$

$$\begin{array}{l} \bar{B}\bar{C}(A + \bar{A}) \\ \bar{B}\bar{C} \cdot 1 \end{array}$$

$$\begin{array}{l} \bar{A} \cdot \bar{B}C \\ \bar{A} \end{array}$$

$$\begin{array}{l} A\bar{B}\bar{C} \\ \downarrow \\ A \end{array}$$

$$\begin{array}{l} A \cdot BC \\ \downarrow \\ A \end{array}$$

$$\Rightarrow \begin{array}{l} 1 \\ \mathcal{D}_0 \end{array}$$

$$\begin{array}{l} \bar{A} \\ \mathcal{D}_1 \end{array}$$

$$\begin{array}{l} A \\ \mathcal{D}_2 \end{array}$$

$$\begin{array}{l} A \\ \mathcal{D}_3 \end{array}$$




## STEPS FOR IMPLEMENTING FUNCTION USING MUX

Implement  $f(A,B,C) = \sum(0,1,4,7)$  using 4:1 MUX

let  $A$  be the input line,  $B$  &  $C$  be the select line

BC →

	00	01	10	11
$\bar{A}$ 0	0 000	1 001	2 010	3 011
A 1	4 100	5 101	6 110	7 111
	1 $D_0$	$\bar{A}$ $D_1$	0 $D_2$	A $D_3$

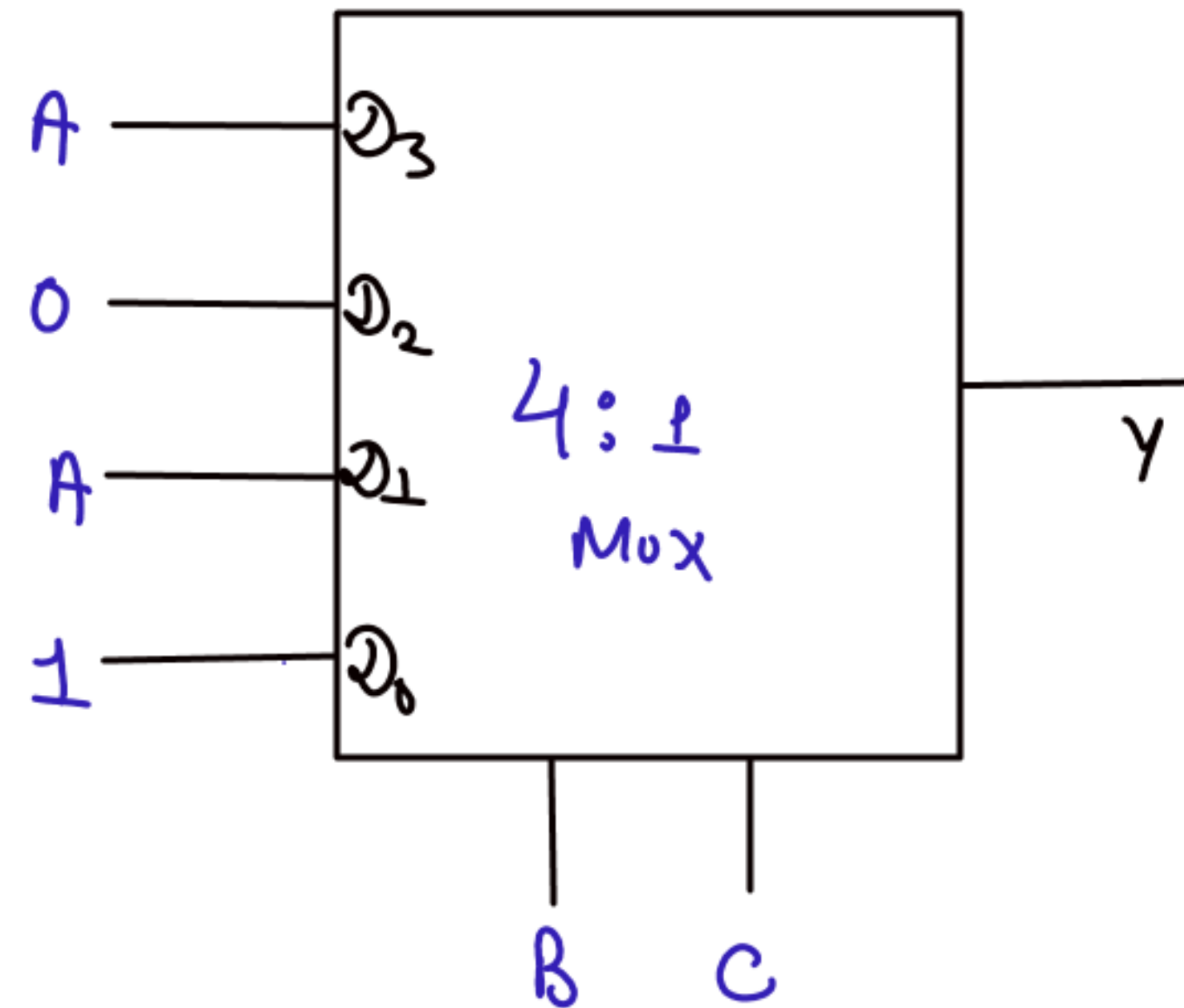


## STEPS FOR IMPLEMENTING FUNCTION USING MUX

Implement  $f(ABCD) = \sum m(2, 3, 4, 5, 8, 9, 12)$  using 8:1 MUX


Let  $A$  be the Input line &  $BCD$  be the Select line

$BCD \rightarrow$

	000	001	010	011	100	101	110	111
$\bar{A} \ 0$	0 0000	1 0001	2 0010	3 0011	4 0100	5 0101	6 0110	7 0111
$A \ 1$	8 1000	9 1001	10 1010	11 1011	12 1100	13 1101	14 1110	15 1111
	$A$ $D_0$	$A$ $D_1$	$\bar{A}$ $D_2$	$\bar{A}$ $D_3$	1 $D_4$	$\bar{A}$ $D_5$	0 $D_6$	0 $D_7$

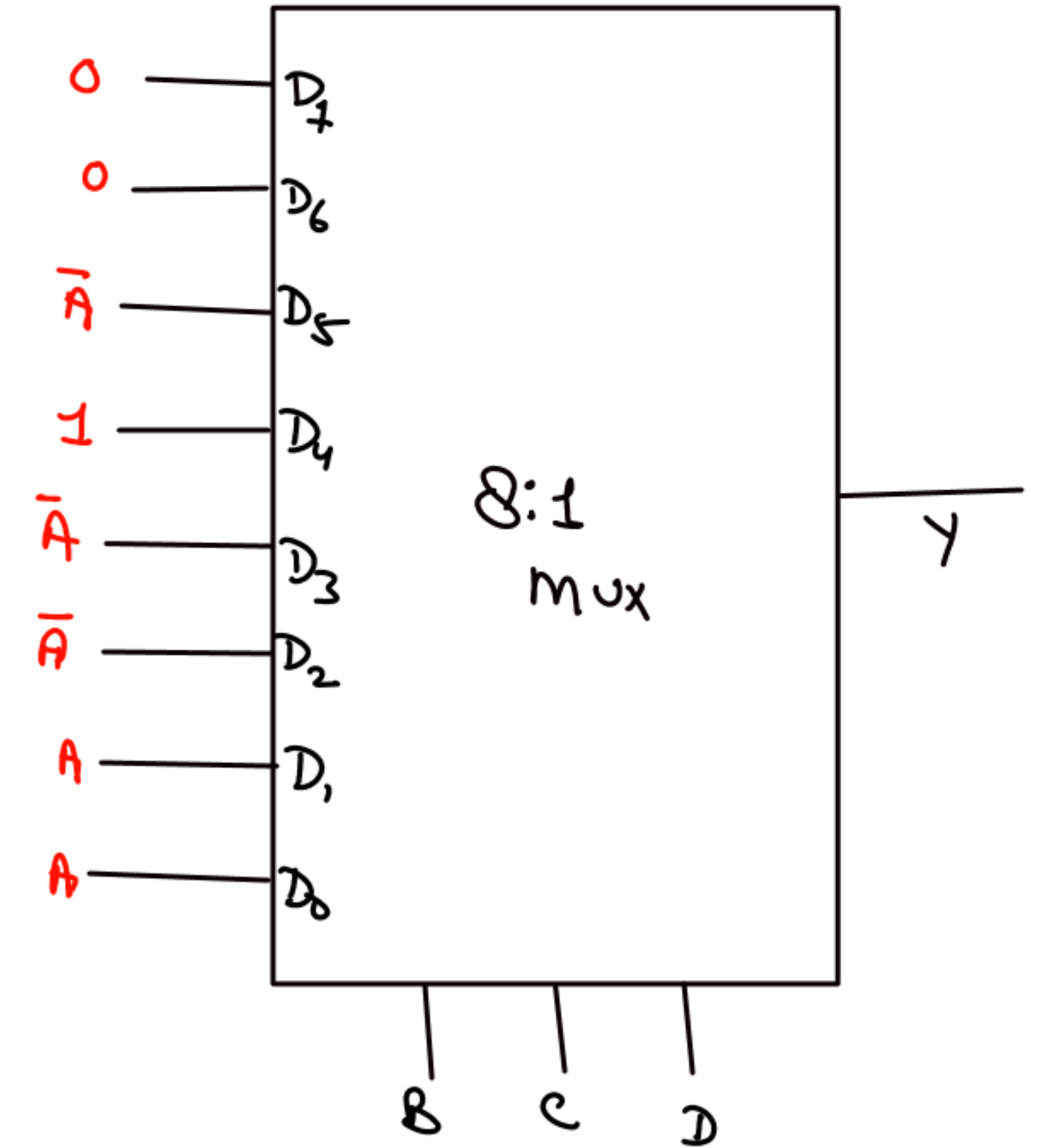
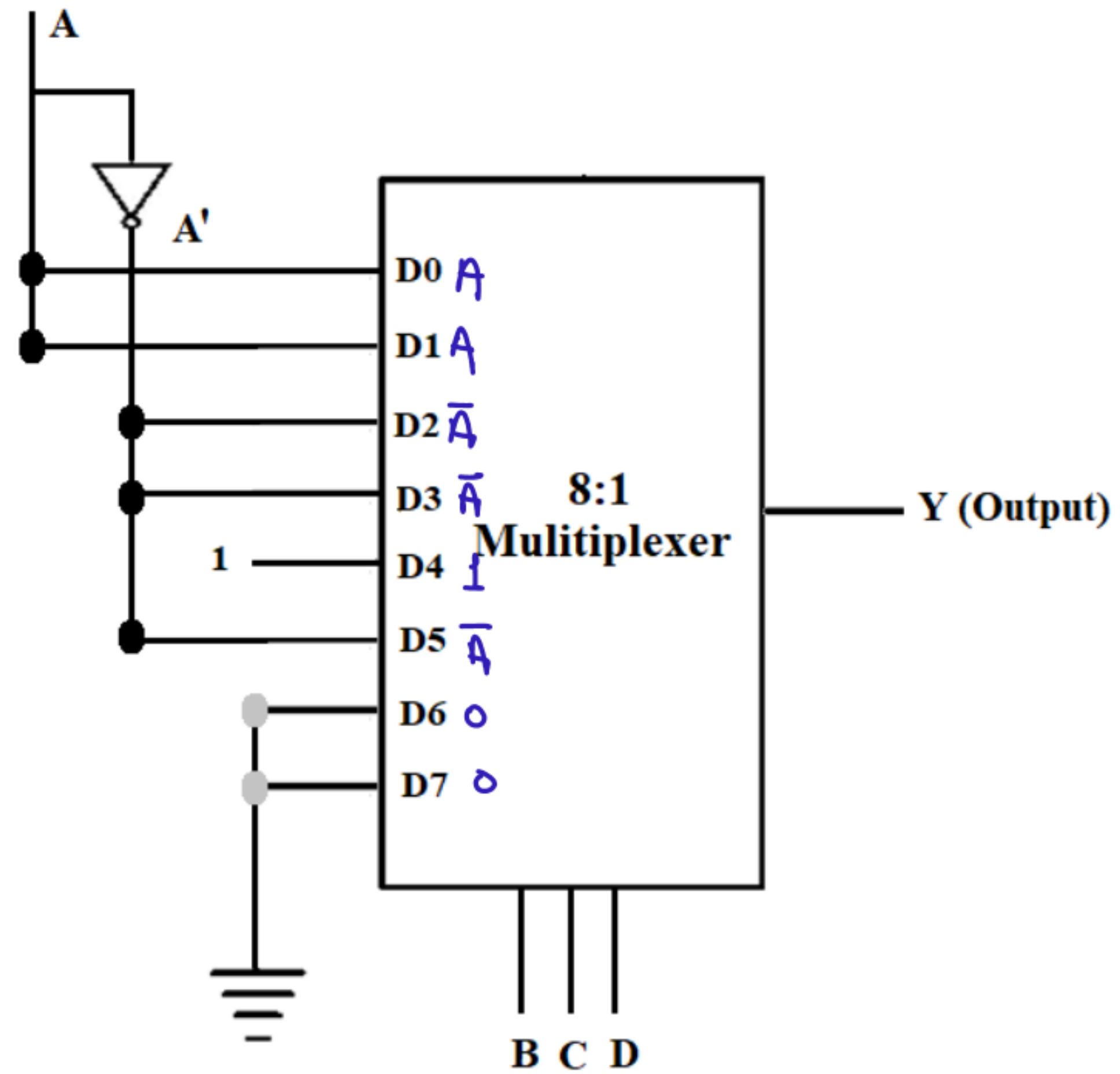
## STEPS FOR IMPLEMENTING FUNCTION USING MUX







# IMPLEMENTATION OF LOGIC GATES USING MUX

The multiplexer is a universal logic. So we can perform any logical function using the multiplexer

### AND Gate using 2:1 Multiplexer

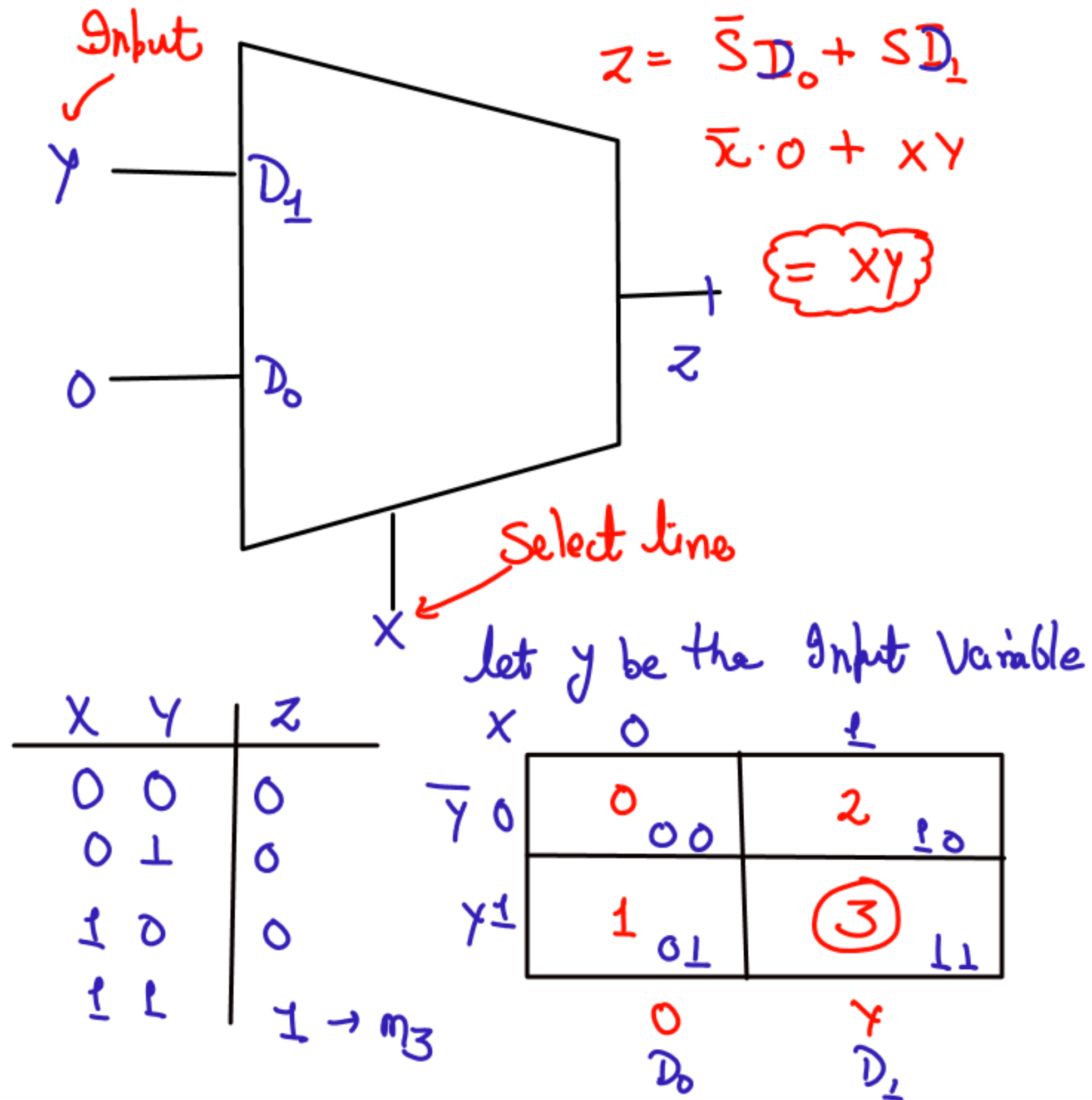


### OR Gate using 2:1 Multiplexer

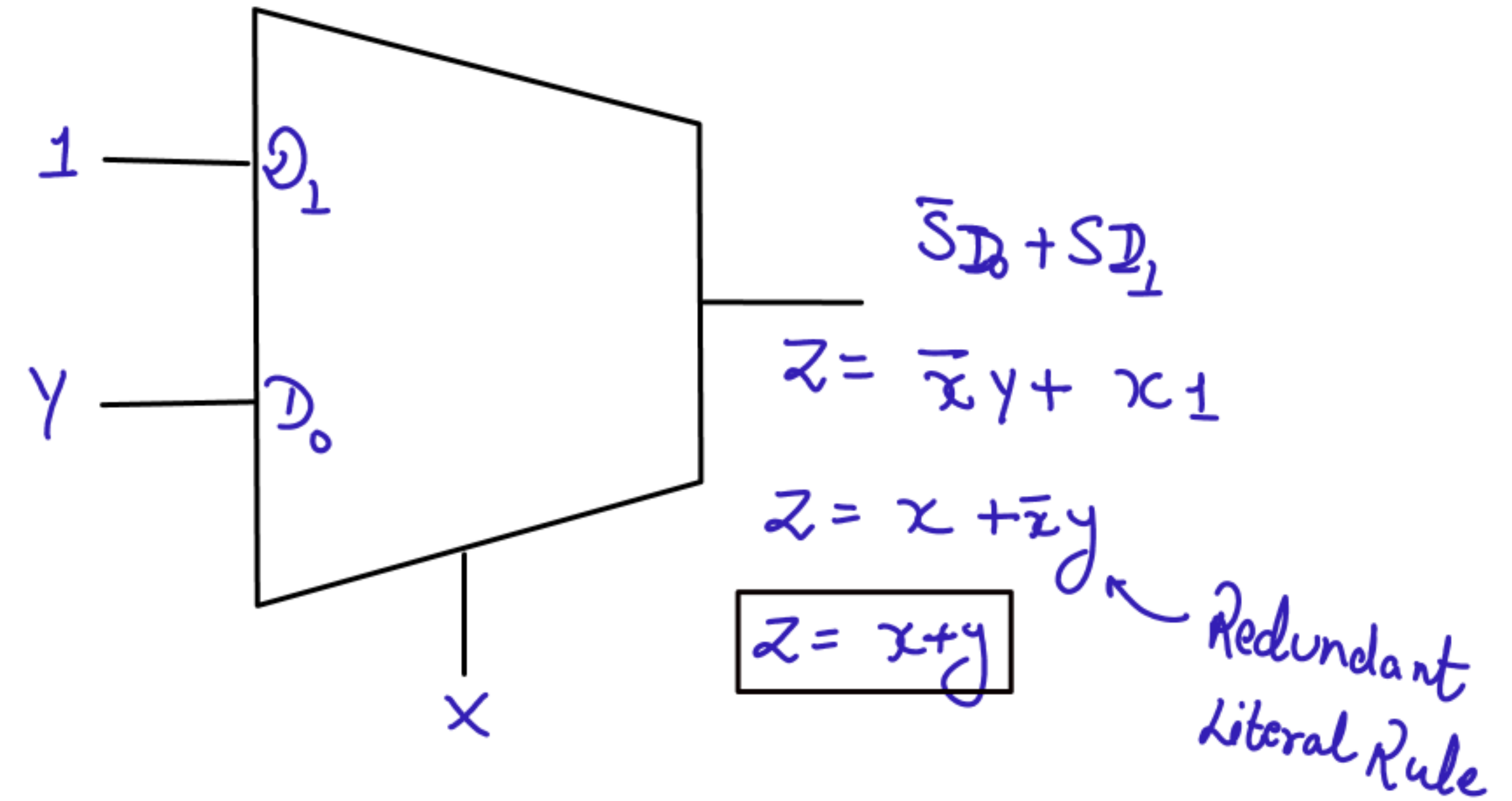


## IMPLEMENTATION OF LOGIC GATES USING MUX

NOT Gate using 2:1 Multiplexer

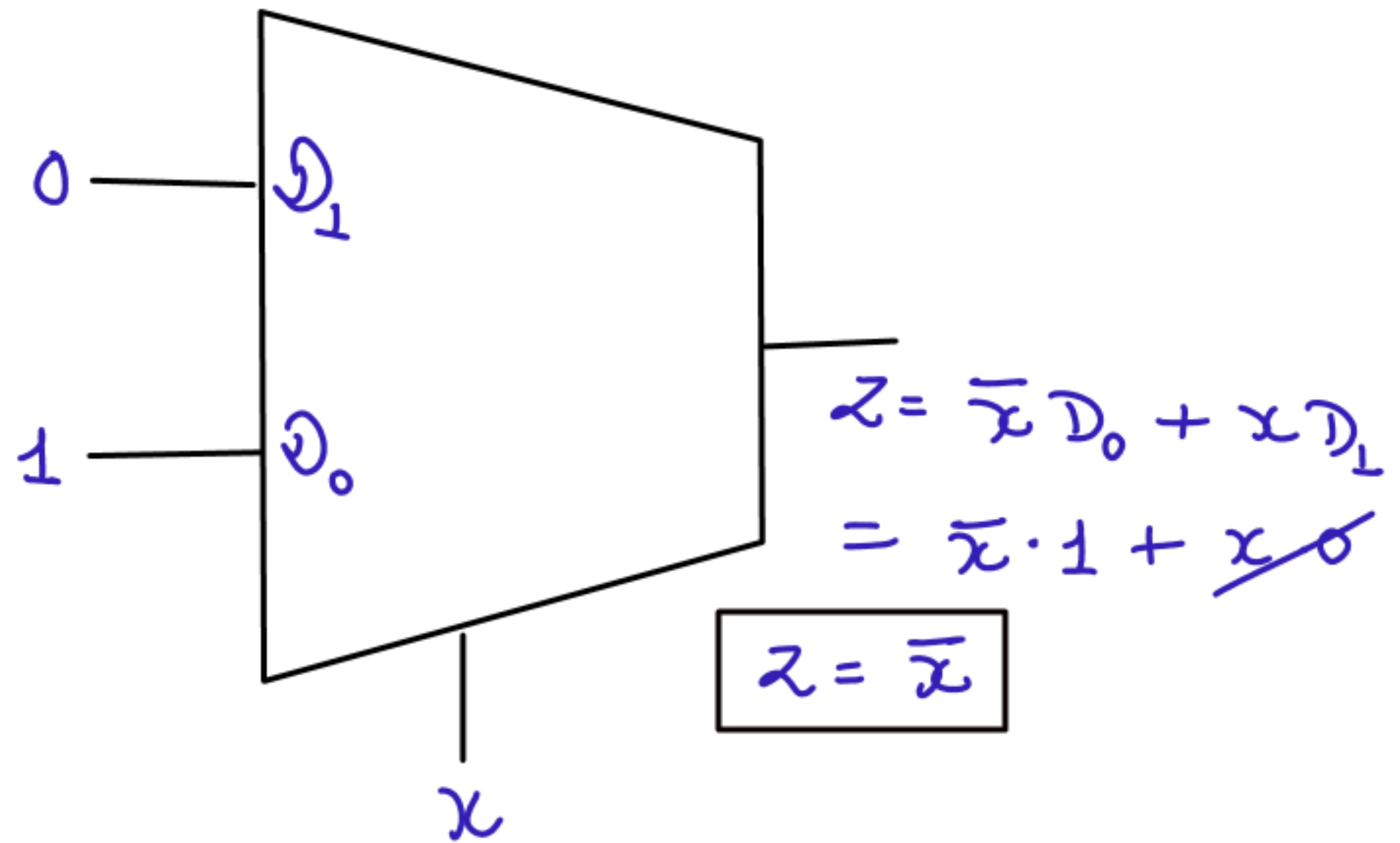


NAND Gate using 2:1 Multiplexer

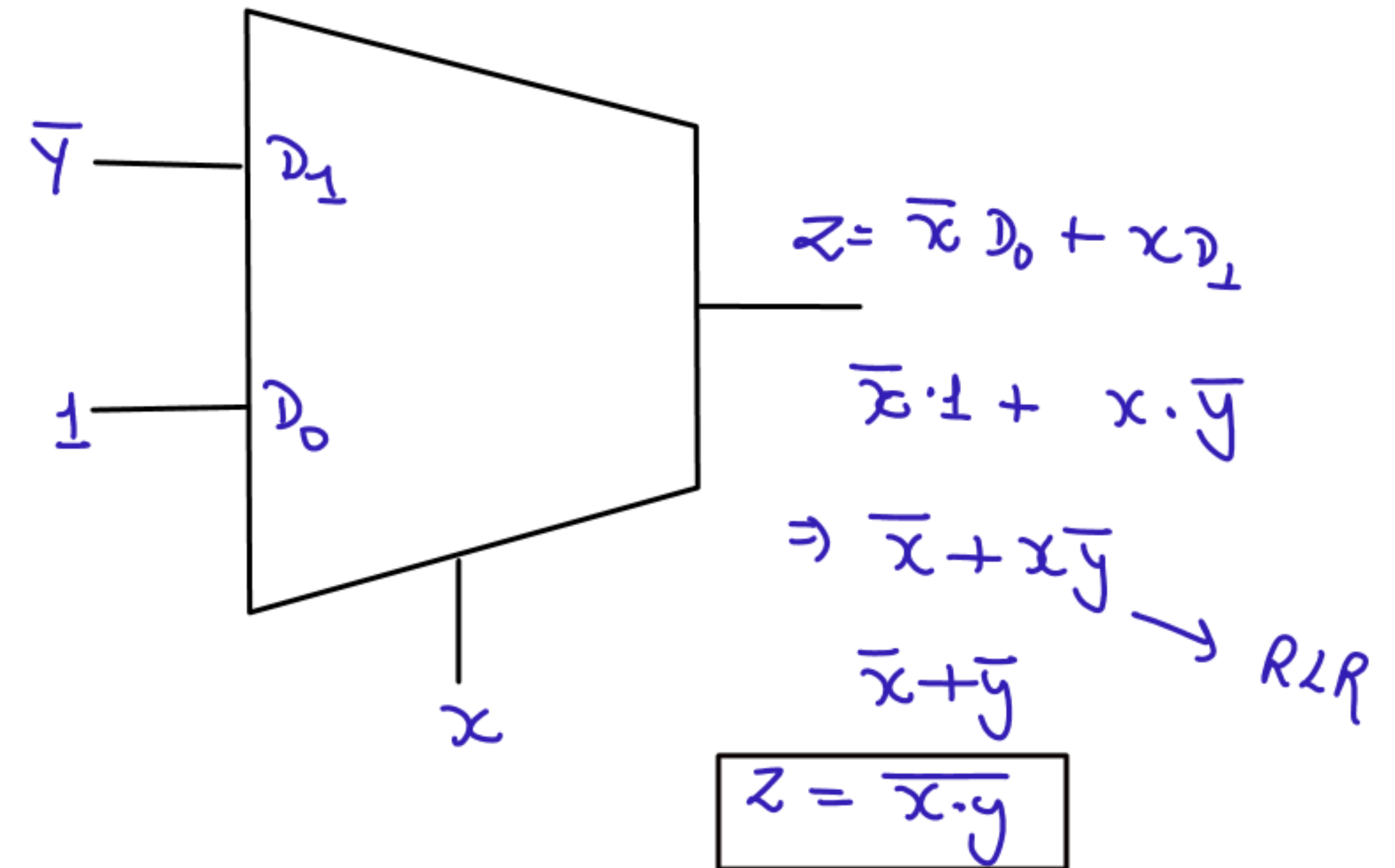


# IMPLEMENTATION OF LOGIC GATES USING MUX


## NOR Gate using 2:1 Multiplexer

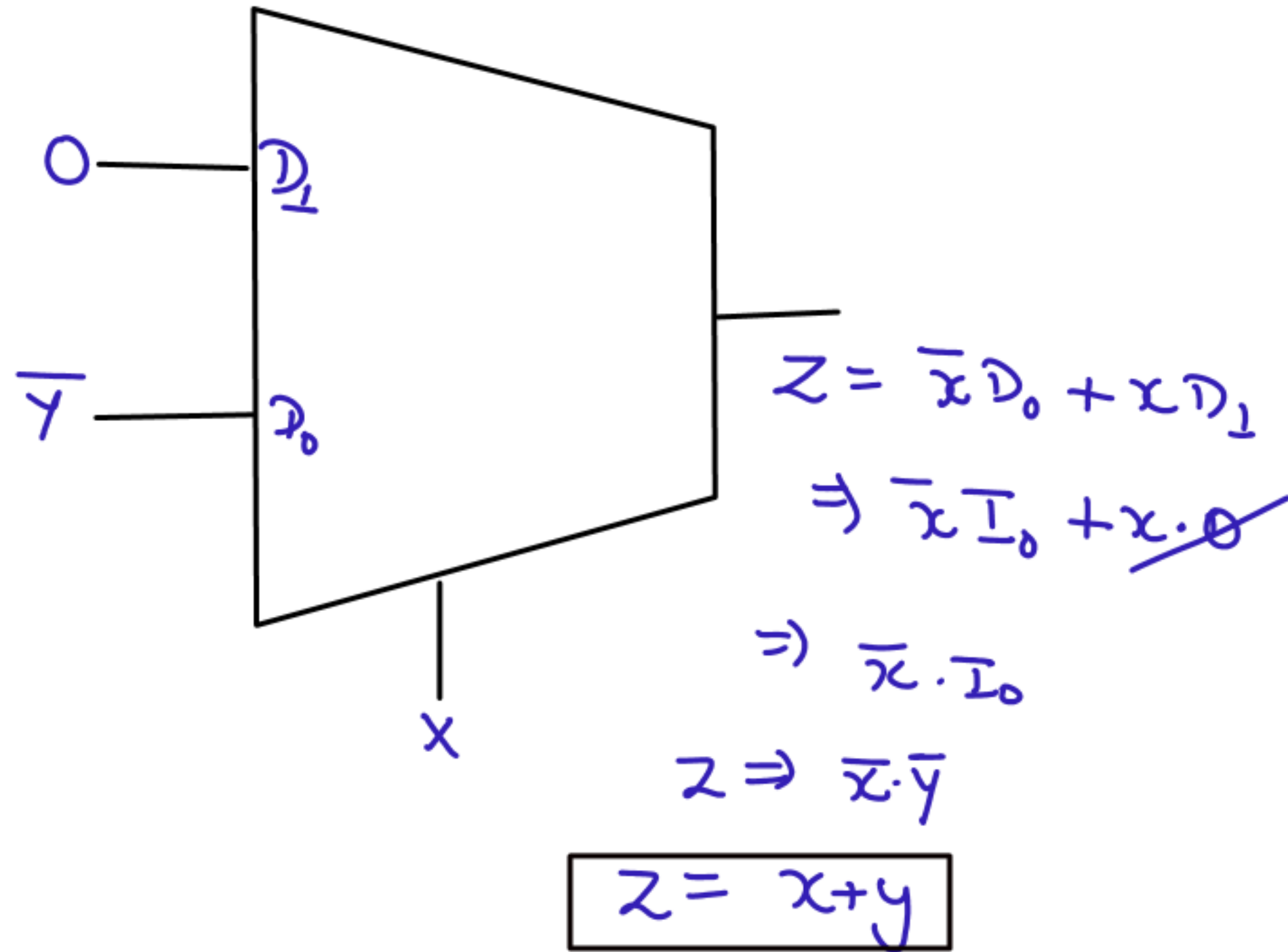


## XOR Gate using 2:1 Multiplexer

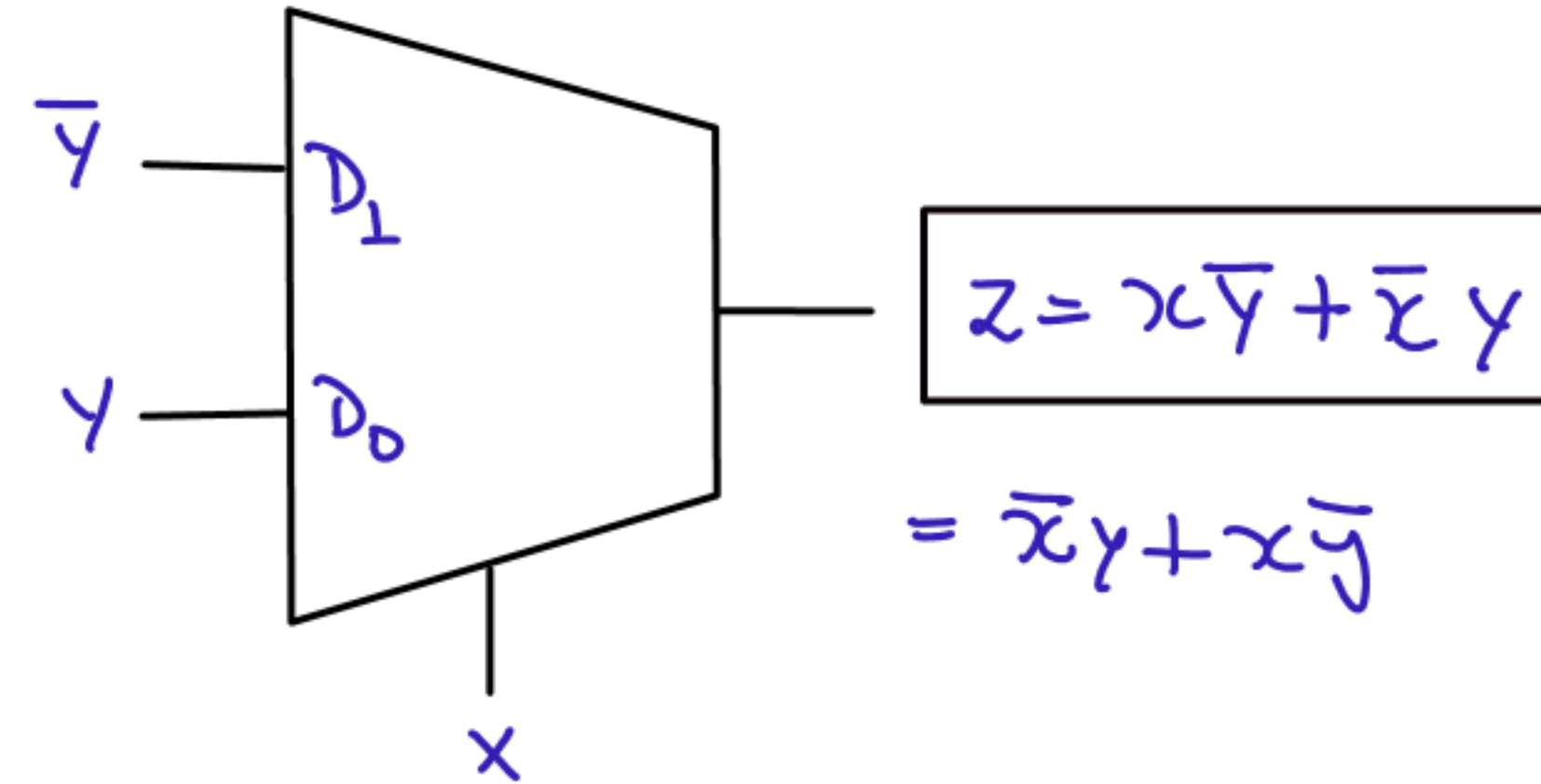

## XNOR Gate using 2:1 Multiplexer

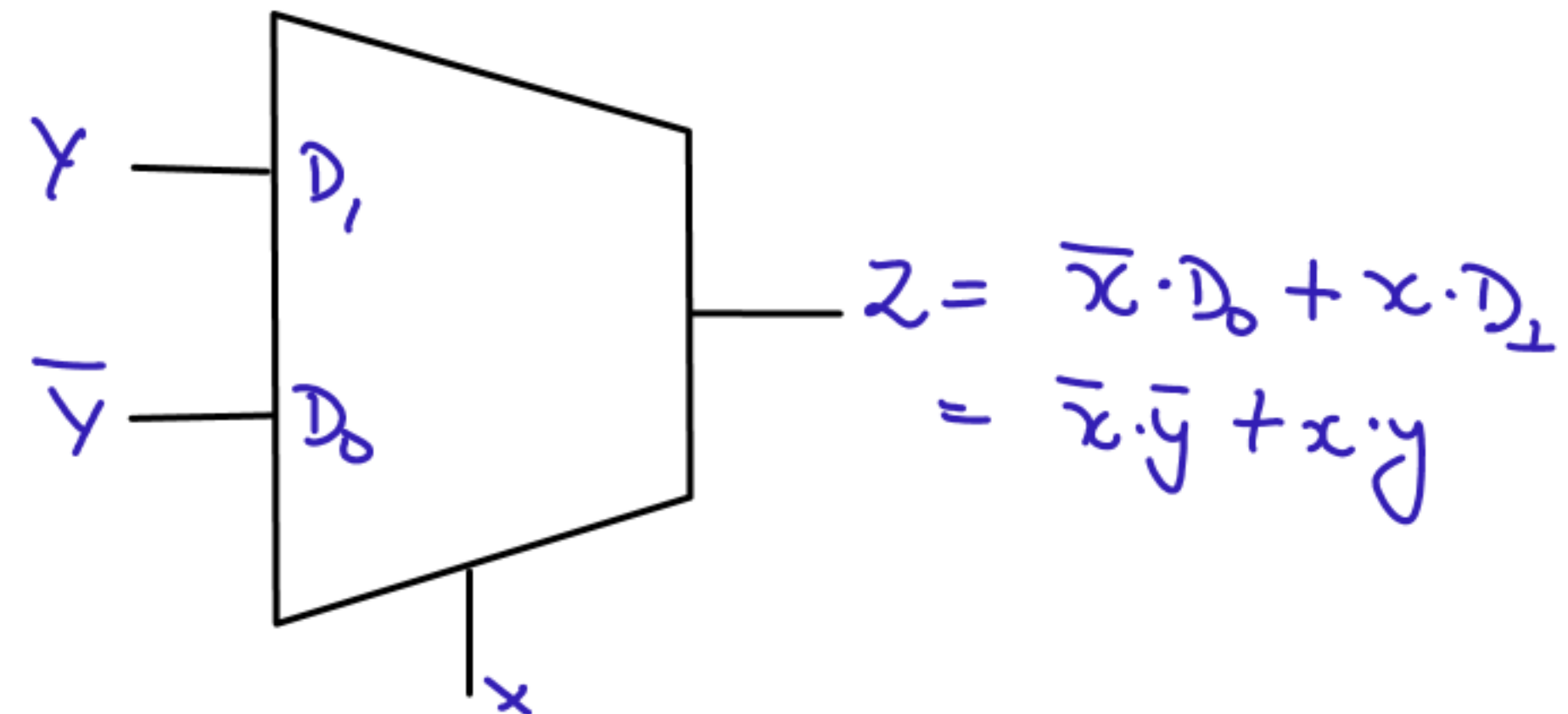

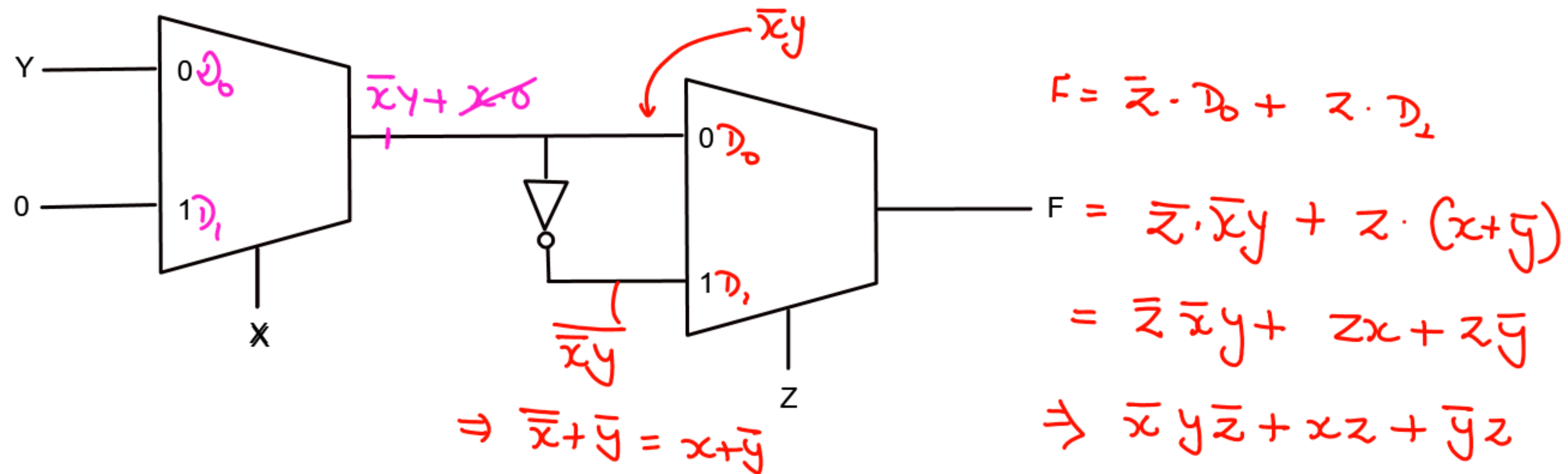Consider the circuit shown in the figure.



The Boolean expression F implemented by the circuit is

☐ A  $\bar{X}\bar{Y}\bar{Z} + XY + \bar{Y}Z$

☒ B  $\bar{X}Y\bar{Z} + XZ + \bar{Y}Z$

☐ C  $\bar{X}Y\bar{Z} + XY + \bar{Y}Z$

☐ D  $\bar{X}\bar{Y}\bar{Z} + XZ + \bar{Y}Z$



## HALF ADDER USING 4:1 MUX

A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## HALF ADDER USING 2:1 MUX

A	B	Sum (S)	Carry (C)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## HALF SUBTRACTOR USING 2:1 MUX

A	B	Difference (D)	Borrow (B)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0