

# DECODERS AND ENCODERS (PART 02)



# Implementation of MUX using Decoder

To implement Multiplexer using Decoder,

- The Inputs of decoder act like 'Select Line' of MUX
- The output of decoder will enable the Tri-State Buffer or AND gate to pass input to

the output

INPUTS		OUTPUTS			
A1	A0	D0	D1	D2	D3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 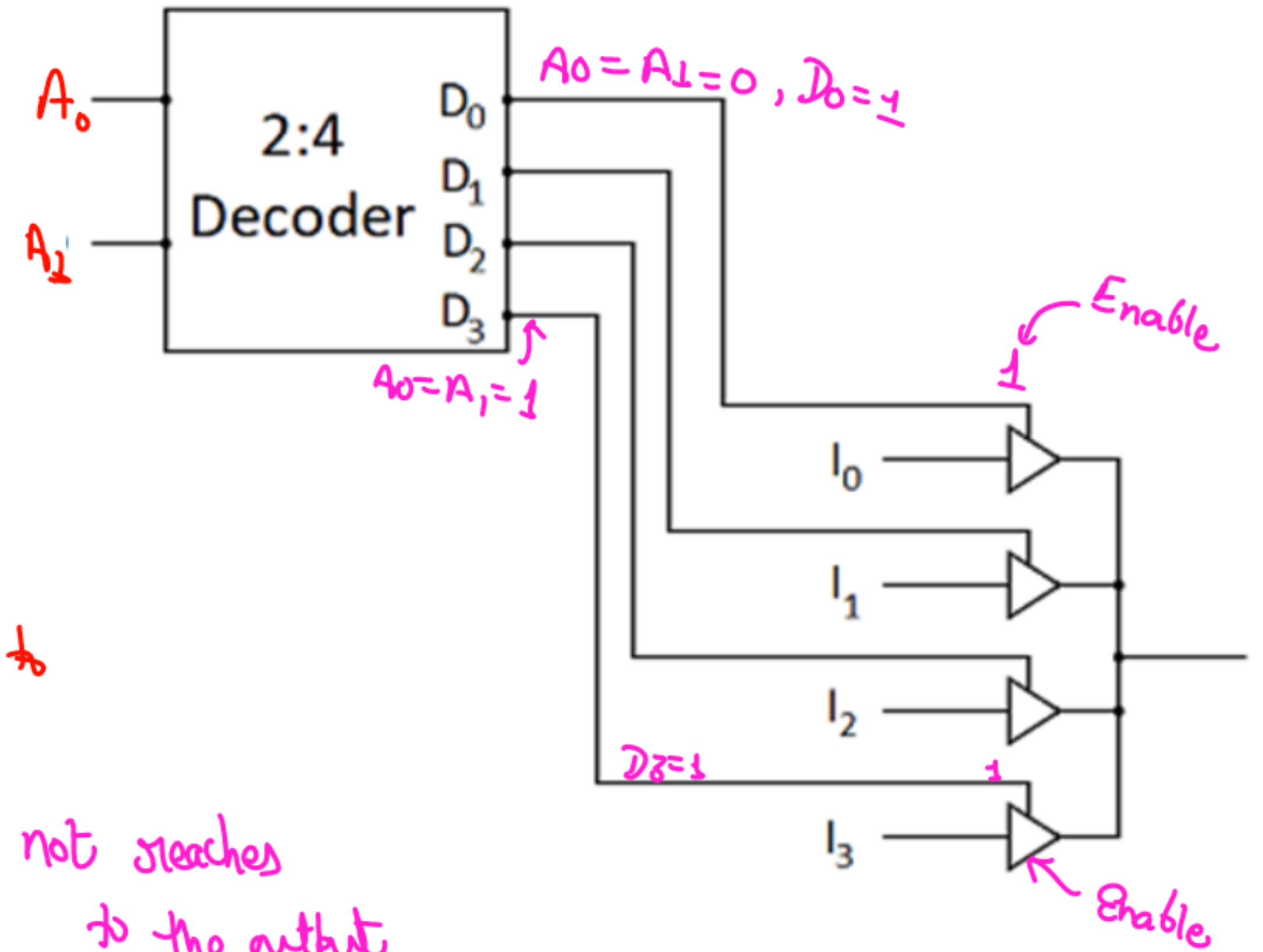

$E=1$  (Activate)  $Y=A$   
 $E=0$  (disabled)

E	A	Y
1	0	0
1	1	1
0	X	X

} Input reach to output

Input will not reaches

to the output


(undefined state)  
 [or High-z state]

} output is NOT zero

# Implementation 8:1 MUX using 3:8 Decoder

Truth table for 8:1 MUX

Enable	Select Inputs			Output
E	S2	S1	S0	Y
0	X	X	X	0
1	0	0	0	$I_0$
1	0	0	1	$I_1$
1	0	1	0	$I_2$
1	0	1	1	$I_3$
1	1	0	0	$I_4$
1	1	0	1	$I_5$
1	1	1	0	$I_6$
1	1	1	1	$I_7$

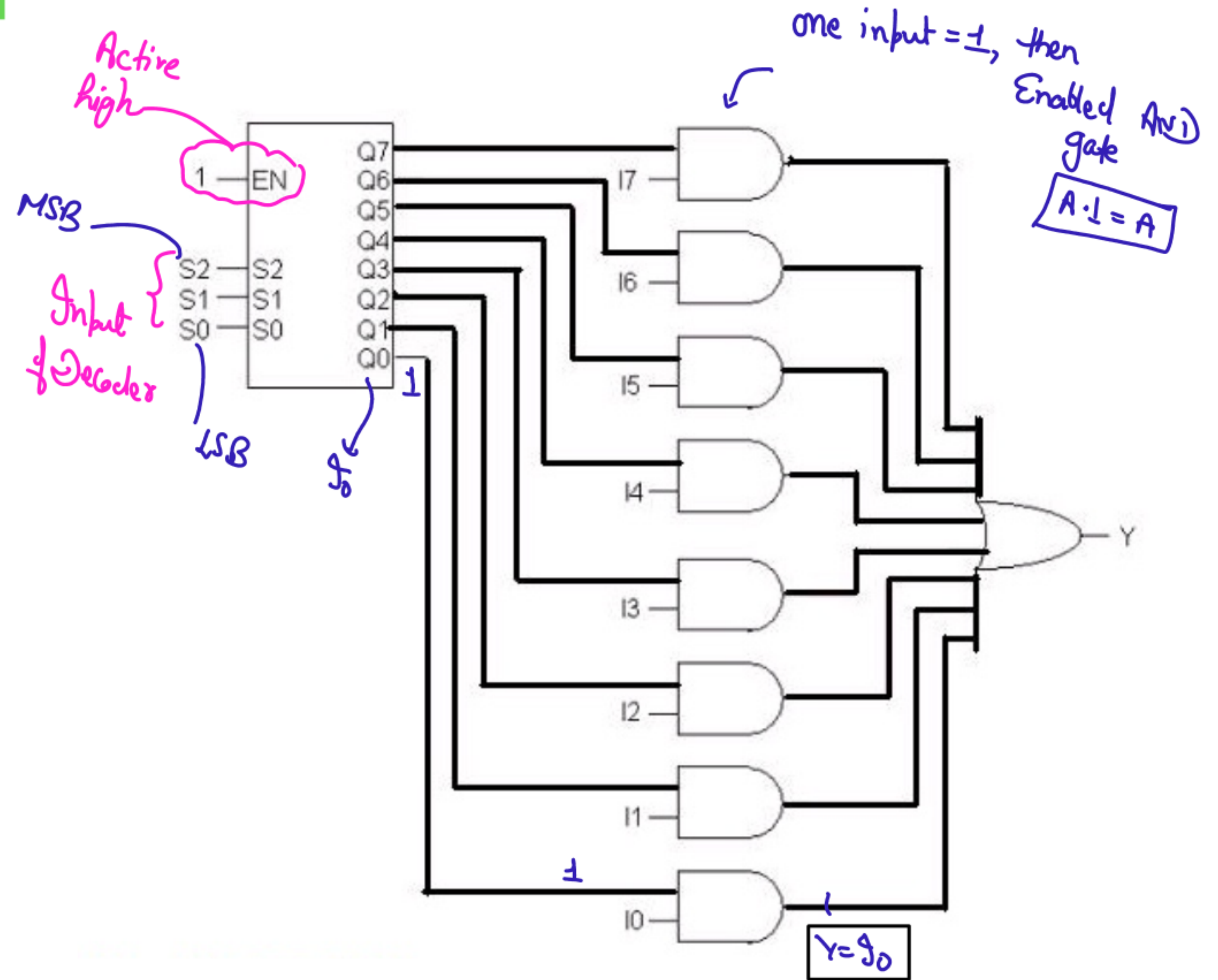

# Implementation of high order Decoder to Low order Decoder

## High order decoder to low order decoder

If we have  $y: 2^y$  decoder that has to be designed by  $x: 2^x$  decoder, then

$$\frac{2^y}{2^x} = K1 \rightarrow n^{\text{th}} \text{ Stage} \rightarrow \text{last stage}$$

$$\frac{K1}{2^x} = K2 \rightarrow n-1^{\text{th}} \text{ Stage}$$

.

.

Till we get 1 or Fraction ← Point (MSB at first stage)

For Fraction we use NOT gate at first stage to Enable the corresponding decoder




# Implement 3:8 Decoder using 2:4 Decoder

$$\frac{2^3}{2^2} = \frac{8}{4} = 2 \leftarrow \text{last stage}$$

$$\frac{2}{4} = 0.5 \leftarrow \text{fraction (Not gate at first stage)}$$

$I_2$	$I_1$	$I_0$	$y$
0	0	0	$m_0$ $Q_0$
0	0	1	$m_1$ $Q_1$
0	1	0	$\vdots$ $Q_2$
0	1	1	$\vdots$ $Q_3$
1	0	0	$\vdots$ $Q_4$
1	0	1	$\vdots$ $Q_5$
1	1	0	$\vdots$ $Q_6$
1	1	1	$m_7$ $Q_7$

first 4 output

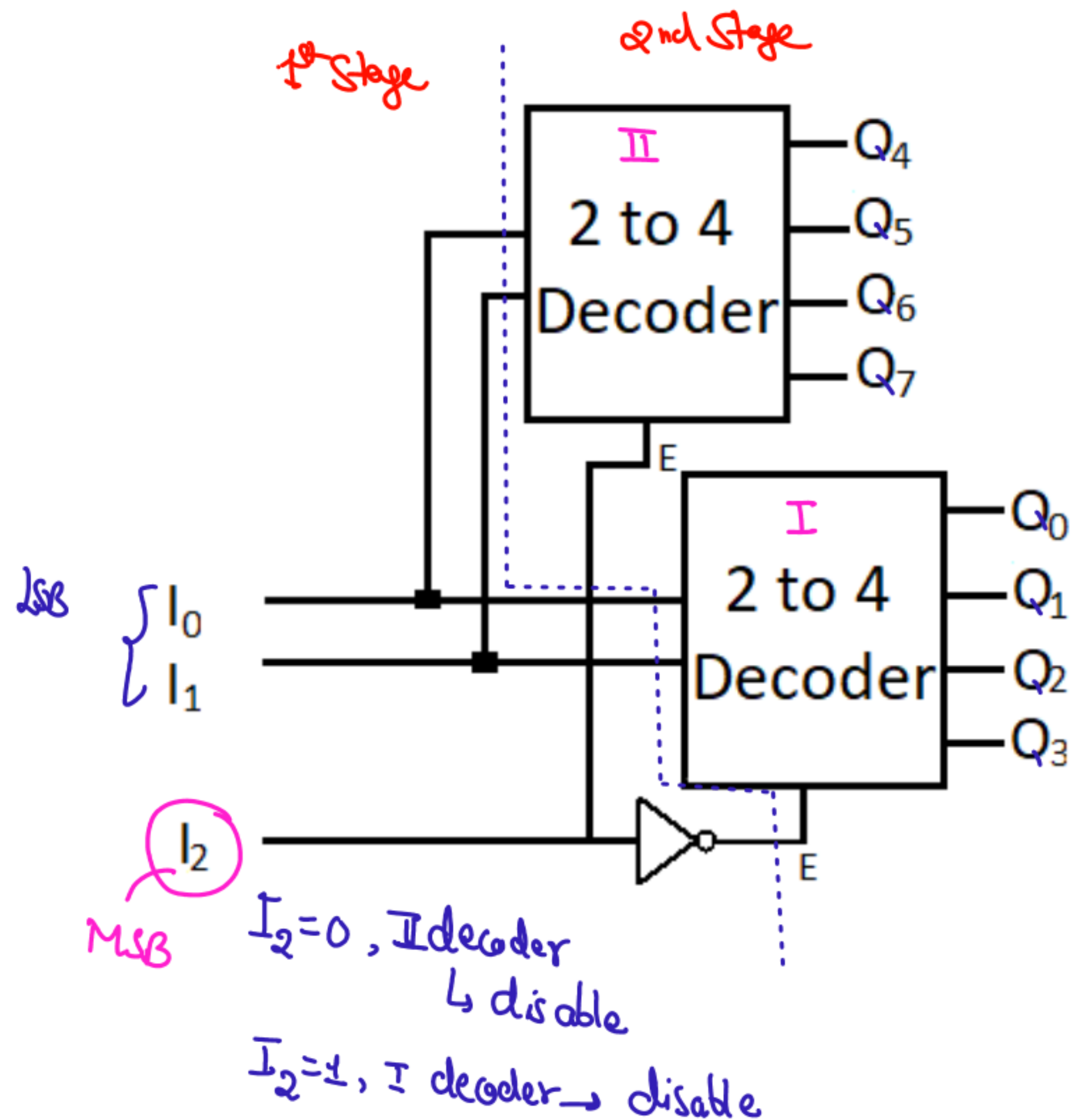

# Implement 4:16 Decoder using 2:4 Decoder

High order  
Low order

$\frac{16}{4} = 4 \leftarrow \text{last stage (LSB)}$


$\frac{4}{4} = 1 \leftarrow \text{1st Stage} \rightarrow 1 \text{ decoder}$

2 inputs  
msb

for input  
 $I_3 I_2 I_1 I_0$   
msb  
1st Stage  
last Stage  
LSB




Make Truth Table

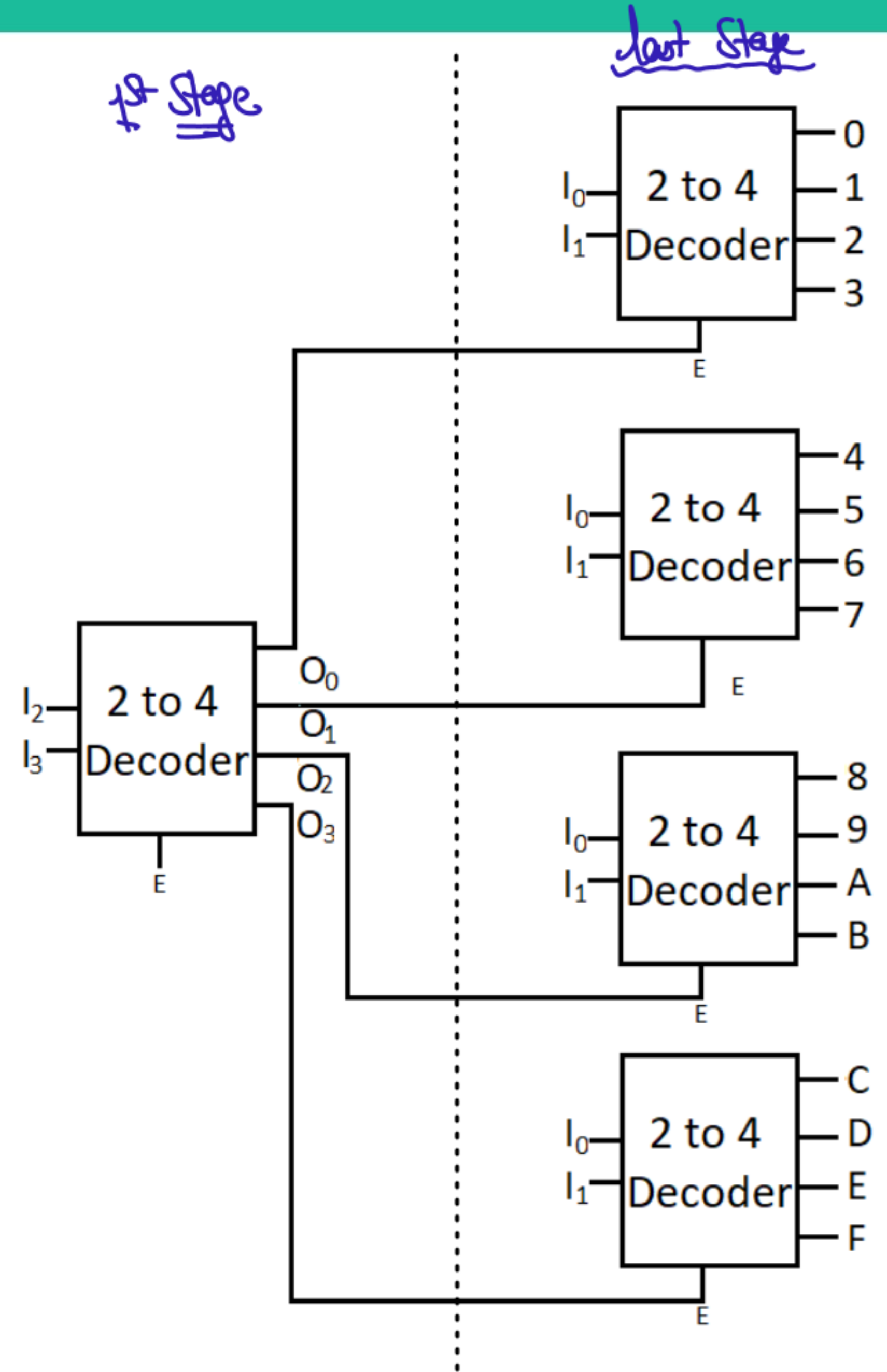$I_3 I_2 I_1 I_0$   
00 0 0  
01  
10  
11



   
# 7 Segment Decoder

A 7-segment display is an electronic display device used to display decimal numerals and some alphabets. It consists of seven LEDs (segments) arranged in a way to display numbers from 0 to 9 and a few characters like A, b, C, d, E, F, etc.



LEDs

Example:

 



## 7 Segment Decoder

For each output, we have to design K-Map to get simplified expression.

\* We need to K-Map for each LED to glow with a certain combinations of input

$$a = \sum m(0, 2, 3, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15) \quad (\text{common for all})$$

$$b = \sum m(0, 1, 2, 3, 4, 7, 8, 9)$$


$$c = \sum m(0, 1, 3, 4, 7, 8, 9)$$

$$d = \sum m(0, 2, 3, 5, 6, 8, 9)$$

$$e = \sum m(0, 2, 6, 8)$$








$$f = \sum m(0, 4, 5, 6, 8, 9)$$

$$g = \sum m(2, 3, 4, 5, 6, 8, 9)$$

 

Decimal Digit	Input lines				Output lines							Display pattern
	A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	0
1	0	0	0	1	0	1	1	0	0	0	0	1
2	0	0	1	0	1	1	0	1	1	0	1	2
3	0	0	1	1	1	1	1	1	0	0	1	3
4	0	1	0	0	0	1	1	0	0	1	1	4
5	0	1	0	1	1	0	1	1	0	1	1	5
6	0	1	1	0	1	0	1	1	1	1	1	6
7	0	1	1	1	1	1	1	0	0	0	0	7
8	1	0	0	0	1	1	1	1	1	1	1	8
9	1	0	0	1	1	1	1	1	0	1	1	9

# 7 Segment Decoder

       



## 7 Segment Decoder - Circuit Diagram

